



COMPUTER SCIENCE & IT

DIGITAL LOGIC




Lecture No. ||

Combinational Circuit



By- Chandan Gupta Sir



Recap of Previous Lecture

MUX & Question Discussion

DeMUX




Topics to be Covered

Question Discussion Cont.

[Question 7]



A digital circuit is as given below :

 

$$y = \overline{A}\overline{B}\cdot\overline{C} + \overline{A}B\cdot\overline{C} + A\overline{B}\cdot C + AB\cdot C$$

$$= \overline{A}\overline{C}(\overline{B}+B) + AC(\overline{B}+B)$$

$$= A\odot C$$


Output y is

- (a) ~~$A \oplus B \oplus C \Rightarrow C$~~ (b) ~~$A \odot C \Rightarrow \overline{C}, \overline{C}$~~
- (c) ~~$A \odot B \oplus C \Rightarrow C$~~ (d) ~~$A \oplus B \Rightarrow C$~~

 [Question 8]



A digital circuit is as given below : $= C \oplus S_1 \oplus S_0$




$$y = \bar{A} \bar{B} \cdot C + \bar{A} B \bar{C} + A \bar{B} \cdot \bar{C} + ABC$$


$$= \sum(1, 2, 4, 7) = A \oplus B \oplus C$$

Output is

 
- (a) $A \oplus B \oplus C$ C (b) $A \odot B \oplus C$ \bar{C}
- (c) $\overline{A \oplus B \odot C}$ \bar{C} (d) $A \oplus B$ 0


 
$$\begin{aligned}
 &= D \oplus S_1 \oplus S_0 \\
 &= \bar{C} \oplus \bar{A} \oplus B \\
 &= A \oplus B \oplus C
 \end{aligned}$$


 
$$\begin{aligned}
 &= C \oplus S_1 \oplus S_0 \\
 &= C \oplus \bar{A} \oplus \bar{B} \\
 &= C \oplus A \oplus B \\
 &= A \oplus B \oplus C
 \end{aligned}$$




$$\begin{aligned}
 &= AB \oplus S_1 \oplus S_0 \\
 &= A \oplus B \oplus AB \\
 &= (A+B)
 \end{aligned}$$


[Question 9]



A digital circuit is as given below :

 
 
$$y = \bar{B}\bar{C} \cdot 1 + \bar{B}C \cdot 1 + B\bar{C} \cdot 1 + B \cdot C \bar{A}$$



Above circuit works as :

(a) ☒ 3-input OR gate \bar{A}

(b) ☒ 3-input NOR gate \bar{A}

(c) ☒ 3-input AND gate 0

(d) ☒ 3-input NAND gate 1

Question 10 $1001 \rightarrow 9$ 0001
 $1011 \rightarrow 11$ 0011

A digital circuit is as given below:

Output y will be: $y(A, B, C, D)$

(a) $y = \Sigma(0, 3, 4, 6, 7, 9, 11, 12, 14, 15)$

(b) $y = \Sigma(0, 1, 3, 4, 6, 8, 9, 11, 12, 14, 15)$


(c) $y = \Sigma(0, 3, 4, 6, 9, 11, 12, 14, 15)$

(d) $y = \Sigma(0, 3, 4, 6, 9, 10, 11, 12, 14, 15)$

1010

$A=1, B=0, D=0$

 $= \Sigma(0, 3, 4, 6, 9, 11, 12, 14, 15)$



$+ A \bar{B} D \cdot 1$
 $+ A B \bar{D} \cdot 1$
 $+ A B D \cdot C \rightarrow 15$
 $y =$
 $\bar{A} \bar{B} \bar{D} \bar{C} \rightarrow 0$
 $+ \bar{A} \bar{B} C D \rightarrow 3$
 $+ \bar{A} B \bar{C} \bar{D}$
 $0100 \rightarrow 4$
 $0110 \rightarrow 6$

$$\overline{A} B D \cdot 0$$

$$\begin{array}{ccc} \overline{A} & B & D \\ 0 & 1 & 0 \rightarrow 5 \\ 0 & 1 & 1 \rightarrow 7 \end{array} \left. \vphantom{\begin{array}{ccc} \overline{A} & B & D \\ 0 & 1 & 0 \\ 0 & 1 & 1 \end{array}} \right\} X$$

$$A \overline{B} \overline{D} \cdot 0$$

$$\begin{array}{ccc} 1 & 0 & 0 \rightarrow 8 \\ 1 & 0 & 1 \rightarrow 10 \end{array} \left. \vphantom{\begin{array}{ccc} 1 & 0 & 0 \\ 1 & 0 & 1 \end{array}} \right\}$$

[Question 11]



A 4 : 1 multiplexer is used for generating output carry of a full adder. A and B are bits to be added while C_{in} is input carry and C_{out} is output carry. Which of the following is choice of signals at I_0, I_1, I_2, I_3 .

(a) $I_0 = 0, I_1 = C_{in}, I_2 = C_{in}, I_3 = 1$


(b) $I_0 = 1, I_1 = C_{in}, I_2 = C_{in}, I_3 = 1$

(c) $I_0 = C_{in}, I_1 = 0, I_2 = 1, I_3 = C_{in}$

(d) $I_0 = 0, I_1 = C_{in}, I_2 = 1, I_3 = C_{in}$

$A=0, B=1, \Rightarrow C_{out}=C_{in}, I_1=C_{in}$

$A=1, B=1, C_{out}=1, I_3=1$

 

$$C_{out} = AB + BC_{in} + AC_{in}$$

$$A=B=0 \Rightarrow C_{out} = 0 \\ I_0 = 0$$


$$C_{out}$$

$$A=1, B=0,$$

$$C_{out}=C_{in} \\ I_2=C_{in}$$

$y(A, B, C, D)$ will be

- e
- | | $\bar{C}\bar{D}$ | $\bar{C}D$ | CD | $C\bar{D}$ |
|------------------|------------------|------------|------|------------|
| $\bar{A}\bar{B}$ | | | 1 | |
| $\bar{A}B$ | 1 | 1 | 1 | |
| AB | 1 | 1 | | |
| $A\bar{B}$ | | | | |
- $B\bar{C} + \bar{A}CD$




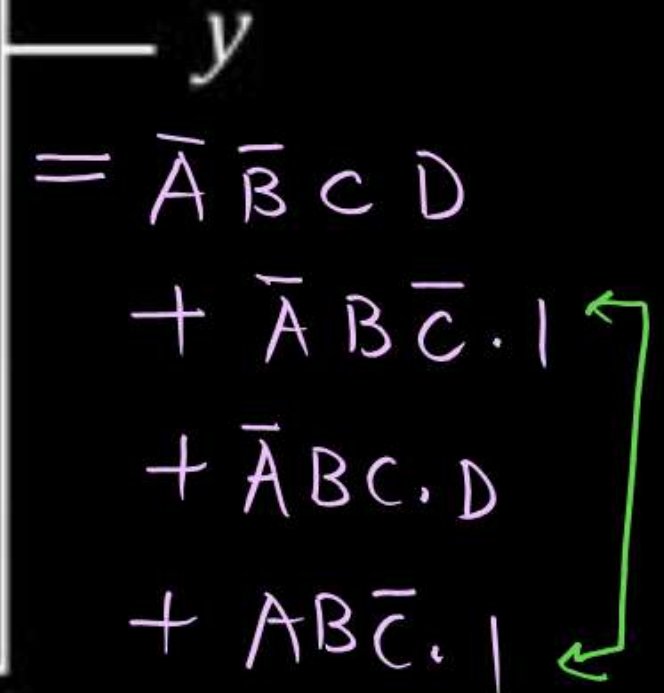


    [Question 13]



A logical function is given as : $f(A, B, C) = \overline{A}B + B\overline{C} + AB = \sum ($

Its implementation using MUX is given below. Then which implementation is correct



	I_0	I_1	I_2
0 \overline{A}	0	1	2
1 A	4	5	6

$$B=0, C=0$$

$$f(A, B=0, C=0)$$

$$= 1, I_0 = 1$$

$$B=0, C=1, f(A, B, C) =$$


$$B=1, C=0, f(A, B, C) = A$$

$$B=1, C=1, f(A, B, C) = A$$

Question 14



A MUX circuit is as given below :

 

Delay of each NOT gate $t_{\text{not}} = 4$ nsec, delay of AND gate is $t_{\text{AND}} = 3$ nsec, delay of OR gate is $t_{\text{OR}} = 4.5$ nsec and delay of each MUX is 5 nsec. If P , Q , R , S are applied at $t = 0$, then maximum delay in generating output y is 18 nsec.

[H.A. and F.A. using 2 : 1 MUX]



- H.A. using 2 : 1 MUX :

$$\left. \begin{array}{l} S = x \oplus y \longrightarrow 2 (2:1) \text{ MUX} \\ C = x \cdot y \longrightarrow 1 (2:1) \text{ MUX} \end{array} \right\} 3 (2:1) \text{ MUX}$$

Note: • 3 (2:1) MUX is required to implement H.A or H.S.

- 7 (2:1) MUX is required to implement F.A or F.S.


[DeMUX]




What is DeMUX?

↳ It is combinational CKT having one i/p & many o/p and on the basis of select line i/p is transferred to one of the o/p line.


- 1 : 2 DeMUX

 

Internal Circuit

 


- 1 : 4 DeMUX

 

$$S_1 = 1, S_0 = 0 \Rightarrow \begin{aligned} y_0 &= 0 \\ y_1 &= 0 \\ y_2 &= I \\ y_3 &= 0 \end{aligned}$$

Internal Circuit

 

[Higher order DeMUX using lower order DeMUX]



- $1:4$ $\xrightarrow{\text{Using } 1:2}$ $2+1=3=2^2-1$
 $1:2^2$
- $1:8$ $\xrightarrow{\text{Using } 1:2}$ $4+2+1=7=2^3-1$
 $1:2^3$
- $1:16$ $\xrightarrow{\text{Using } 1:2}$ $8+4+2+1=15=(2^4-1)$
 $1:2^4$
- $1:2^n$ $\xrightarrow{\text{Using } 1:2}$ (2^n-1)


- $1 : 16 \xrightarrow{\text{Using } 1 : 4} 4 + 1$
- $1 : 32 \xrightarrow{\text{Using } 1 : 4} \left(\frac{8 + 2}{(1:4)} \right) + 1(1:2) = 11(1:4)$
One (1:4) will be used as (1:2)
- $1 : 64 \xrightarrow{\text{Using } 1 : 8} 8 + 1$
- $1 : 256 \xrightarrow{\text{Using } 1 : 8} \left(\frac{32 + 4}{(1:8)} \right) + 1(1:4) = 37(1:8)$
One (1:8) will be used as (1:4).

$$(1:8) \xrightarrow{1:2} 4+2+1$$

$$\hookrightarrow s_2, s_1, s_0$$

$$\hookrightarrow I, y_0 - y_7$$

$$s_2 s_1 s_0 = 101$$

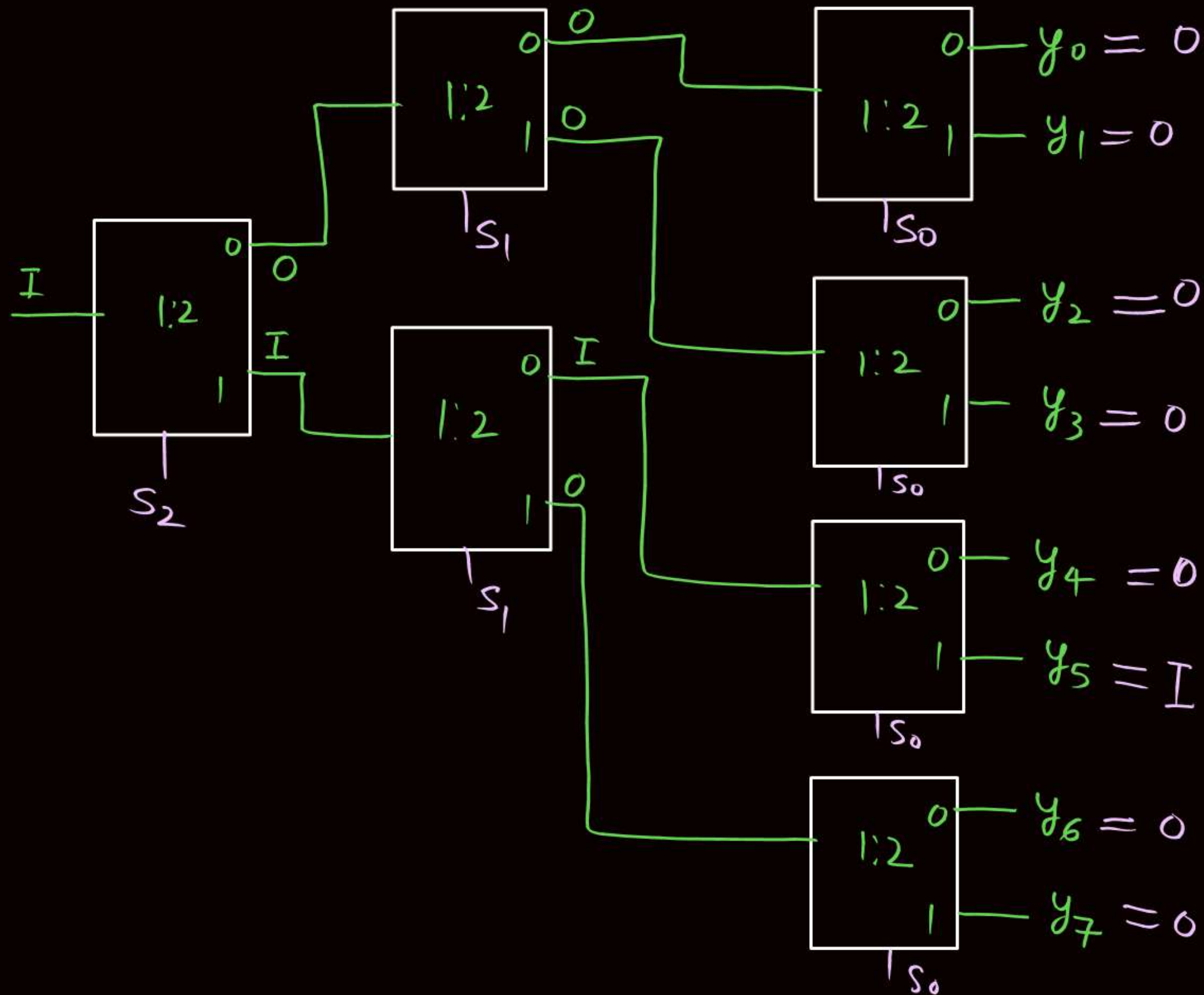

Q. Implement (1:8) DeMUX using (1:4) DeMUX.

Q. Implement (1:32) DeMUX using (1:8) DeMUX.



2 Minute Summary

- MUX & Question Discussion
- De MUX.

Thank you

GW
Soldiers !

