

# COMPUTER SCIENCE & IT

## DIGITAL LOGIC



## Sequential Circuits

Practice Sheet 01 Discussion Notes

**By- Chandan Gupta Sir**





In a S-R flip-flop, the present output is  $Q = 1$ . then after applying input  $S = 0$ ,  $R = 1$  and then  $S = 0$ ,  $R = 0$ , output will be:

$$Q(n) = 1$$

$$S=0, R=1 \rightarrow Q(n+1) = 0$$

$$S=0, R=0 \rightarrow Q = 0$$

☒ **A**  $Q = 0$

☐ **B**  $Q = 1$

☐ **C**  $Q = \rightarrow$  invalid state

☐ **D** None of these

In a JK flip-flop output  $Q = 0$ . To change it to  $Q = 1$ , the inputs J and K will be:

$$Q(n)=0 \longrightarrow 1 \quad Q(n+1)$$

$$J=1 \quad K=X$$

$$\begin{array}{l} J=1, K=1 \\ J=1, K=0 \end{array} \longrightarrow J=1, K=X$$

**A**  $J=1, K=1$

**B**  $J=1, K=X$

**C**  $J=0, K=0$

**D**  $J=0, K=1$

Which of the following is true?

- A**  $S = 1, R = 1$ , is a valid state input for S-R ff ✗
- B**  $J = 1, K = 1$  is a invalid state input for J-K ff ✗
- C** Input (0, 0) is hold state input for both S-R as well as JK ff ✓
- D** None of these





A flip flop has characteristic equation

$$Q(n+1) = \bar{A}\bar{Q} + \bar{B}Q$$

$$B=1, A=0$$

$$Q(n+1) = \bar{Q} \rightarrow \text{toggle mode of operation}$$

Then it will be in toggle mode of operation if

$$Q(n+1) = \bar{0}\bar{Q} + \bar{1}Q = \bar{Q} + 0 = \bar{Q}$$


☐ **A**  $A=1, B=1$

☒ **B**  $A=0, B=1$

☐ **C**  $A=1, B=0$

☐ **D**  $A=0, B=0$

A logic circuit is as given below:

 

Then which of the following is true about above circuit?

NAND  $S=0, R=0$   
invalid state

NOR  $\rightarrow S=1, R=1 \rightarrow$  invalid state

- ☒ **A** Race around condition at  $J = 1, k = 1$  ✗
- ☒ **B** Race around condition at  $J = 0, k = 0$  ✗
- ☒ **C**  $J = 1, K = 1$  is invalid state input ✗
- ☒ **D** None of these

In J-K FF, to change output from 0 to 1 input is changed from

☒ A  $J = 0, K = 0$  to  $J = 0, K = 1$

☒ B  $J = 0, K = 1$  to  $J = 1, K = 0$

☒ C  $J = 0, K = 1$  to  $J = 0, K = 0$

☒ D  $J = 1, K = 0$  to  $J = 0, K = 1$

$J = 0, K = 1 \rightarrow 0$   
 $J = 1, K = 0 \rightarrow 1$

$J = 0, K = 0 \rightarrow 0$   
 $J = 1, K = 0 \rightarrow 1$




Which of the following statement is **true**?

- ☒ **A** Master-Slave ff is used to avoid race-around condition.
- ☐ **B** Edge triggered J-K FF has problem of race-around condition when  $J = 1, K = 1$
- ☐ **C** Race-around condition occurs in S-R ff with  $S = 1, R = 1$
- ☐ **D** None of these



To solve the problem of invalid state at input  $S = 1$  and  $R = 1$  in S-R ff, S and R are replaced by
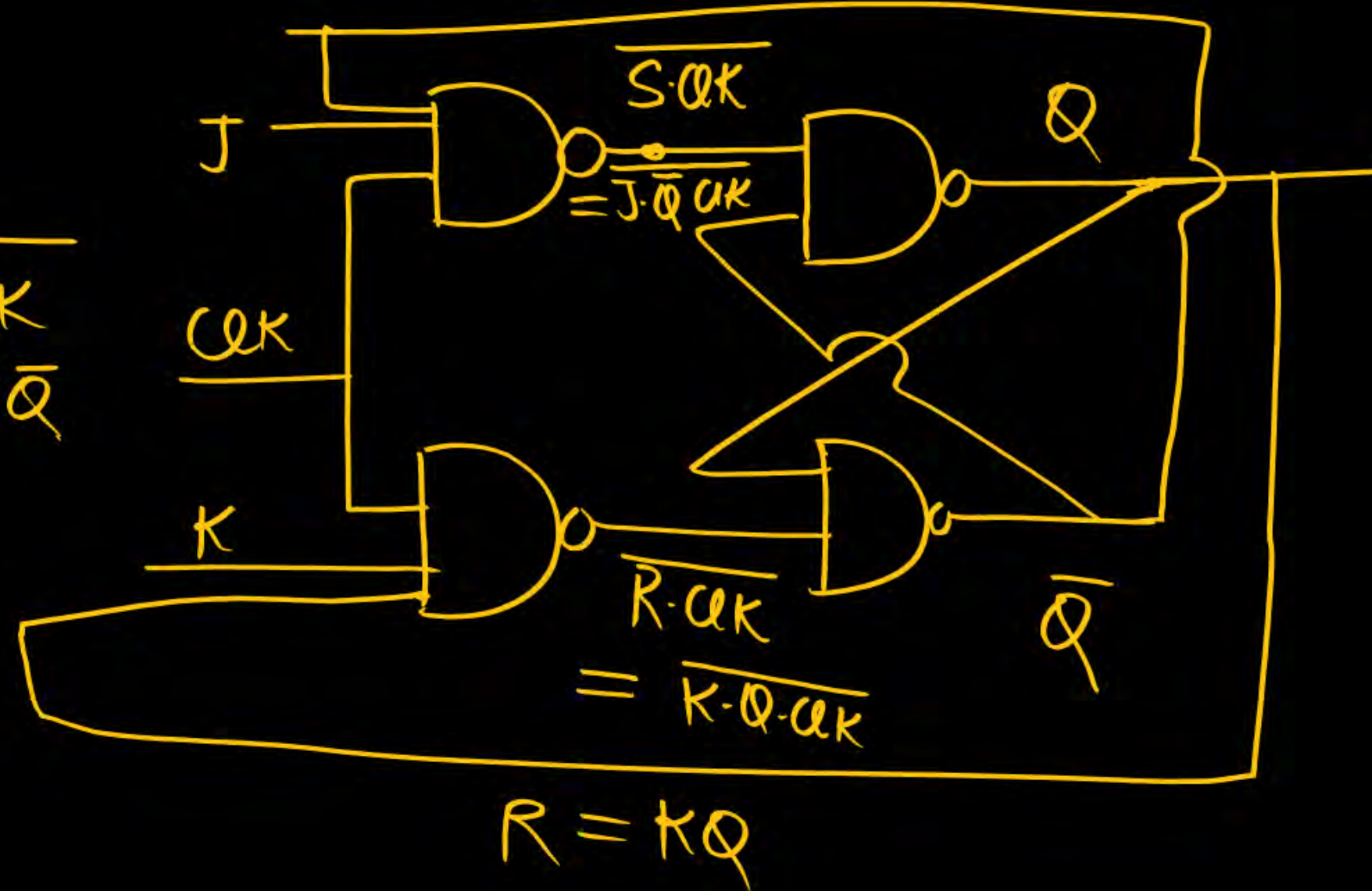
$$\frac{S \cdot CK}{(J \bar{Q}) \cdot CK} \\ S = J \bar{Q}$$



**A**  $S = J \bar{Q}, R = \bar{K} Q$


**B**  $S = J \bar{Q}, R = K Q$

**C**  $S = J Q, R = \bar{K} Q$

**D**  $S = J Q, R = K Q$



In J-K FF, J and K inputs are given as:

 

Then which of the following is true?

$$\begin{aligned}
 Q(n+1) &= J\bar{Q} + \bar{K}Q = A\bar{Q} + \overline{AB}Q \\
 &= A\bar{Q} + ABQ \\
 &= A[\bar{Q} + (B \cdot Q)] \\
 &= A[(\bar{Q} + B) \cdot (\bar{Q} + Q)] \\
 &= A[\bar{Q} + B] \\
 Q(n+1) &= A\bar{Q} + AB
 \end{aligned}$$

☒ **A**  $Q(n+1) = A\bar{Q} + AB$

☐ **B**  $Q(n+1) = A\bar{Q} + \bar{B}Q$

☐ **C**  $Q(n+1) = A \oplus B \oplus Q$

☐ **D**  $Q(n+1) = A \oplus B$



Which of the following is true?

- ☒ **A**  $Q(n+1) = S + \bar{R}Q$  is valid for all S and R values  $\rightarrow S \cdot R = 0$
- ☒ **B**  $Q(n+1) = J\bar{Q} + \bar{K}Q$  is valid when  $J \cdot K = 1$
- ☒ **C**  $Q(n+1) = S + \bar{R}Q$  is valid when  $S \cdot R = 1$
- ☒ **D**  $Q(n+1) = S + \bar{R}Q$  is valid when  $S \cdot R = 0$

A counter sequence is given as:

2 – 3 – 1 – 0 – 4 – 7, then MOD no. of the counter is

MOD no. = Total no. of different states

MOD no. = 6

☐ A 7

☒ B 6

☐ C 5

☐ D 4



A counter sequence is given as:

3 - 2 - 1 - 4 - 6 - 3 - - - - -

If its starting state is  $(100)_2$  then after application of 1049 clock pulses, counter will be at 1<sub>10</sub>.


$$3 - 2 - 1 - 4 - 6 \Rightarrow \text{MOD } n = 5$$

$$\text{Starting state} = (100)_2 = (4)_{10}$$

$$(4)_{10} \xrightarrow{5 \text{ CLK}} (4)_{10} \xrightarrow{5 \text{ CLK}} (4)_{10}$$

$$(4)_{10} \xrightarrow[209 \times 5]{1045} (4)_{10} \xrightarrow{1046} 6 \xrightarrow{1047} 3 \xrightarrow{1048} 2 \xrightarrow{1049} 1$$

A sequential circuit is as given below:

 

Value of  $f_{\text{out}}$  will be 2.75 MHz.


Counter sequence:

1-2-9-11  $\Rightarrow$  MOD no = 4

$$f_{\text{out}} = \frac{11 \text{ MHz}}{4} = 2.75 \text{ MHz}$$




Which of the following is not true?

 

- A** In asynchronous counter different FFs are driven by different clock *True*
- B** In asynchronous counter at output of each FF input frequency is divided by 2 *→ True*
- C** The sequence 0 – 1 – 3 – 2 require 2 FFs to design it with asynchronous counter *→ not true*
- D** Fixed up sequence and fixed down sequence is possible to design with asynchronous counter *→ True*

2 FFs  $\rightarrow$  Total state =  $2^2 = 4$

 A sequential circuit is as given below:  
The above circuit is



- ☒ A MOD-4 up counter
- ☐ B MOD-4 down counter
- ☐ C MOD-4 neither up nor down counter
- ☐ D MOD-2 counter

$$\bar{Q}_0 \rightarrow (1 \rightarrow 0)$$
$$Q_0 \rightarrow (0 \rightarrow 1)$$




$Q_0 \rightarrow$  toggles at every clk

$Q_1 \rightarrow$  toggle when  $\overline{Q_0}$   $(1-0) \rightarrow Q_0 \rightarrow (0-1)$

	$Q_1$	$Q_0$
	0	0
clk-1	1	1
clk-2	1	0
clk-3	0	1
clk-4	0	0

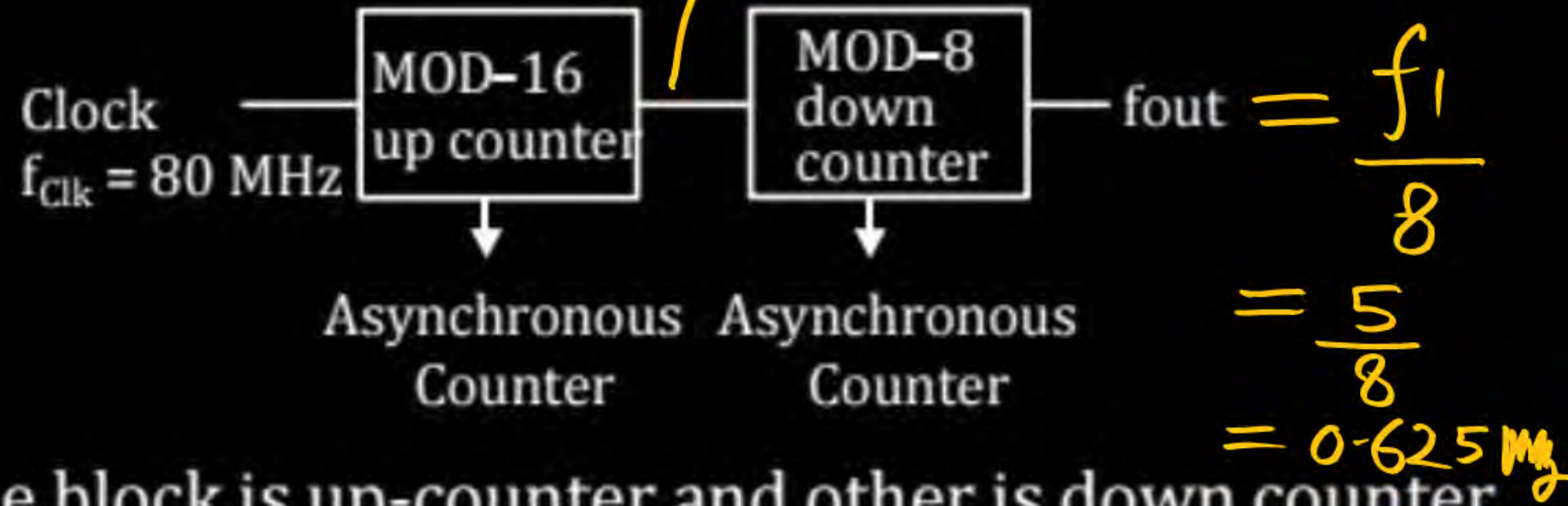**Question****MCQ**

A sequential circuit as given below:  
Value of  $f_{out}$  will be



- ☐ **A** Can not be calculated as one block is up-counter and other is down counter
- ☐ **B** 5 MHz
- ☒ **C** 0.625 MHz
- ☐ **D** 3.33 MHz



MOD-12 counter can be designed

$$M = \underline{\underline{N_1 \cdot N_2}}$$

- ☐ **A** Cascading two MOD-6 counter  $\times [36]$
- ☐ **B** Cascading MOD-4 counter and MOD-8 counter  $\times [32]$
- ☒ **C** Cascading MOD-4 & MOD-3 counter 12
- ☐ **D** Cascading MOD-3 & MOD-9 counter  $[27] \times$

# Question

NAT



A sequential circuit is as given below:

Initially counter is at  $Q_0Q_1Q_2 = (100)_2$  then after 2 clock pulses, o/p will be  $(7)_{10}$ .

$2^3 = 8 \rightarrow \text{MOD-8 down counter}$   
0 — 7


$Q_0 \rightarrow \text{LSB}$

$Q_2 \rightarrow \text{MSB}$

MSB      LSB

$Q_2 \ Q_1 \ Q_0$

0 0 1

 

$\overline{Q_1} \rightarrow (1-0)$

$\downarrow$   
 $Q_1 \rightarrow (0-1)$

1st 0 0 0

2nd 1 1 1

3rd 1 1 0

$\rightarrow Q_0Q_1Q_2 = 100$   
 $= (4)_{10}$

100

011

010

X




A sequential circuit is as given below:

Total 20 FFs are connected as shown above:

If input clock frequency is 128 MHz then, at output of 16<sup>th</sup> FF frequency of the waveform will be:

 $2^{20} = \text{MOD no}$   
 $\rightarrow \text{down counter}$



**A** 8 MHz  $= 128 \text{ MHz}$

**B** 12.8 MHz

**C** 1.95 KHz

**D** 4 MHz

$$f_{16} = \frac{128 \text{ MHz}}{2^{16}} = \frac{2^7 \text{ MHz}}{2^{16}} = \frac{1 \text{ MHz}}{2^9} = \frac{1000 \text{ KHz}}{512} = \frac{1000 \text{ KHz}}{2^9}$$

Sequential circuit A is designed with 5 FFs and sequential circuit -B is designed with 6-FFs, then maximum MOD no. possible combinedly using sequential circuit-A & sequential circuit-B is 2048.

$$\text{Circuit-A} \rightarrow 5 \text{ FF} \rightarrow \text{Max}^m \text{ MOD no. } M_1 = 2^5 = 32$$

$$\text{Circuit-B} \rightarrow 6 \text{ FF} \rightarrow \text{Max}^m \text{ MOD no. } M_2 = 2^6 = 64$$

$$\begin{aligned} \text{Max}^m \text{ MOD no combinedly } M &= M_1 \cdot M_2 \text{ [Cascading]} \\ &= 2^5 \times 2^6 \\ &= 2^{11} = 2048 \\ &= 2 \cdot 2^{10} \end{aligned}$$



To design a MOD-224 counter, minimum no. of FFs required is 8.

$$n \text{ FFs} \rightarrow 2^n \rightarrow \text{State}$$


$$7 \text{ FFs} \rightarrow 2^7 \rightarrow \text{States} = (128)$$

$$n \geq \log_{10} \text{MOD no.}$$
$$n \geq \log_2 224 \Rightarrow n \geq 7.80 \rightarrow n \geq \underline{\underline{8}}$$
$$8 \text{ FFs} \rightarrow 2^8 \rightarrow \text{State}$$
$$\parallel$$
$$256 \text{ States}$$

A sequential circuit is as given below:

Both the ffs are at reset state initially, then MOD-no. of the counter:

 - ☐ A MOD-4 counter
- ☐ B MOD-3 counter
- ☒ C MOD-2 counter
- ☐ D None of these





	$Q_1$	$Q_0$
	0	0
clk-1	1	1
clk-2	1	0
clk-3	1	1
clk-4	1	0
clk-5	1	1
clk-6	1	0
clk-7	1	1




0-2-3-0-2-3  
-0-2-3

2-3-2-3-2-3

A sequential circuit is as given below:

down counter  
→ MOD- $2^3$

$Q_2 Q_1 Q_0$

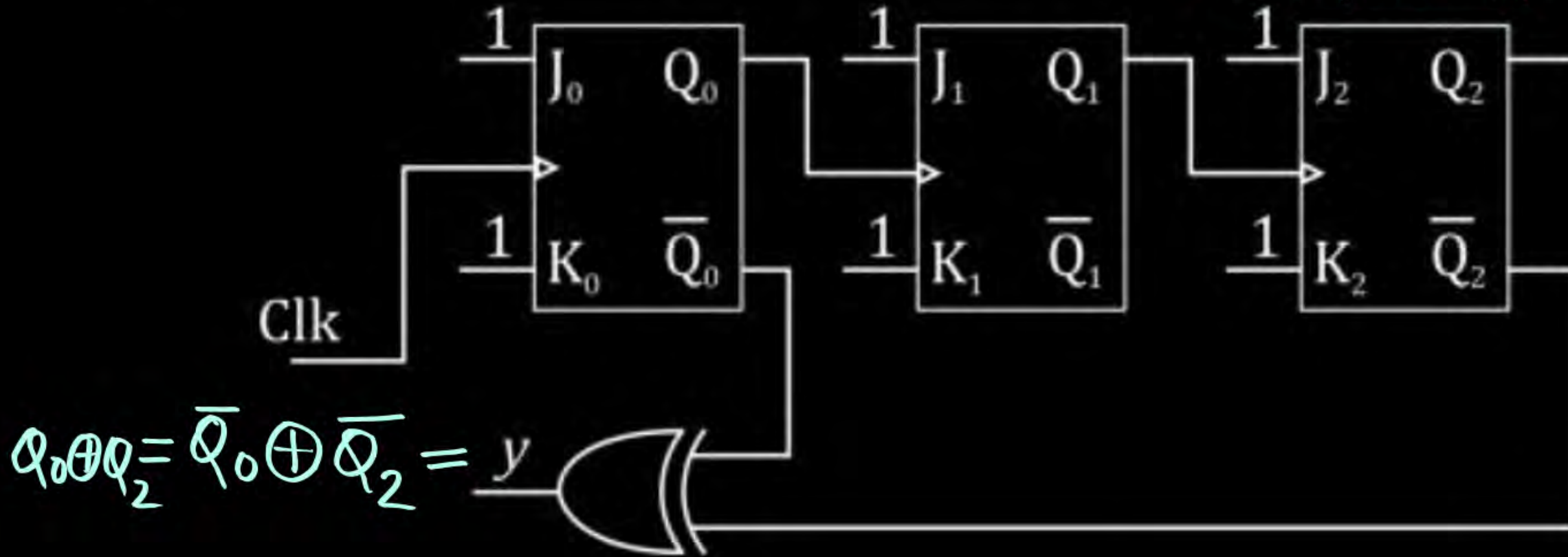


We have applied 32 clock pulses then number of times output  $y$  toggles is 24



	$Q_2$	$Q_1$	$Q_0$	$y$
	0	0	0	0
clk-1	1	1	1	0
clk-2	1	1	0	1
clk-3	1	0	1	0
clk-4	1	0	0	1
clk-5	0	1	1	1
clk-6	0	1	0	0
clk-7	0	0	1	1
clk-8	0	0	0	0

→  $6+6+6+6=24$

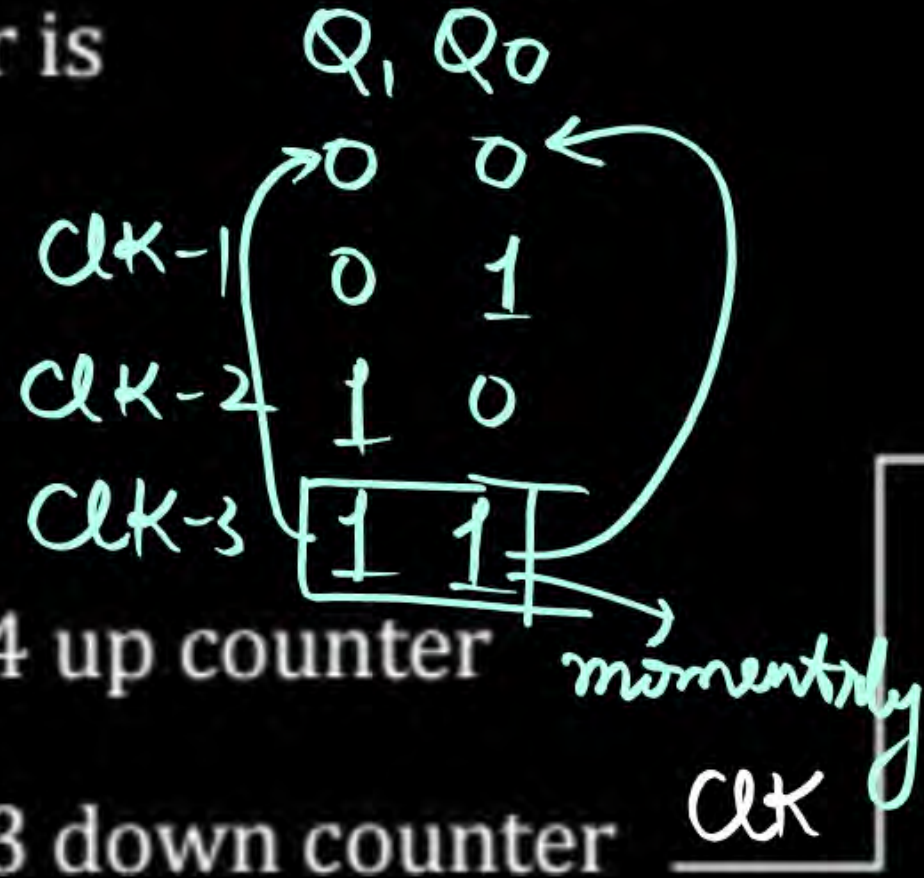A sequential circuit is as given below:  
The counter is




- ☐ A Mod-4 up counter
- ☐ B Mod-3 down counter
- ☒ C Mod-3 up counter
- ☐ D Mod-4 down counter

up-counter

Handwritten notes on the right:

 $\overline{Q_0} = 0 \rightarrow Q_0 = 1$   
 $\overline{Q_1} = 0 \rightarrow Q_1 = 1$   
 pin activated





Asynchronous counter designed using 4-FFs has Mod number  $M$ . By adding FFs in cascade, we changed the MOD number to  $6M$ , then the minimum number of additional FFs used is 3.

Asynchronous Counter  $\rightarrow$  4 FF  $\rightarrow$  Mod no =  $M$



$$\underline{n \geq 3}$$


using this we have to design MOD-6 counter and for this  $n \geq 3$
 
# Question

NAT



A sequential circuit is designed as shown:



The value of  $F_{out}$  41.67 kHz



upcounter

A sequential circuit is as given below:

If above sequential circuit has to work as MOD-3 counter then logic circuit will be:

	$Q_1$	$Q_0$
CLK-1	0	0
CLK-2	0	1
CLK-3	1	0
CLK-4	1	1


When  $Q_1=1$  &  $Q_0=1 \rightarrow$  CLR pin must activate

**A** ☒ Two input OR gate

**B** ☒ Two input AND gate

**C** ☒ Two input NAND gate

**D** ☒ Two input NOR gate

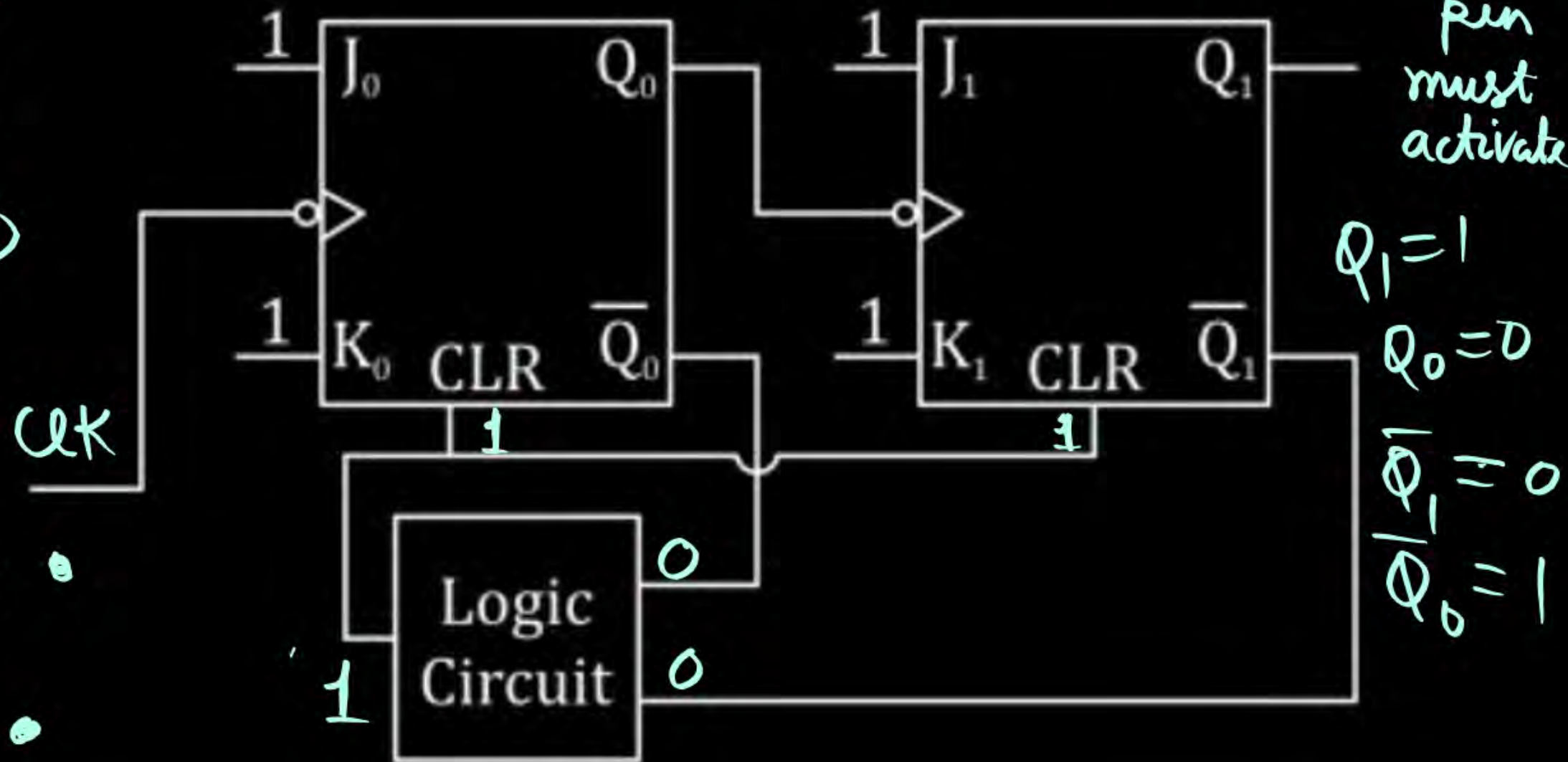



Which of the following is true:

- A** Asynchronous counters are faster compare to synchronous counters. ✗
- B** For same MOD-number, synchronous counters require fewer FFs compared to asynchronous counter ✗
- C** Sequence 0-1-2-3-0 can be designed only in asynchronous counter. ✗
- D** ✓ Sequence 0-1-3-2-0 can be designed only in synchronous counter.



**Question****MCQ**
 $M^N$  — Counter

We have two sequential circuits:

Circuit-A  $\rightarrow$  MOD number M.

Circuit-B  $\rightarrow$  MOD number N.

To design a counter of MOD no.  $M^N$ , we can

$$\underbrace{N \cdot N \cdot N \cdots N}_{M \text{ times}} = N^M$$




**A** Cascade Circuit-A and Circuit-B ~~X~~

**B** ✓ Cascade N Blocks of circuit-A

**C** Cascade M blocks of circuit-B ~~X~~

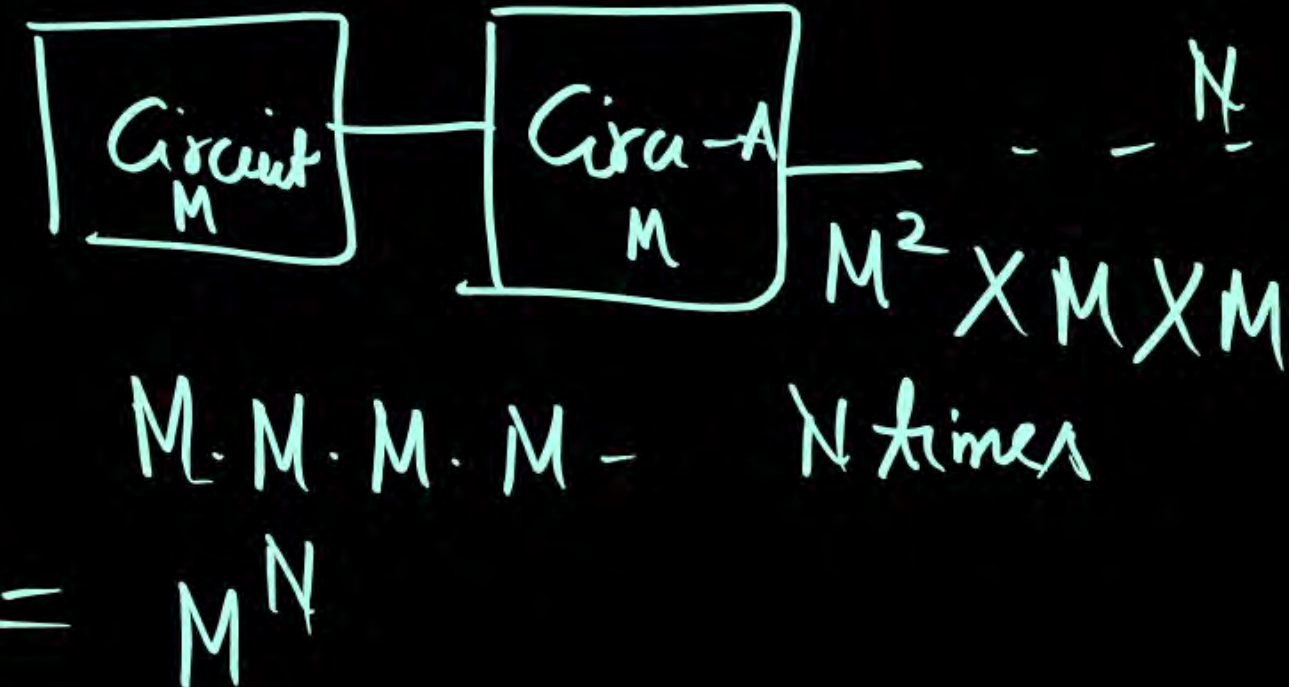**D** ~~X~~ Cascade circuit A with M blocks of circuit-B.




Lets consider the circuit given below:

Counter is at  $Q = 0$  initially, then after applying clock pulses the sequence

generated at  $\bar{Q}$  will be

- A** ✓ 1010101010.....
- B** ✗ 1100110011005..
- C** ✗ 0110001010011...
- D** ✗ 01011011101....


$Q = 0$	$\bar{Q} = 1$
$= 1$	$0$
$= 0$	$1$
$= 1$	$0$
$= 0$	$1$
$= 1$	$0$
$= 0$	$1$

 

$$\begin{aligned}
 Q(n+1) &= J\bar{Q} + \bar{K}Q \\
 &= \bar{Q} \cdot \bar{Q} + \bar{Q} \cdot Q \\
 &= \bar{Q} + 0 \\
 Q(n+1) &= \bar{Q}
 \end{aligned}$$



 MOD-10 & MOD-20 counters are cascaded to design MOD-200 counter, then minimum number of ffs required is 9.




An asynchronous counter is designed using 10 FFs having MOD No. 1000. Delay of each FF used is 8-n sec, then for which clock frequencies, counter will work properly.

Worst case delay =  $10 \times 8 = 80 \text{ nsec}$   
for proper operation

$$T_{clk} \geq 80 \text{ nsec}$$

$$\frac{1}{T_{clk}} \leq \frac{1}{80 \text{ nsec}}$$
 
$$f_{clk} \leq \frac{10^9}{80} \text{ Hz}$$



$$f_{clk} \leq \frac{10^3}{80} \text{ MHz}$$

$$f_{clk} \leq 12.5 \text{ MHz}$$

☒ **A** 12.5 MHz.

☒ **B** 1.25 MHz.

☐ **C** 125 MHz. X

☐ **D** 25 MHz. X







We have MOD-8 asynchronous counter, counting in up-sequence. Delay of each FF is  $t_d$ . Initially it is at  $(011)_2$  and 1-clock is applied then decoding errors that will appear  $\rightarrow$

MOD-8 (0-7)

0 1 1

1 0 0

  - ☒ **A**  $(010)_2$  &  $(000)_2$
- ☐ **B**  $(000)_2$  &  $(101)_2$
- ☐ **C**  $(101)_2$  &  $(010)_2$
- ☐ **D**  $(010)_2$  &  $(110)_2$



$t=0 \rightarrow QK-1$

$t=0$   
 $Q_2, Q_1, Q_0$   
 $0 \ 1 \ 1$   
 $t=td$   
 $0 \ 1 \ 0$   
 $t=2td$   
 $0 \ 0 \ 0$   
 $t=3td$   
 $1 \ 0 \ 0$



Starting state  $(111)_{10} \xrightarrow{1280K} (111)_{10} \xrightarrow{1280K} (111)_{10} \xrightarrow{1110K} (0)_{10}$

MOD-128 downcounter  $\rightarrow 0 - 127$


$370 - 256 = (114)$

$(125)_{10} \xleftarrow{3} 126 \xleftarrow{2} 127$

$127 - 126 - 125 - \dots - 0 - 127 - 126 -$

A sequential circuit is as given below:

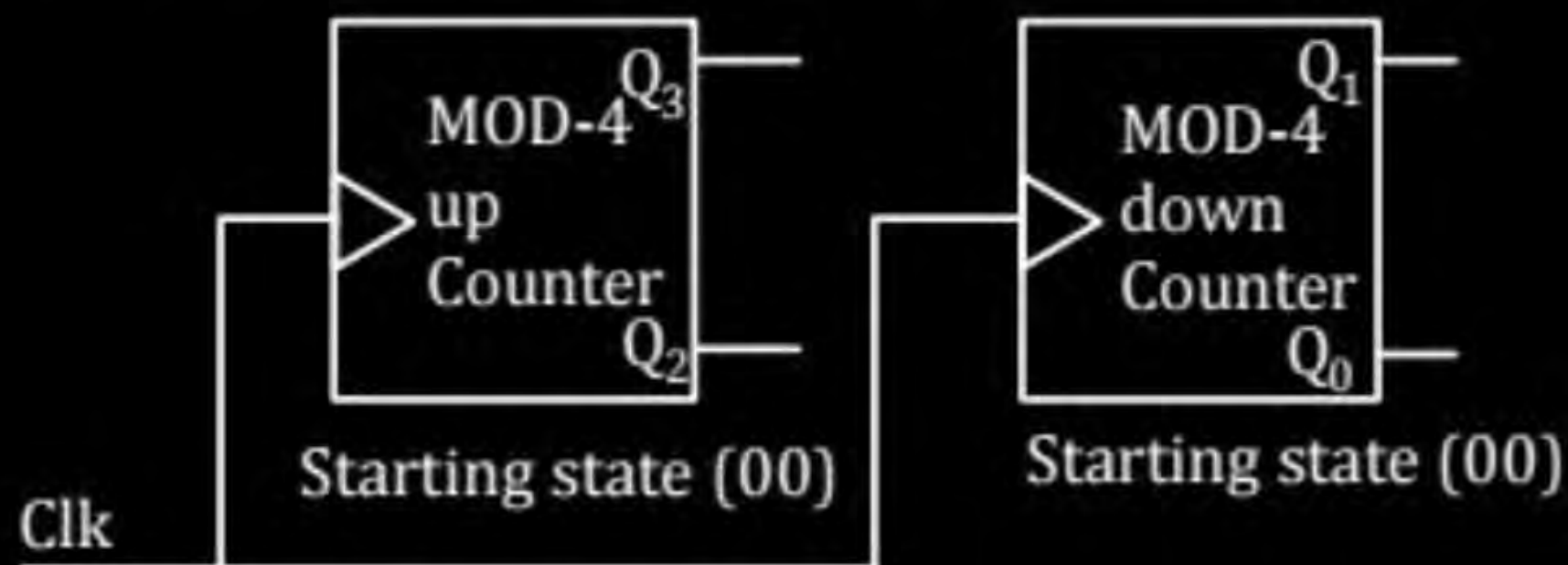After applying clock pulses, which count sequence will not appear at output  $Q_3Q_2Q_1Q_0$  is



- A**  $(0)_{10}$
- B**  $(7)_{10}$
- C**  $(10)_{10}$
- D**  $(11)_{10}$






0-3-2-1-0-

	$Q_3$	$Q_2$	$Q_1$	$Q_0$	
	0	0	0	0	$\longrightarrow (0)_{10}$
CLK-1	0	1	1	1	$\longrightarrow (7)_{10}$
CLK-2	1	0	1	0	$\longrightarrow (10)_{10}$
CLK-3	1	1	0	1	$\longrightarrow (13)_{10}$
CLK-4	0	0	0	0	

Asynchronous up counter

We have sequential circuit as given below: -

The above circuit is

 

**A** MOD-3 counter

**B** MOD-2 counter

**C** MOD-4 counter

**D** None of these


$\bar{Q}_0 = 0, \bar{Q}_1 = 0 \rightarrow$  CLR of  $Q_1$  will be activated.  
 $Q_0 = 1, Q_1 = 1 \rightarrow$  CLR pin of  $Q_1$  will be activated.



	$Q_1$	$Q_0$
	0	0
CLK-1	0	1
CLK-2	1	0
CLK-3	1	1

momentarily

CLR of  $Q_1$  activated

 

MOD-2 Counter → 1-2-1-2-1-2

MOD-32 up counter has starting state  $(00110)_2$  and MOD-16 down counter has starting state  $(0110)_2$ . After application of 75 clock pulses up counter is in state M and down counter is in state N then value of  $M + N$  is  $\underline{(28)}_{10}$ .

0-31 ← MOD-32 - up counter → starting state  $(00110)_2 = (6)_{10}$   
 MOD-16 → down counter → starting state →  $(0110)_2 = (6)_{10}$   
 ↳ 0-15 ⇒ 15-14-13-12 ... 0 ⇒ 15

up  $(6)_{10} \xrightarrow{32\text{clk}} (6)_{10} \xrightarrow{32\text{clk}} (6)_{10} \xrightarrow{11\text{clk}} (17)_{10} = M$

down  $(6)_{10} \xrightarrow{16\text{clk}} (6)_{10} \xrightarrow{16\text{clk}} (6)_{10} \xrightarrow{16} (6)_{10} \xrightarrow{16\text{clk}} (6)_{10} \xrightarrow{6\text{clk}} (0)_{10} \xrightarrow{1\text{clk}} (15)_{10}$   
 $N = (11)_{10} \xleftarrow{4\text{clk}}$



Which of the following is true about decoding error in asynchronous counter?


- ☐ A It is removed by using additional signalling ✗
- ☒ B It can be avoided using strobe signal ✓
- ☒ C Decoding error is present in asynchronous as well as in synchronous counter ✗
- ☐ D None of these

# Question

NAT



A sequential circuit is as given below:

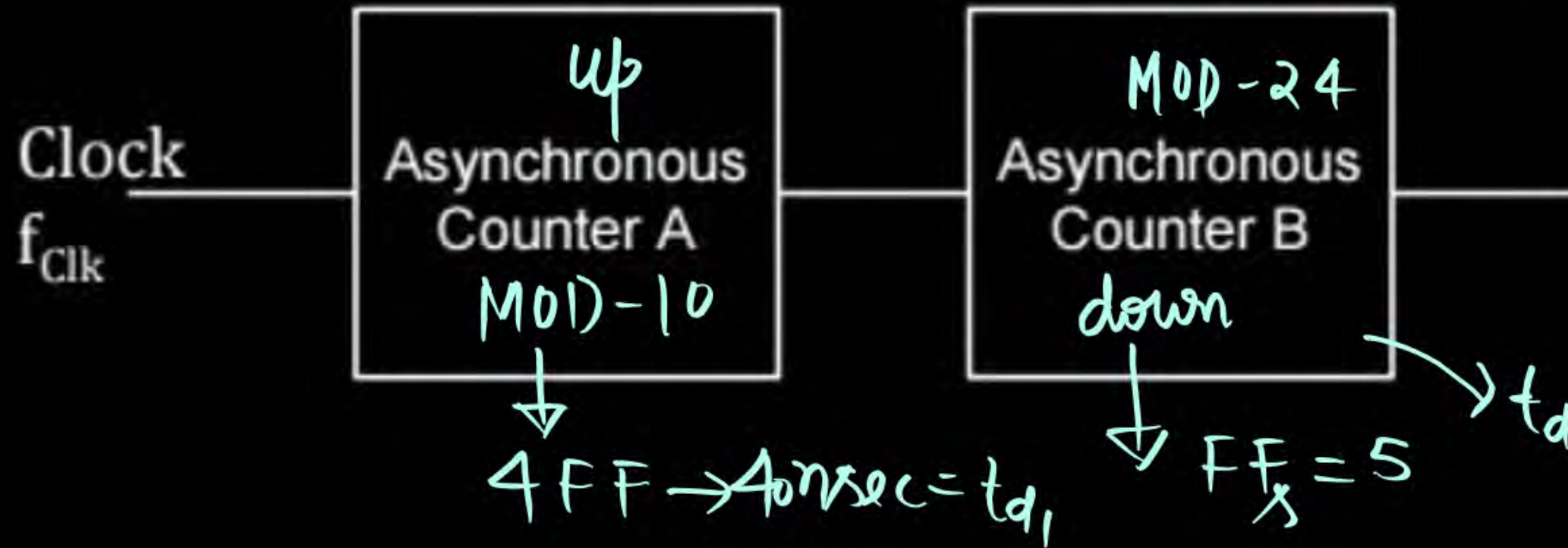

$$T_d = t_{d1} + t_{d2} = 90nsec$$

$$T_{clk} \geq T_d \quad f_{clk} \leq \frac{1}{T_d}$$

$$f_{clk} \leq \frac{1}{90nsec}$$

$$f_{clk} \leq \frac{10^9}{90} Hz$$


$$f_{clk} \leq \frac{100MHz}{9}$$

Counter A is MOD-10 up counter and counter B is MOD-24 down counter. FF used in designing has equal delay of  $t_d = 10nsec$ . Then maximum clock frequency value of  $f_{clk}$  that can be used to have proper operation of the circuit is 11.11 MHz.




A sequential circuit is as given below:

 If input clock frequency is 5 MHz, the frequency of output waveform at output  $Q_0$  is 2.5 MHz.




Which of the following circuit represents toggle mode of operation.

A

 


B

 


$$\begin{aligned}
 Q_0(n+1) &= J_0 \cdot \bar{Q}_0 + \bar{K}_0 Q_0 \\
 &= Q_0 \cdot \bar{Q}_0 + Q_0 \cdot Q_0 \\
 &= 0 + Q_0 = Q_0
 \end{aligned}$$

C

 

$$\begin{aligned}
 Q_0(n+1) &= \bar{Q}_0 \cdot \bar{Q}_0 + \bar{Q}_0 \cdot Q_0 \\
 &= \bar{Q}_0
 \end{aligned}$$

D

 

$$\begin{aligned}
 Q_0(n+1) &= \bar{Q}_0 \cdot \bar{Q}_0 + 1 \cdot Q_0 \\
 &= \bar{Q}_0 + Q_0 = 1
 \end{aligned}$$



**Question****MSQ** $(A, C, D)$ 

T-FF

$$\rightarrow Q(n+1) = T \oplus Q(n)$$

for this  $A \odot B = T$ 


A FF is given as:

Characteristic equation of above FF is

$$Q(n+1) = A \odot B \oplus Q(n)$$

To convert this FF into T-FF,

A &amp; B will be:

 
☒ **A**  $A = T, B = 1$ 

$$A \odot B = T \odot 1 = \overline{T}$$

☒ **B**  $A = \overline{T}, B = 1$ 

$$\overline{T} \odot 1 = T \oplus 1 = \overline{T}$$

☒ **C**  $A = \overline{T}, B = 0$ 

$$\overline{T} \odot 0 = T \oplus 0 = T$$

☒ **D**  $A = 0, B = \overline{T}$ 

$$0 \odot \overline{T} = T$$

To convert J-K FF into D-FF, J-K input will be

**A**  $J = \bar{D}, K = D$

**B**  $J = K = D$

**C**  $J = D, K = \bar{D}$



**D**  $J = K = \bar{D}$

$$\begin{aligned} JK \text{ to } D &\rightarrow J = D, K = \bar{D} \\ JK \text{ to } T &\rightarrow J = T, K = T \end{aligned}$$


$$\begin{aligned} Q(n+1) &= J\bar{Q} + \bar{K}Q = D\bar{Q} + DQ = D[\bar{Q} + Q] \\ &= D \cdot 1 = D \end{aligned}$$



 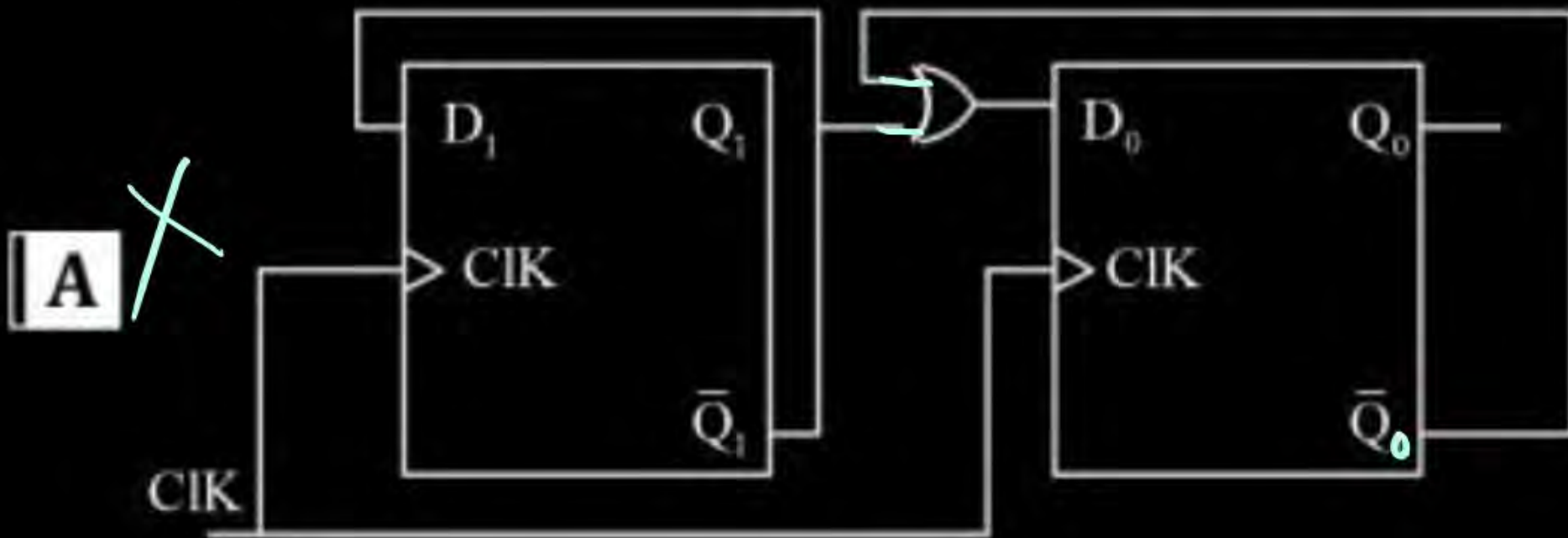To design a counter with counting sequence 0 – 3 – 1 – 2 – 0 the circuit will be



$Q_1$	$Q_0$	$Q_0(n+1)$
0	0	$= D_0$
1	1	$= \overline{Q_0} + \overline{Q_1}$
0	1	$= \overline{Q_0 \cdot Q_1}$
1	0	$Q_0(n+1)$
0	0	$= Q_0 \oplus \overline{Q_1}$
		$= Q_0 \odot Q_1$

 

**C**

**D**

None of these




**Question****MCQ**

A circuit is as given below:

The circuit can work as
 
$$\begin{aligned} \text{if } B=0 &\rightarrow y(n+1) = y(n) \\ \text{if } B=1 &\rightarrow y(n+1) = A \oplus y(n) \end{aligned}$$



- ☒ **A** Positive level triggered T-FF.
- ☐ **B** Negative level triggered T-FF.
- ☐ **C** Level triggered D-FF.
- ☐ **D** Edge triggered T-FF

# Question

MCQ



A circuit is as given below:

$$Q_0(n+1) = T_0 \oplus Q_0 =$$


$$= Q_1 \oplus Q_0$$

$$Q_1(n+1) = D_1 = \overline{Q_1 \cdot Q_0}$$

$$\begin{array}{cc} Q_0 & Q_1 \\ 0 & 0 \\ \text{clk-1} & 0 & 1 \end{array}$$

Initially FFs are at rest  $\underline{Q_0 Q_1} = (00)_2$ , then sequence that will be generated after application of clock pulses:
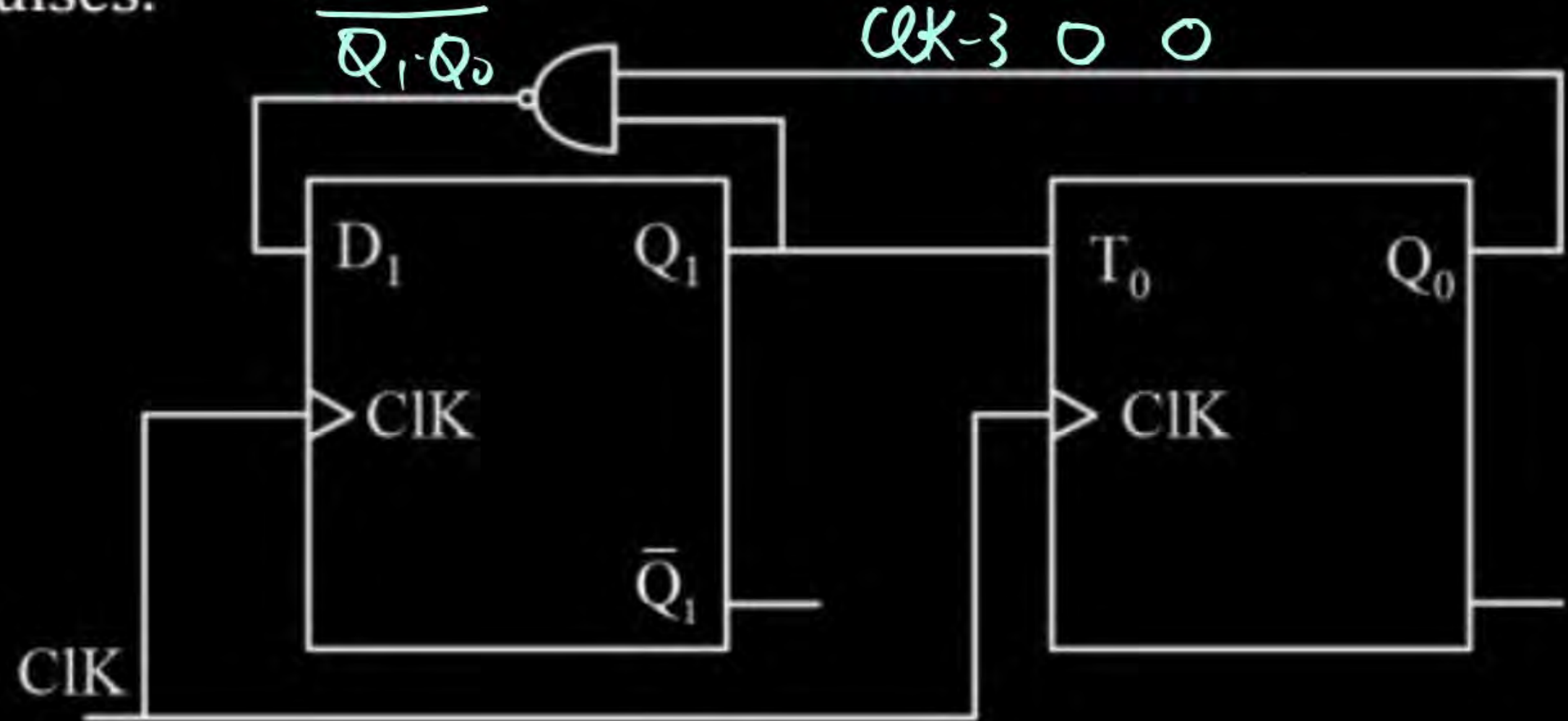
$$\begin{array}{cc} \text{clk-2} & 1 & 1 \\ \text{clk-3} & 0 & 0 \end{array}$$



- A** 00 - 10 - 11 - 00 ~~X~~
- B** 00 - 01 - 10 - 11 - 00
- C** 00 - 01 - 11 - 00 ✓
- D** 00 - 01 - 11 - 10 - 00 ~~X~~




$Q_2=0$  &  $Q_0=1 \rightarrow CLR$  pin activated

A sequential circuit is as given below:

Above counter will be:

	$Q_2$	$Q_1$	$Q_0$
	0	0	0
clk-1	1	1	1
clk-2	1	1	0
clk-3	1	0	1
clk-4	1	0	0
clk-5	0	1	1

↓ momentarily

 

☐ A MOD-4 Counter

☒ B MOD-5 Counter

☐ C MOD-2 Counter

☐ D MOD-6 Counter

A synchronous counter is designed using D-FFs that generate sequence 0 - 3 - 1 - 2 - 0. FFs used have delay of  $t_d = 45$  nsec and logic gates used has zero delay, then maximum clock frequency that can be used to have proper operation of the circuit is 22.22 MHz.

0 - 3 - 1 - 2 - 0  
01



$$f_{clk} \leq \frac{10^3}{45} \text{ MHz}$$

$$f_{max} = \frac{10^3}{45} \text{ MHz}$$

$$C_{lk} = \frac{200}{9} \text{ MHz} = 22.22 \text{ MHz}$$

$$T_{clk} \geq 45 \text{ nsec}$$



$$f_{clk} \leq \frac{1}{45 \text{ nsec}}$$



# Question

MCQ

$$Q_1(n+1) = J_1 \bar{Q}_1 + \bar{K}_1 Q_1$$



A sequential circuit is as given below:

$$= \bar{Q}_0 \cdot \bar{Q}_1 + Q_0 Q_1 = Q_1 \odot Q_0$$

Initially counter is at  $\underline{Q_1 Q_0} = (11)_2$  then after applying clock next state will


$$Q_0(n+1) = J_0 \bar{Q}_0 + \bar{K}_0 Q_0 = \bar{Q}_1 \bar{Q}_0 + 0 = \overline{Q_1 + Q_0}$$

be

$Q_1, Q_0$   
1 1

clk-1 1 0

 - ☐ A  $(01)_2$
- ☒ B  $(10)_2$
- ☐ C  $(00)_2$
- ☐ D None of these



We have a T-FF, to convert it into D-FF, input T must be

$$T \Rightarrow Q(n+1) = T \oplus Q(n)$$

$$\text{DFF} \rightarrow Q(n+1) = D$$

$$T = D \oplus Q(n) \Rightarrow Q(n+1) = \underline{D \oplus Q(n)} \oplus Q(n)$$
$$Q(n+1) = D \oplus 0 = D$$

- ☐ A  $D \odot Q$  ✗
- ☒ B  $D \oplus Q$
- ☐ C  $D$  ✗
- ☐ D  $\bar{D}$  ✗





We want to design a counter with counting sequence 0 - 1 - 2 - 3 - 0, using  
 Circuit-A  $\rightarrow$  Asynchronous counter  $\rightarrow FF_s = 2 \rightarrow T_d = 50 \text{ nsec}$   
 Circuit-B  $\rightarrow$  Synchronous counter  $\rightarrow FF_s = 2$   $(T_{clk})_A \geq (50 \text{ nsec})$   
 FFs used in circuit-A and circuit-B are of same logic family and logic gates used has 0 delay while FFs have delay of 25 nsec. Then which of the following is true?

$$(T_d)_B = 25 \text{ nsec}$$

$$(T_{clk})_B \geq 25 \text{ nsec}$$

$$(f_{clk})_A \leq 1/50 \text{ nsec}$$

$$(f_{clk})_{A \text{ max}} = 1/50 \text{ nsec}$$

- ☒ **A** Maximum clock frequency is same in both the circuits
- ☒ **B** Maximum clock frequency is double in circuit-B compare to circuit-A.
- ☒ **C** Maximum clock frequency is half in circuit-B compare to circuit-A
- ☐ **D** None of these

$$(f_{clk})_B \leq 1/25 \text{ nsec} \quad (f_{clk})_{B \text{ max}} = 1/25 \text{ nsec} = 2 \cdot 1/50 \text{ nsec}$$



A counter has to be designed to generate a sequence

$0 - 2 - 2^2 - 2^3 - 2^4 - 2^5 - 2^6$ , to design the counter appropriate number of FFs needed is 7.

$$0 - 2 - 4 - 8 - 16 - 32 - \textcircled{64} \quad \text{MOD no} = 7$$

$$2^6 = 64$$

$$6 \rightarrow \text{FF} \rightarrow \text{MOD no} = 64$$

$$2^6 \quad 2^5 \quad 2^4 \quad 2^3 \quad 2^2 \quad 2^1 \quad 2^0$$

$$| \quad 0 \quad 0 \quad 0 \quad 0 \quad 0 \quad 0 = \textcircled{63}$$

$$| \quad 0 \quad 0 \quad 0 \quad 0 \quad 0 \quad 0 = (64)_{10}$$

$$2^7 = \underline{\underline{128}}$$



Thank you

**GW**  
*Soldiers !*

