

COMPUTER SCIENCE & IT

DIGITAL LOGIC



Lecture No: 06

Miscellaneous Topics



By- Chandan Gupta Sir

Recap of Previous Lecture



- Question Practice
-
-



Topics to be Covered

State transition Diagram





[State Transition Diagram]




→ What is state transition diagram ?

- A diagram that represents all the possible transitions of a sequential CKT.

0-1-3-2 → Counter

  

00 — 01 — 10 — 11


 


$$Q_1(n+1) = \overline{Q_1(n)}$$

$$Q_0(n+1) = \overline{Q_0(n)}$$



- Lets understand it with an example :

 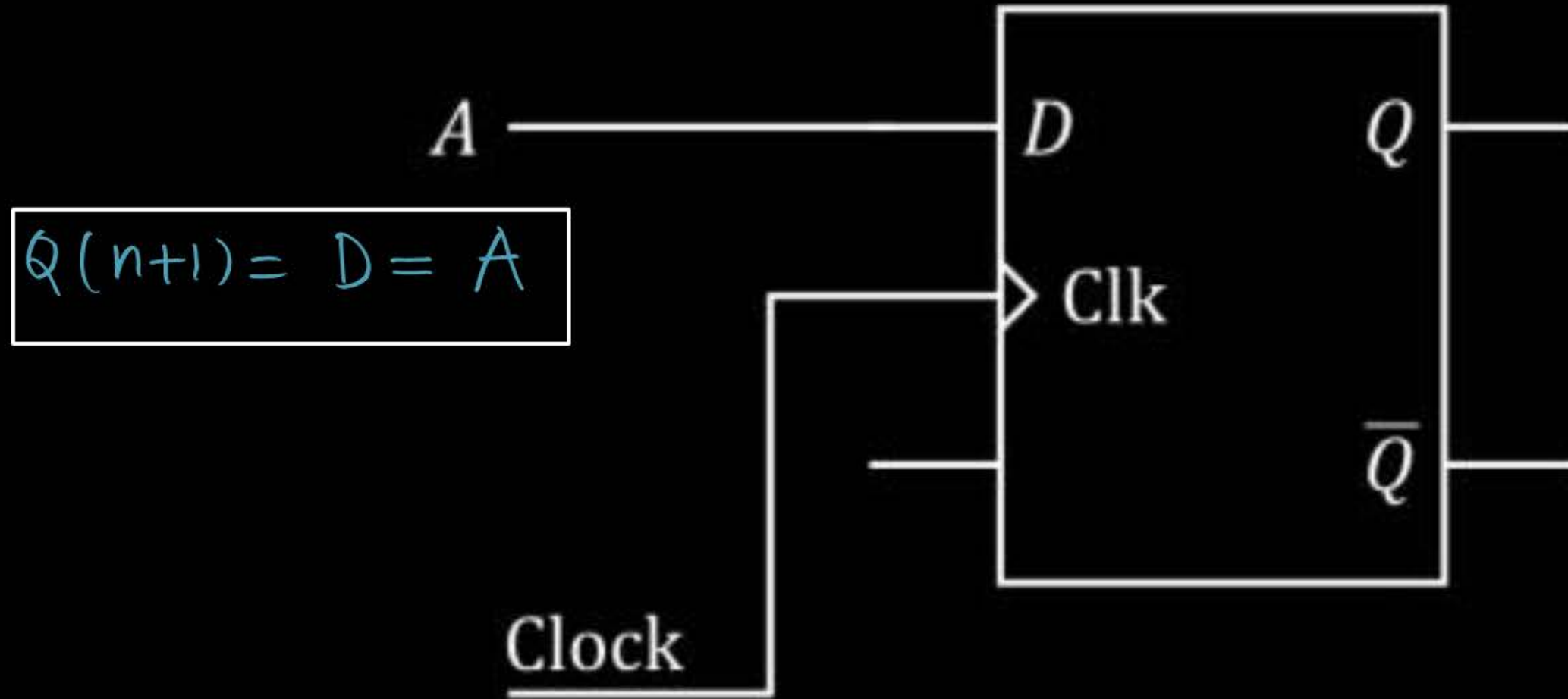

State transition diagram for above circuit will be :



	\bar{Q}	Q
\bar{A}		
A	1	1

$$Q(n+1) = A$$

$$Q(n+1) = \{2, 3\}$$

A	$Q(n)$	$Q(n+1)$
0	0	0
0	1	0
1	0	1
1	1	1

 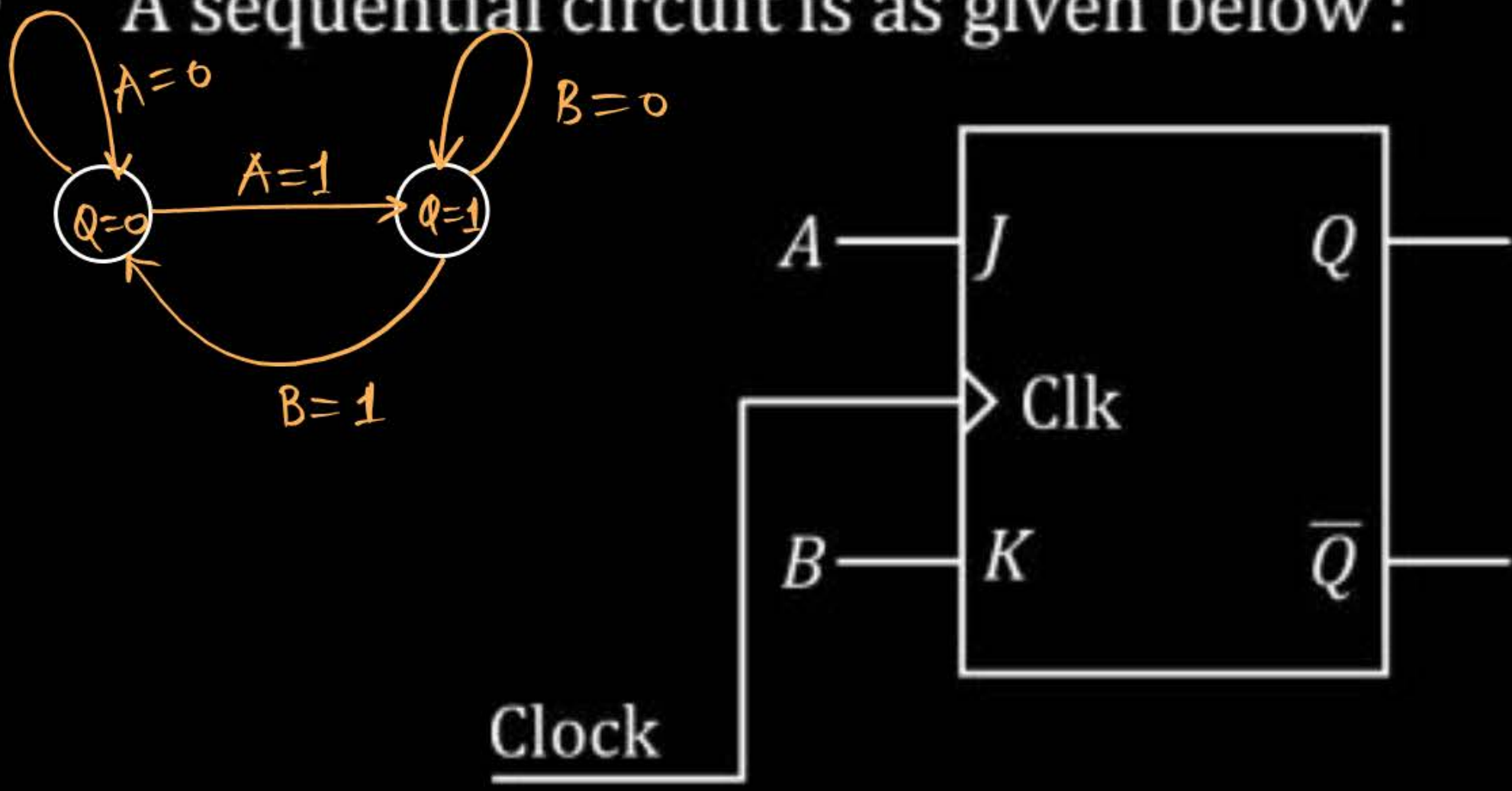- A sequential circuit is as given below :



State transition diagram of above circuit will be :

A	B	Q(n)	Q(n+1)
0	0	0	0
0	0	1	1
0	1	0	0
0	1	1	0
1	0	0	1
1	0	1	1
1	1	0	1
1	1	1	0

$$Q(n+1) = \Sigma(1, 4, 5, 6)$$

	$\bar{B}\bar{Q}$	$\bar{B}Q$	BQ	$B\bar{Q}$
\bar{A}		1		
A	1	1		1

$$Q(n+1) = A\bar{Q} + \bar{B}Q$$

$$\bar{J} = A$$

$$K = B$$



[Question]

A sequential circuit is as given below :

$$Q(n+1) = J\bar{Q}(n) + \bar{K}Q(n)$$

$$= A\bar{Q}(n)\bar{Q}(n) + \bar{A}Q(n)$$





$$Q(n+1) = A \oplus Q(n)$$

  

State transition diagram of above sequential circuit is


$$Q(n)=1, \quad A=0 \rightarrow Q(n+1)=1$$

$$A=1 \rightarrow Q(n+1)=0$$

    

[Question]


A sequential circuit is as given below :

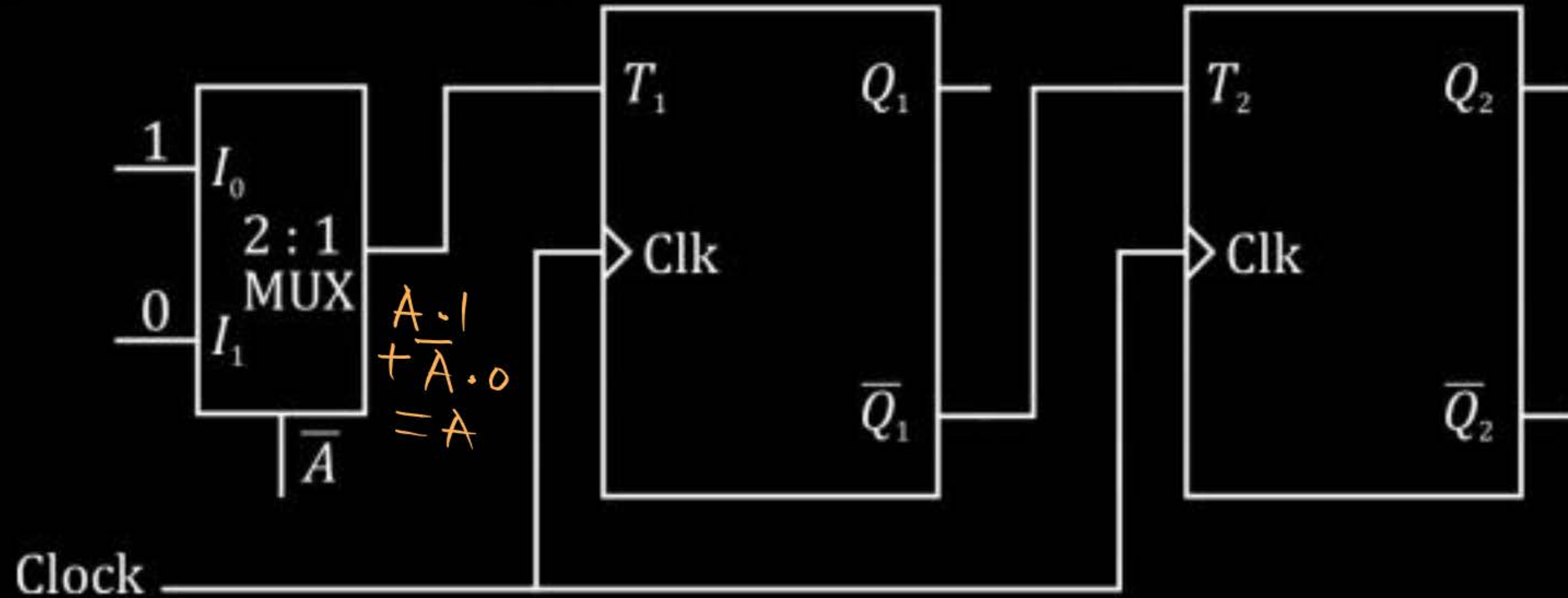

State transition diagram of above circuit will be :

$$Q_1(n+1) = T_1 \oplus Q_1(n) = A \oplus Q_1(n)$$
 
$$Q_2(n+1) = T_2 \oplus Q_2(n) = \bar{Q}_1(n) \oplus Q_2(n) = Q_1(n) \odot Q_2(n)$$







Initial conditions and next state calculations:

- $Q_1(n)=0, Q_2(n)=0$:
 - $A=0 \rightarrow Q_1(n+1)=0, Q_2(n+1)=1$
 - $A=1 \rightarrow Q_1(n+1)=1, Q_2(n+1)=1$


Initial conditions and next state calculations:

    - $Q_1(n)=0, Q_2(n)=1$:
 - $A=0 \rightarrow Q_1(n+1)=0, Q_2(n+1)=0$
 - $A=1, Q_1(n+1)=1, Q_2(n+1)=0$




[Question]

A sequential circuit is as given below :




 


$Q(n+1) = D$
 $= \underline{A \odot Q(n)}$
 $Q(n) = 0,$
 $A = 0 \rightarrow Q(n+1) = 1$
 $A = 1, Q(n+1) = 0$
Clock

 $Q(n) = 1, A = 0, Q(n+1) = 0$
 $A = 1, Q(n+1) = 1$





    State transition diagram of above circuit will be :



  [Question]

The digital logic shown in the figure satisfies the given state diagram when Q_1 is connected to input A of the XOR gate :



$$Q_1(n+1) = D_1 = Q_2(n)$$

$$Q_2(n+1) = D_2 = Q_1(n) \oplus S = A \oplus S$$

$$Q_2(n+1) = A \oplus S$$

$$A = \bar{Q}_1(n) \Rightarrow Q_2(n+1) = Q_1(n) \oplus S$$

$$S \Rightarrow \bar{S} \rightarrow Q_2(n+1) = Q_1(n) \oplus S$$

Suppose XOR gate is replaced by XNOR gate then which of the option preserves the state diagram :

- (a) Input A is connected to \bar{Q}_2 ✗
- (b) Input A is connected to Q_2 ✗
- (c) Input A is connected to \bar{Q}_1 and S is complimented. ✗
- (d) Input A is connected to \bar{Q}_1 ✓

Parity generator :


A	B	C	P_e	P_o
0	0	0	0	1
0	0	1	1	0
0	1	0	1	0
0	1	1	0	1
1	0	0	1	0
1	0	1	0	1
1	1	0	0	1
1	1	1	1	0

$$P_e(A, B, C) = A \oplus B \oplus C$$

$$P_o(A, B, C) = \overline{A \oplus B \oplus C} \\ = A \oplus B \odot C$$


$$P_e(A, B, C, D) = A \oplus B \oplus C \oplus D$$
 
$$P_o(A, B, C, D) = \overline{A \oplus B \oplus C \oplus D}$$




Parity Checker:

 even Parity checker $\rightarrow E_{\text{even}} = A \oplus B \oplus C \oplus D \dots \oplus P_e \Rightarrow 1 \rightarrow \text{error}$



odd parity checker
 
$$E_{\text{odd}} \Rightarrow \overline{A \oplus B \oplus C \oplus D \dots \oplus P_o}$$





Topic : 2 Min Summary

- State transition diagram
- Parity generator/Checker

Thank you

GW
Soldiers !

