

PRACTICE SHEET-1

Computer Science & Information Technology

Digital Logic


Combinational Circuit

Q1 Which of the following is true?

- (A) All gates follow commutative as well as associative law.
- (B) NOR & XNOR do not follow associative law
- (C) NAND & XOR do not follow associative law
- (D) All gates follow commutative law, but some gates do not follow associative law.

Q2 We have to implement half adder as well as half subtractor. The minimum number of 2-i/P NAND gate required is _____.


Q3 A digital circuit is as given below:

 

This circuit implements:

- (A) $A + B$
- (B) $A - B$
- (C) $B - A$
- (D) None of these

Q4 A logical circuit is as given below:

 

Function of logic circuit - 1 & logic circuit - 2 is same. The output y'_1 will be


- (A) $A \oplus B$
- (B) $A \bar{B}$

(C) $\bar{A}B$

(D) $A - B$


Q5 We have two numbers A and B and both are 4-bit numbers. To perform complete addition of these two numbers, total number of H.A.s + OR gate required is _____.

 Q6 Which of the following circuits can be used as universal circuit:



- (A) circuit - 1 and circuit - 2 both
- (B) circuit - 1 only
- (C) circuit - 2 only
- (D) Neither circuit - 1 nor circuit - 2

Q7 A logical circuit is implemented as:

 

Output y is

- (A) '1' when majority of the i/Ps A, B, C are at '1'
- (B) '0' when minority of the i/Ps A, B, C are at '1'
- (C) '1' when minority of the i/Ps A, B, C are at '1'
- (D) '0' when majority of the i/Ps A, B, C are at '1'

Q8 x, y, z are i/Ps of a full adder then, sum output of full adder will be '1' if

- (A) $\bar{x} \bar{y} + \bar{y} \bar{z} + \bar{z} \bar{x} = 1$



- (B) $xyz = 1$
 (C) $(x + y)(y + z)(z + x) = 0$
 (D) None of these


Q9 Which of the following is/are true?

- (A) NOR gate is equivalent to NAND gate with bubbled i/ P_s
 (B) OR gate is equivalent to NAND gate with bubbled i/ P_s
 (C) AND gate is equivalent to NOR gate with bubbled i/ P_s
 (D) NAND gate is equivalent to NOR gate with bubbled i/ P_s


Q10 We have to implement H.A circuit & full adder circuit together. I/P lines for H.A. is x, y and i/P lines for full adder is x, y, z then minimum number of 2 – i/P NAND gate required is _____.

Q11 We have a 4-bit adder in which each full adder has sum delay of $t_s = 4$ nsec and carry delay of 2 nsec. In one minute number of additions completed by this full adder is _____ $\times 10^9$.




Q12 A logical circuit is as given below:

 

 Which of the following circuit is/are equivalent to the above circuit:



(B)

   

Q13 A K-map is as given below:

| | $\bar{y}\bar{z}$ | $\bar{y}z$ | $y\bar{z}$ | yz |
|-----------|------------------|------------|------------|------|
| \bar{x} | 1 | 1 | | 1 |
| x | | 1 | 1 | |

In minimized solution of above K-map, there are terms $x\bar{y}$, xz and one term is missing. The missing term is

- (A) $\bar{y}\bar{z}$
 (B) xz
 (C) $\bar{x}z$
 (D) $\bar{x}\bar{z}$

Q14 A K-Map is as given below:

| | $\bar{y}\bar{z}$ | $\bar{y}z$ | $y\bar{z}$ | yz |
|-----------|------------------|------------|------------|------|
| \bar{x} | 1 | 1 | | X |
| x | X | | 1 | 1 |

Its minimized solution will be

- (A) $x \odot y$



- (B) $x \oplus y$
 (C) $\bar{z} + \bar{x}\bar{y}$
 (D) $\bar{z} + xy + \bar{x}\bar{y}$

Q15 $F(x, y, z) = \overline{x\bar{y}} + \bar{x}y + x\bar{y}z + x\bar{y}\bar{z}$
 Then the minimized solution of $f(x, y, z)$ will be

- (A) $x + \bar{y}$ (B) $\bar{x}y$
 (C) $xy\bar{z}$ (D) $x + \bar{y} + z$

Q16 In a 4-bit parallel adder, sum delay and carry delay of each full adder is $t_s = 1$ nsec and $t_c = 5$ nsec respectively. No. of additions performed per sec by adder is N_1 . If delays are interchanged then no. of additions performed per sec is N_2 , then N_2/N_1 _____.

Q17 A K-map is as given below:

Then minimized solution of K-map is:

| | $\bar{C}\bar{D}$ | $\bar{C}D$ | CD | $C\bar{D}$ |
|------------------|------------------|------------|------|------------|
| $\bar{A}\bar{B}$ | 1 | 1 | 1 | |
| $\bar{A}B$ | 1 | 1 | 1 | X |
| AB | | | 1 | |
| $A\bar{B}$ | | X | X | |


- (A) $\bar{A}\bar{C} + \bar{A}D + CD$
 (B) $\bar{A}\bar{C} + CD$
 (C) $\bar{A}B + CD + \bar{A}\bar{C}$
 (D) None of these

Q18 K-map of two logical functions $f_1(A, B)$ and $f_2(A, B)$ is as given below:

| f_1 | \bar{B} | B |
|-----------|-----------|-----|
| \bar{A} | 1 | |
| A | | 1 |

| f_1 | \bar{B} | B |
|-----------|-----------|-----|
| \bar{A} | 1 | 1 |
| A | | |

Then K-map of $f(A, B)$ will be

 

(A)

| f | \bar{B} | B |
|-----------|-----------|-----|
| \bar{A} | 1 | 1 |
| A | | 1 |

| (B) f | \bar{B} | B |
|-----------|-----------|-----|
| \bar{A} | | 1 |
| A | 1 | 1 |

| (C) f | \bar{B} | B |
|-----------|-----------|-----|
| \bar{A} | 1 | 1 |
| A | | |

| (D) f | \bar{B} | B |
|-----------|-----------|-----|
| \bar{A} | | 1 |
| A | 1 | |

Q19 $f(A, B, C, D)$ is as given below:

$$f(A, B, C, D) = \overline{BD} + AC + \overline{AB} + ABCD + \overline{ABC} + ABC$$

Then no. of entries in K-map of $f(A, B, C, D)$ that are filled with '1' are _____.

Q20 $f(x, y, z)$ is given as: $f(x, y, z) = \bar{x}\bar{y} + \bar{x}z + zy$, The equivalent $f(x, y, z)$ can also be

- (A) $(\bar{x} + y + \bar{z})(x + \bar{y} + \bar{z})(x + \bar{y} + z)$
 (B) $(x + \bar{y} + z)(\bar{x} + y + z)(\bar{x} + y + \bar{z})$
 (C) $(\bar{x} + \bar{y})(\bar{x} + z)(x + y)$
 (D) None of these

Q21 Which of the following is true?

- (A) K-map has more than one solution.
 (B) K-map always has unique solution.
 (C) K-map can have more than one solution.
 (D) None of these


Q22 A & B are two-bit numbers as

$$A = a_1a_0 \text{ and } B = b_1b_0$$

Then no. of combination in which $A > 2B$ are _____.




Q23 A digital circuit is as given below:

 

Input lines of the circuit are a_1 , b_1 , a_0 , b_0 and output line is y .

Then no. of combinations of input lines in which output y will be '1' are _____.


Q24 A MUX circuit is as given below:

 

Output y is

- (A) $\overline{A} + \overline{B}$
- (B) $\overline{A} + B$
- (C) $A \oplus B$
- (D) $A\overline{B}$


Q25 A MUX circuit is as given below:

 

$f(A, B, C, D)$ is:


- (A) $\Sigma (0, 1, 2, 3, 4, 5, 6, 14, 15)$
- (B) $\Sigma (0, 1, 2, 3, 4, 6, 13, 15)$
- (C) $\Sigma (0, 1, 2, 3, 4, 6, 14, 15)$
- (D) $\Sigma (1, 2, 3, 4, 5, 6, 7, 13, 14, 15)$

 Q26 A MUX circuit is as given below, output y is



- (A) \overline{A}
- (B) A
- (C) 0
- (D) 1


Q27 A 4:1 MUX is given as:

 

Output y is

- (A) \overline{B}
- (B) B
- (C) $A \oplus B$
- (D) $A \odot B$

 Q28 A combinational circuit is designed using MUX as shown below: -




output y is

- (A) $\overline{A} + \overline{B}$
- (B) $A \cdot B$
- (C) $A \oplus B$
- (D) $A \odot B$

 Q29 A MUX circuit is implemented as shown:






output y represents

- (A) Comparator output when $B < A$
- (B) Comparator output when $B = A$
- (C) Comparator output when $B > A$
- (D) Comparator output when $B < 2A$

Q30 In a full subtractor the corresponding input bits of two numbers are x & y [$x - y$] and input borrow is z and output borrow is B . Output borrow is implemented as shown.

The values of I_0, I_1, I_2 & I_3 are:

 

- (A) $I_0 = z, I_1 = 1, I_2 = 0, I_3 = z$
- (B) $I_0 = z, I_1 = 0, I_2 = 1, I_3 = \bar{z}$
- (C) $I_0 = 1, I_1 = z, I_2 = 0, I_3 = z$
- (D) $I_0 = \bar{z}, I_1 = 1, I_2 = 0, I_3 = z$

Q31 To implement $1024 : 1$, the required $4 : 1$ MUXs are _____.


Q32 Which of the following is true:

- (A) MUX is non-universal circuit.
- (B) MUX can be used to implement half adder as well as full adder.
- (C) 2:1 MUX has 1-input line, 1-output line and 2-select line
- (D) If in a MUX input lines are 24 then minimum 4-select lines are required for proper functioning.

Q33 Which of the following is true:

- (A) Decoder and MUX have same internal circuitry
- (B) MUX & De MUX have same internal circuitry
- (C) De MUX and decoder have same internal circuitry
- (D) None of these

 Q34 A combinational circuit using decoder and OR gate is as given below:
o/p y_1 & y_2 combinedly represents:



- (A) Half adder
- (B) Half subtractor with subtraction $(B-A)$
- (C) Half subtractor with subtraction $(A-B)$
- (D) Comparator o/p with $(A > B)$


Q35 To implement $1 : 512$ De MUX, we require $N, 1:8$ De MUX, then the value of N is _____.

Q36 To implement $1:128$ De MUX, we require

- (A) $127 - 1:4$ DeMUX
- (B) $127 - 1:2$ DeMUX
- (C) $18 - 1:8$ DeMUX & $1 - 1:2$ DeMUX
- (D) $40 - 1:8$ DeMUX & $1 - 1:2$ DeMUX




 - Q37** A combinational circuit is as given below. When input is $A = 0$ & $B = 1$, then LED no. that glows will be_____.



- Q38** For a decoder having 4 input lines, no. of output lines are
 (A) 1 (B) 2
 (C) 16 (D) 4

 
- Q39** A digital circuit is as given below:



Output y is

- (A) A (B) B
 (C) A.B (D) (A + B)
- Q40** Which of the following is 'not true'?
- (A) DeMUX is not a universal circuit
 (B) For 52 output lines, no. of select lines must be atleast 6 for DeMUX.
 (C) DeMUX is parallel to serial converter.
 (D) DeMUX is serial to parallel converter

- Q41** A circuit is as shown below:

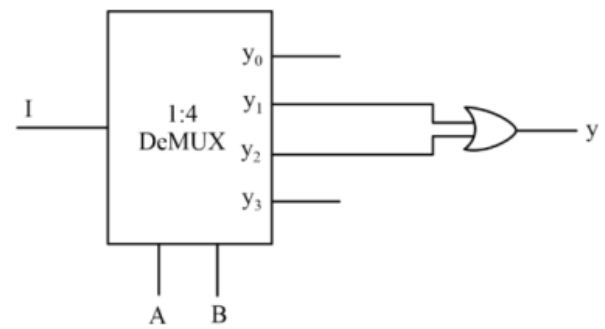

- (A) $A \oplus B$ if $I = 1$
 (B) $A \odot B$ if $I = 0$
 (C) $A \cdot B$ if $I = 1$
 (D) $A + B$ if $I = 0$

- Q42** For implementing full adder and full subtractor we require a decoder of the order $n : M$, where n is no. of input lines & M is no. of output lines, then value of M is _____.


- Q43** It is given that:

$$x_1 \odot x_2 \odot x_3 \odot x_4 = 0$$

Then which of the following is true?

- (A) $x_1 x_2 + x_3 x_4 = 1$
 (B) $x_1 \oplus x_2 + x_2 \oplus x_3 + x_3 \oplus x_4 = 1$
 (C) $x_1 x_2 x_3 x_4 = 0$
 (D) $\overline{x_1 x_2} + x_2 x_3 + \overline{x_3 x_4} = 1$

 - Q44** A digital circuit is as given below:




Output y is

- (A) $AB\overline{C}$
 (B) $A \oplus B \oplus C$
 (C) $A \odot B \oplus C$
 (D) $\overline{A + B + C}$

- Q45** A circuit is designed as shown:



 

Output P is 1 when majority of input lines are '0'.

Output is


- (A) $xy + yz + zx$
 (B) $\bar{x}\bar{y} + \bar{y}\bar{z} + \bar{z}\bar{x}$
 (C) $\overline{xy + yz}$
 (D) $\overline{xy + yz}$

Q46 Two logical functions:

$$f_1(A, B) = \Sigma(1, 2)$$

$$f_2(A, B) = \Sigma(0, 1, 3)$$

then output $f(A, B)$ will be

 

- (A) $\Sigma(1, 2)$
 (B) $\Sigma(0, 1, 3)$
 (C) $\Sigma(0, 1, 2, 3)$
 (D) $\Sigma(1)$


Q47 A K-Map is as given below:

| | | |
|-----------|-----------|-----|
| | \bar{B} | B |
| \bar{A} | X | 1 |
| A | \bar{C} | |

Its simplified solution will be

- (A) $(\bar{A} + \bar{B})\bar{C}$
 (B) $(\bar{A} + \bar{B})(\bar{A} + \bar{C})$
 (C) $\bar{A}\bar{B} + \bar{B}\bar{C}$
 (D) None of these

Q48 A 4 : 2 Encoder is as given below:

 

Output y_1 will be

- (A) $(P + Q)$ (B) $(Q + R)$
 (C) $(R + S)$ (D) $(P + S)$

Q49 Which of the following is not true?

- (A) $\bar{A} + \bar{B}C = (\bar{A} + \bar{B})(\bar{B} + C)$
 (B) $\bar{A} + \bar{B}C = \bar{A}\bar{B} \cdot (\bar{A} + C)$
 (C) $\bar{A}B + \bar{A}C + \bar{B}C = \bar{A}B + \bar{B}C$
 (D) $\bar{A}B + \bar{B}C + \bar{A}C = (\bar{A} + B)(B + C)(C + A)$

Q50 For n-variable, the number of self dual functions are found to be 256, then the value of n is_____.

Q51 To add two 5-bit numbers, we required m H.A.s and n-OR gates then minimum value of $(m + n)$ is _____.

Q52 Two stage SOP circuit can directly be implemented

- (A) Using NAND gates at first stage & AND gate at second stage.
 (B) Using NAND gates only at both first & second stage.
 (C) Using AND gates only at both first & second stage.
 (D) Using NOR gates only at both stages.



Answer Key

Q1 (D)
Q2 6
Q3 (C)
Q4 (B)
Q5 (10)
Q6 (B)
Q7 (A, B)
Q8 (D)
Q9 (B, C)
Q10 10
Q11 6
Q12 (A, C)
Q13 (B)
Q14 (A)
Q15 (A)
Q16 2.5
Q17 (B)
Q18 (B)
Q19 8
Q20 (B)
Q21 (C)
Q22 4
Q23 6
Q24 (A)
Q25 (C)
Q26 (D)

Q27 (A)
Q28 (B)
Q29 (C)
Q30 (A)
Q31 341
Q32 (B)
Q33 (C)
Q34 (C)
Q35 73
Q36 (B, C)
Q37 2
Q38 (C)
Q39 (C)
Q40 (C)
Q41 (A)
Q42 8
Q43 (C)
Q44 (A)
Q45 (B)
Q46 (B)
Q47 (B)
Q48 (C)
Q49 (A)
Q50 4
Q51 13
Q52 (B)



Hints & Solutions

Q1 Text Solution:

(d)

Q2 Text Solution:

6

Q3 Text Solution:

(c)

Q4 Text Solution:

(b)

Q5 Text Solution:

(10)

Q6 Text Solution:

(b)

Q7 Text Solution:

(a, b)

Q8 Text Solution:

(d)

Q9 Text Solution:

(b, c)

Q10 Text Solution:

10

Q11 Text Solution:

6

Q13 Text Solution:

(b)

Q14 Text Solution:

(a)

Q15 Text Solution:

(a)

Q16 Text Solution:

2.5

Q17 Text Solution:

(b)

Q18 Text Solution:

(b)

Q19 Text Solution:

8

Q20 Text Solution:

(b)

Q21 Text Solution:

(c)

Q22 Text Solution:

4

Q23 Text Solution:

6

Q24 Text Solution:

(a)

Q25 Text Solution:

(c)

Q26 Text Solution:

(d)

Q27 Text Solution:

(a)

Q28 Text Solution:

(b)

Q29 Text Solution:

(c)

Q30 Text Solution:

(a)

Q31 Text Solution:

341

Q32 Text Solution:

(b)

Q33 Text Solution:



(c)

Q34 Text Solution:

(c)

Q35 Text Solution:

73

Q36 Text Solution:

(b, c)

Q37 Text Solution:

2

Q38 Text Solution:

(c)

Q39 Text Solution:

(c)

Q40 Text Solution:

(c)

Q41 Text Solution:

(a)

Q42 Text Solution:

8

Q43 Text Solution:

(c)

Q44 Text Solution:

(a)

Q45 Text Solution:

(b)

Q46 Text Solution:

(a)

Q47 Text Solution:

(b)

Q48 Text Solution:

(c)

Q49 Text Solution:

(a)

Q50 Text Solution:

4

Q51 Text Solution:

13

Q52 Text Solution:

(b)



[Android App](#) | [iOS App](#) | [PW Website](#)