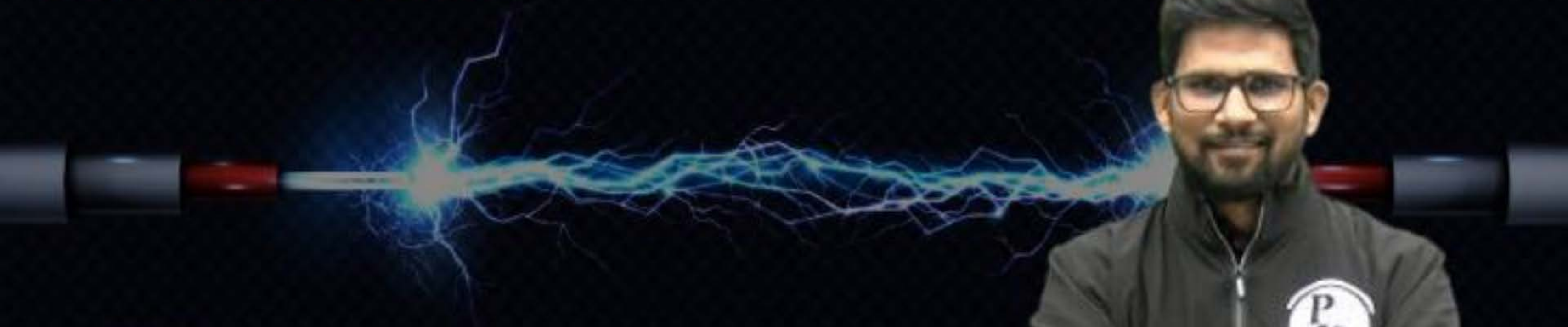


COMPUTER SCIENCE & IT

DIGITAL LOGIC




Lecture No. 05

**BOOLEAN THEOREMS AND
GATES**

By- Chandan Gupta Sir





Recap of Previous Lecture

Arithmetic gates



Topics to be Covered

XOR & XNOR gates

- Properties of XNOR gate :

- $A \odot A = \bar{A} \cdot \bar{A} + A \cdot A = \bar{A} + A = 1$

- $A \odot \bar{A} = \bar{A} \cdot \bar{\bar{A}} + A \cdot \bar{A} = 0$

- $A \odot A = 1 \Rightarrow A \odot 1 = A = \bar{A} \cdot \bar{1} + A \cdot 1 = A$, $\bar{A} \odot 1 = \bar{A}$

- $A \odot \bar{A} = 0 \Rightarrow A \odot 0 = \bar{A} \Rightarrow \bar{A} \cdot \bar{0} + A \cdot 0 = \bar{A}$
 $\bar{A} \odot 0 = A$

$$AB \odot 0 = \overline{AB}$$

- Exchange properties of XNOR gate :

- $A \odot B = C \rightarrow \text{Given} \Rightarrow B \odot A = C$

then $A \odot C = B \rightarrow \text{true}$

$$A \odot C = A \odot A \odot B = 1 \odot B = B$$

then also $B \odot C = A$


$$\Rightarrow B \odot C = B \odot A \odot B = B \odot B \odot A = 1 \odot A = A$$

- $A \odot A \odot A \odot A \dots n \text{ times}$ [n - represents no. of A]

then o/p = 1 for n -even

= A for n -odd

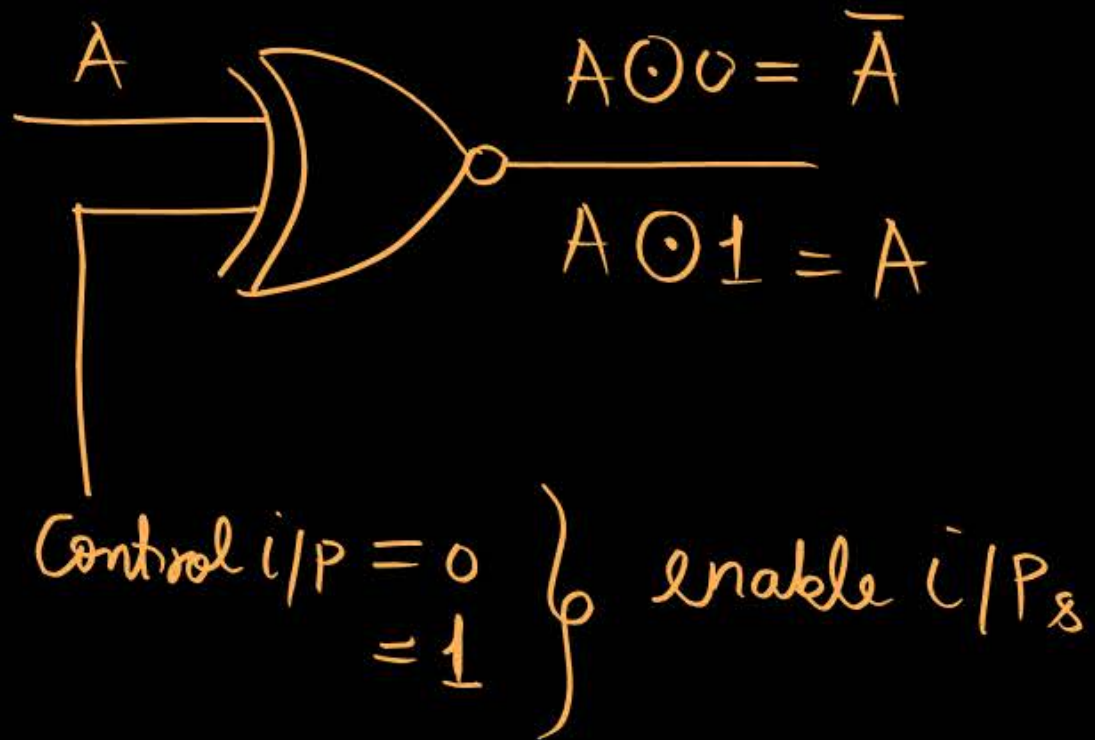- Buffer and inverting buffer using XNOR :



$$A \odot A = 1$$

$$\underbrace{A \odot A} \odot \underbrace{A \odot A} =$$

$$1 \odot 1 = 1$$

$$\underbrace{A \odot A} \odot A = 1 \odot A = A$$

[Combined IMP Properties of XOR and XNOR]

- $$\left. \begin{aligned} \bar{A} \oplus B &= \bar{\bar{A}} \cdot B + \bar{A} \cdot \bar{B} = A \odot B \\ A \oplus \bar{B} &= \bar{A} \cdot \bar{B} + A \cdot \bar{\bar{B}} = A \odot B \end{aligned} \right\} \rightarrow \boxed{\overline{A \oplus B} = \bar{A} \oplus B = A \oplus \bar{B} = A \odot B}$$

$$\bar{A} \oplus \bar{B} = \bar{\bar{A}} \cdot \bar{B} + \bar{A} \cdot \bar{\bar{B}} = A \cdot \bar{B} + \bar{A} \cdot B = A \oplus B$$

- $$\bar{A} \odot B = \bar{\bar{A}} \cdot \bar{B} + \bar{A} \cdot B = A \oplus B$$
- $$A \odot \bar{B} = \bar{A} \cdot \bar{\bar{B}} + A \cdot \bar{B} = A \oplus B$$
- $$\bar{A} \odot \bar{B} = \bar{\bar{A}} \cdot \bar{\bar{B}} + \bar{A} \cdot \bar{B} = A \odot B$$

$$\left. \begin{aligned} \bar{A} \odot B &= A \oplus B \\ A \odot \bar{B} &= A \oplus B \\ \bar{A} \odot \bar{B} &= A \odot B \end{aligned} \right\} \rightarrow \boxed{\overline{A \odot B} = \bar{A} \odot B = A \odot \bar{B} = A \oplus B}$$

$$\overline{A \oplus B} = A \odot B$$

$$\bar{A} \oplus \bar{B} = A \oplus B$$



- $A \oplus B \oplus C = \overline{A \odot B \odot C} \rightarrow \text{true or false} \rightarrow \text{false}$

	^{2²} A	^{2¹} B	^{2⁰} C	$y_1 = A \oplus B \oplus C$	$y_2 = A \odot B \odot C$
0	0	0	0	0	0
1	0	0	1	1	1
2	0	1	0	1	1
3	0	1	1	0	0
4	1	0	0	1	1
5	1	0	1	0	0
6	1	1	0	0	0
7	1	1	1	1	1

$$A \oplus B \oplus C = A \odot B \odot C$$

$$\begin{aligned} f(A, B, C) &= \sum(1, 2, 4, 7) \\ &= A \oplus B \oplus C \\ &= A \odot B \odot C \end{aligned}$$

$$\cdot 1 \oplus 0 \oplus 1 = 0$$

$$\cdot 1 \oplus 0 \oplus 1 \oplus 1 = 1$$

$$\cdot 1 \oplus 1 \oplus 0 \oplus 0 = 0$$

$$\cdot 1 \oplus 0 \oplus 0 \oplus 1 \oplus 1 = 1$$

$$\cdot 0 \oplus 0 \oplus 0 \oplus 0 = 0$$

$$\cdot 0 \oplus 1 = 1$$

$$\cdot 0 \oplus 0 \oplus 0 = 0$$

$$1 \oplus 0 \oplus 1 \oplus 1 \oplus 0 \oplus 1 \oplus 0 = 0$$

$$\cdot |0| = 1$$

$$\cdot |0|0| = 1, \quad |0|0|0 = 0$$

$$\cdot 0|0|0|0| = 0$$

$$\cdot |0|0|0|0 = 1$$

$$\cdot |0|0|0|0|0| = 0$$

$$\cdot |0|0|0|0|0 = 1$$

$$\cdot 0|0| = 1$$

$$\cdot 0|0|0|0 = 0$$

$$\cdot |0|0|0|0|0|0|0|0| = 1$$

$$\begin{aligned} \overline{A \oplus B} &= A \odot B = \overline{A \bar{B} + \bar{A} B} \\ &= \overline{A \bar{B}} \cdot \overline{\bar{A} B} \\ &= (\bar{A} + B) \cdot (A + \bar{B}) \end{aligned}$$

From above we conclude that :

- XOR gate search for → odd no. of 1's for any no. of inputs.
↳ i.e. when total no. of 1's are odd then o/p will be '1'
and if total no. of 1's are even or zero (not odd)
then o/p will be '0'.

- XNOR gate search for → for even no. of 1's or zero no. of 1's for even no. of i/p lines
→ for odd no. of 1's for odd no. of input lines.

and that's why for odd no. of input XOR & XNOR are same and for even no. of i/p lines they are complement of each other.

- $A \oplus B \oplus C = A \odot B \odot C$
 $A \oplus B \oplus C \oplus D = \overline{A \odot B \odot C \odot D}$
- $A \oplus B \oplus C \oplus D \oplus E = A \odot B \odot C \odot D \odot E$

$$1 \oplus 1 \oplus 0 \oplus 1 = 1$$

$$\overline{1 \odot 1 \odot 0 \odot 1} = 0$$

$$0 \odot 1 \odot 0 \odot 1 = 1$$

$$1 \odot 0 \odot 0 \odot 1 = 1$$

$$1 \odot 1 \odot 1 \odot 1 = 1$$

$$1 \odot 1 \odot 0 \odot 0 = 1$$

$$1 \oplus 0 \odot 1 = 1$$

$$\left. \begin{array}{l} \overline{1 \oplus 0 \odot 1} = 0 \\ 0 \oplus 0 \odot 1 = 0 \\ 1 \oplus 1 \odot 1 = 0 \\ 1 \oplus 0 \odot 0 = 0 \end{array} \right\}$$

$$\overline{1 \oplus 0 \odot 1} = 1 \odot 0 \odot 1 = 1 \oplus 0 \oplus 1 = 0$$

$$1 \oplus \overline{0} \odot 1 = 1 \oplus 0 \oplus 1 = 1 \odot 0 \odot 1 = 0$$

$$1 \oplus 0 \odot \overline{1} = 1 \oplus 0 \oplus 1 = 1 \odot 0 \odot 1 = 0$$

- Compliment property of XOR and XNOR GATE :

- $\overline{A \oplus B} = \bar{A} \oplus B = A \oplus \bar{B} = A \odot B$

$$\overline{A \odot B} = \bar{A} \oplus B = A \oplus \bar{B} = A \oplus B$$

- $$\overline{A \oplus B \oplus C} = \bar{A} \oplus B \oplus C = A \oplus \bar{B} \oplus C = A \oplus B \oplus \bar{C}$$

$$= A \odot B \oplus C = A \oplus B \odot C$$

$$\overline{\overline{A \oplus B \oplus C}} = \overline{A \odot B \oplus C} = \overline{A \oplus B \odot C} = A \oplus B \oplus C = A \odot B \odot C$$

- $\bar{A} \oplus \bar{B} = \bar{A} \odot B = A \oplus B$

$$A \oplus B \odot C \oplus D$$

$$= A \oplus B \oplus C \odot D$$

- $$\overline{A \oplus B \odot \bar{C} \odot \bar{D}} = \overline{A \odot B \odot C \odot D} = A \oplus \underline{B \odot C \odot D} = A \odot B \oplus C \odot D$$

$$= A \odot B \odot C \oplus D$$

$$= A \oplus B \oplus C \oplus D$$

$$= A \oplus \underline{B \odot C \odot D}$$

$$= A \oplus B \oplus C \oplus D$$

- $$\overline{A \odot \bar{B} \odot \bar{C} \odot \bar{D}} = \overline{A \odot B \odot C \odot D} = A \oplus B \odot C \odot D$$


$$= A \odot B \oplus C \odot D$$

- $$\overline{A \odot \bar{B} \odot \bar{C} \odot D \odot \bar{E}} = \overline{A \odot B \odot C \odot D \odot E} = \underline{A \oplus B \oplus C \oplus D \oplus E}$$

- $$\overline{A \oplus \bar{B} \odot \bar{C} \oplus D} = \overline{A \oplus B \odot C \oplus D} = A \oplus B \oplus C \oplus D$$

$$= A \odot B \odot C \oplus D$$

[Question]

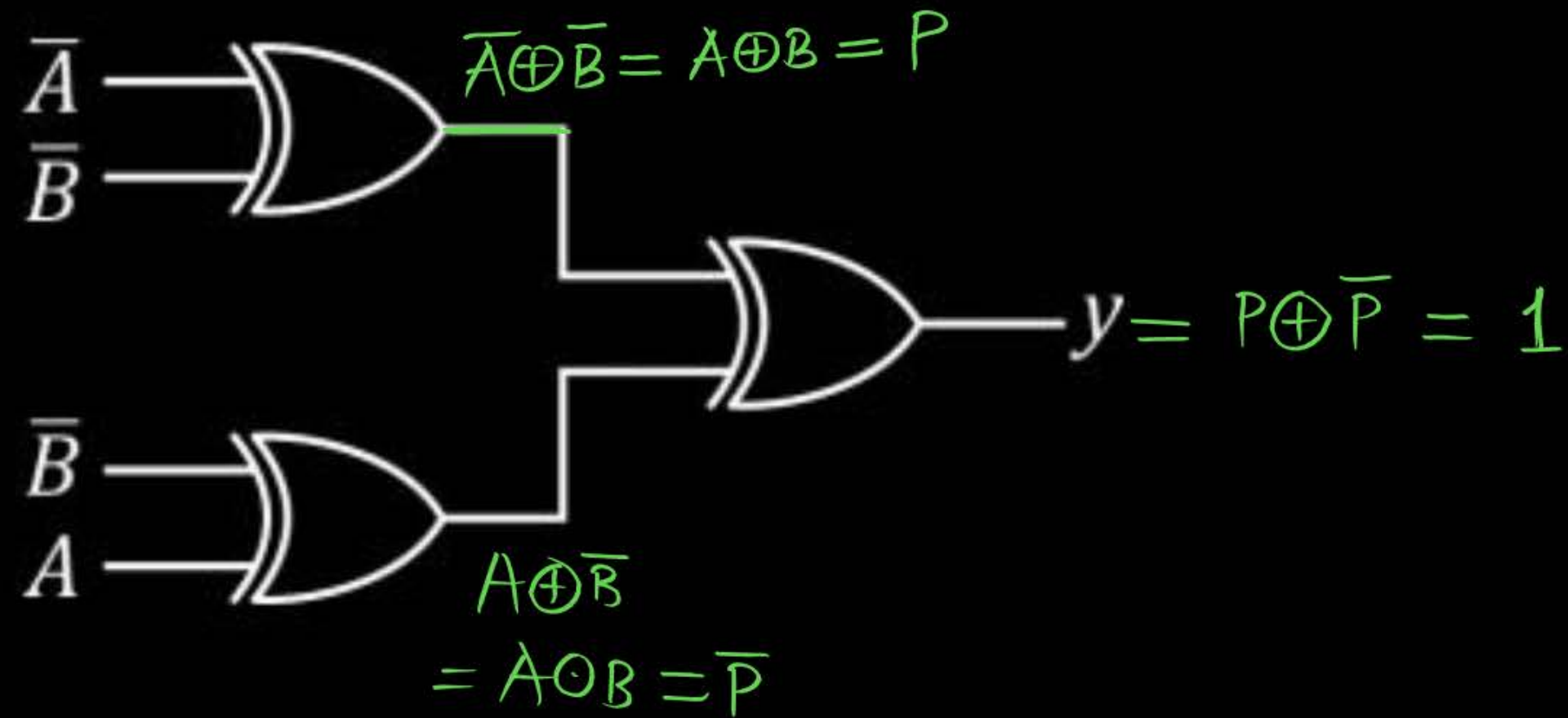

Output y is


(a) $A \odot B$

(b) $A \oplus B$

☒ (c) Always '1'

(d) Always '0'

[Question]

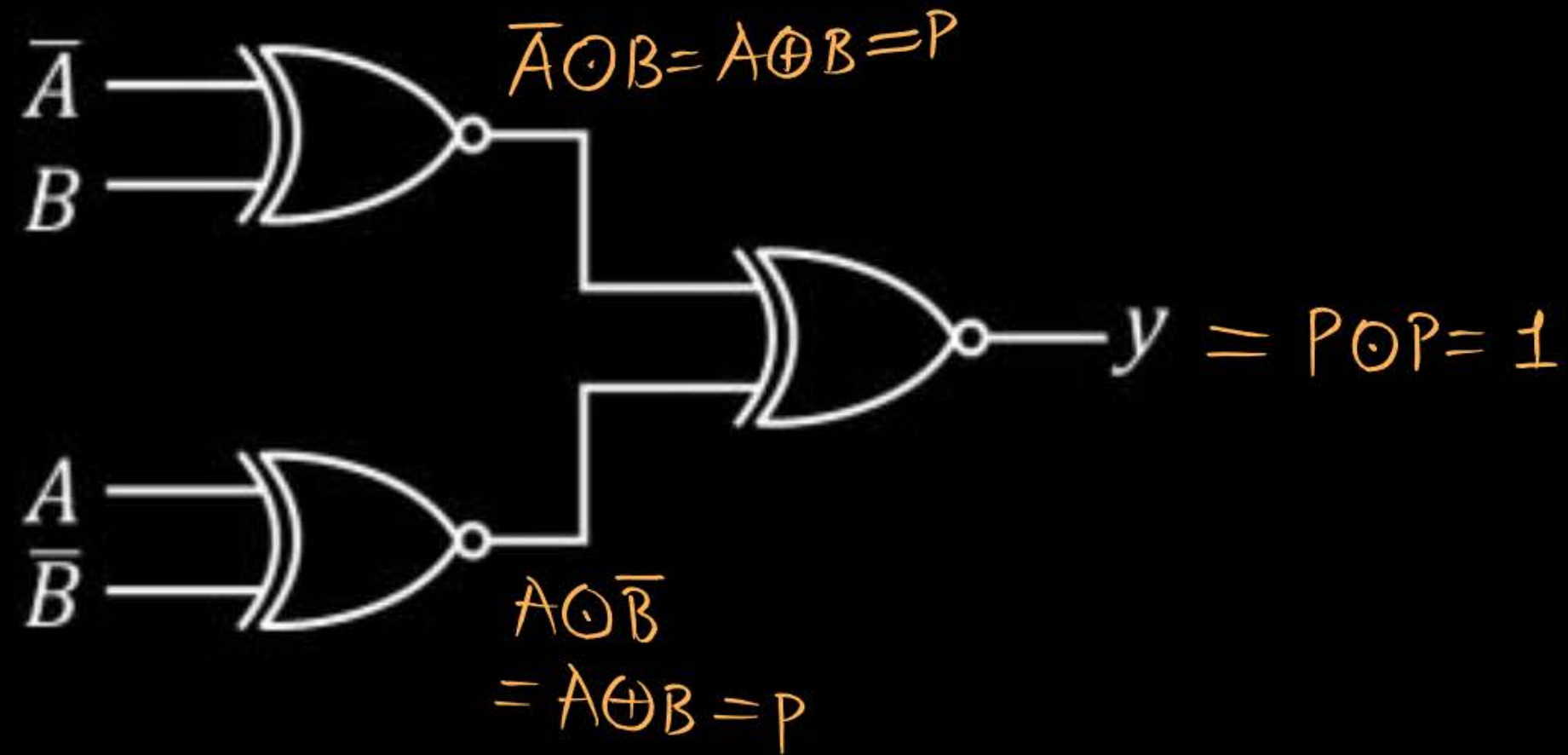

Output y is

(a) $A \oplus B$

(b) $A \odot B$

☒ (c) Always '1'


(d) Always '0'

[Question]



Output y is

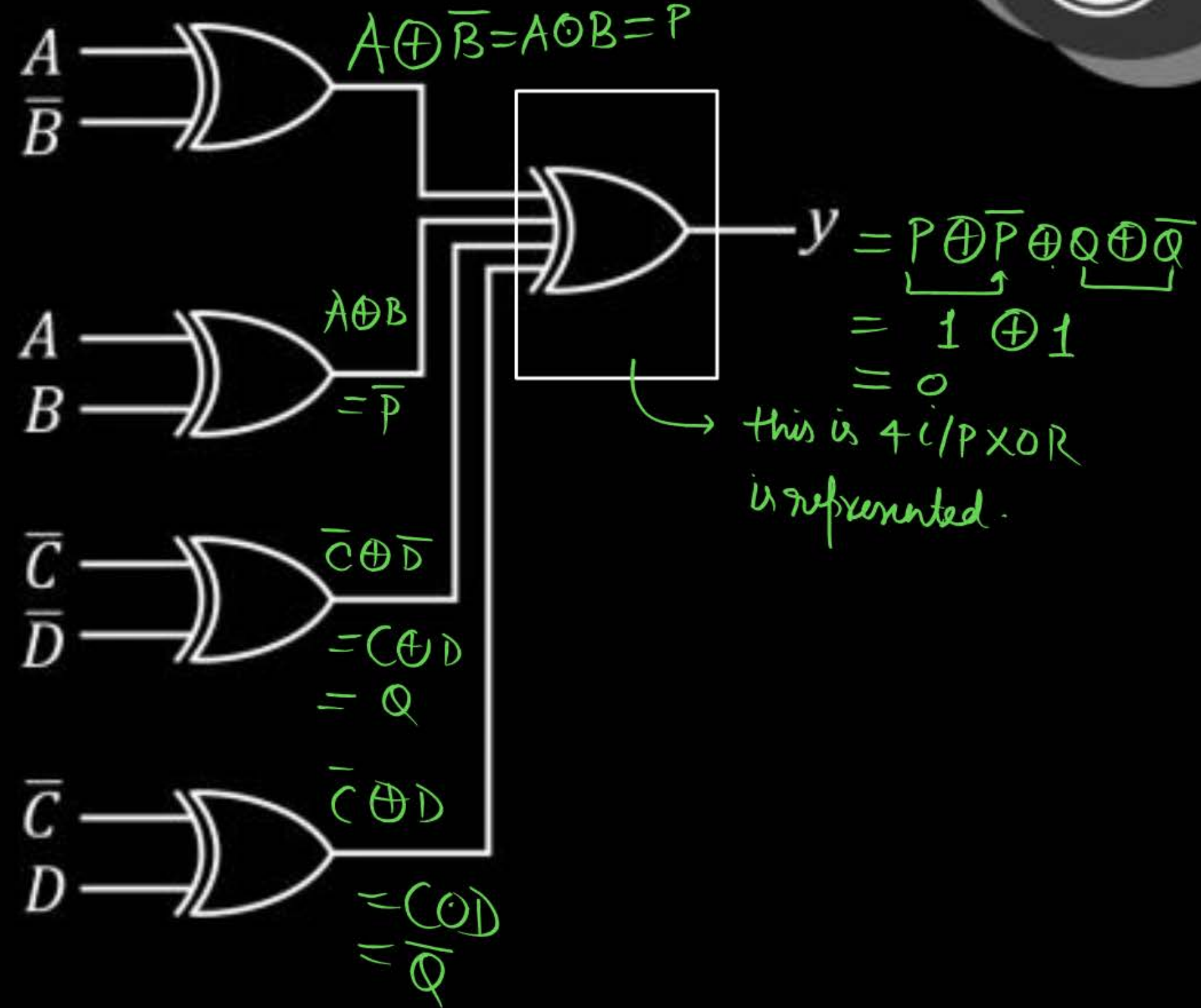- (a) $A \odot B \oplus C \oplus D$
- (b) $A \oplus B \oplus C \oplus D$
- (c) Always '0'
- (d) $A \odot B \odot C \odot D$



[Question]

$y = \overline{\overline{A \oplus B \oplus C}}$ will be equal to $= \overline{A \oplus B \oplus C} = A \odot B \oplus C = A \oplus B \odot C$

(a) ✓ $A \odot B \oplus C$

(b) ✗ $y = \overline{\overline{A} \oplus \overline{B \odot C}} = \overline{A \oplus B \odot C}$

(c) ✗ $y = \overline{A \oplus B \oplus C}$
 $= A \oplus B \oplus C$

(d) None of these $= A \odot B \odot C$

[Question]

$y = A \oplus [A + B]$ equal to

H.W.

(a) $A \oplus B$

(b) $y = A \odot B$

(c) $\bar{A}B$

(d) $A\bar{B}$

Question

$y = A \oplus B \oplus AB$ equal to

H.W.

(a) AB

(b) $(A + B)$

(c) \overline{AB}

(d) $\overline{A + B}$


#Q. $\overline{A \odot B \odot C}$ is/are equal to

a. $A \oplus B \oplus C$

b. $\bar{A} \odot B \odot C$

c. $A \odot \bar{B} \odot \bar{C}$

d. $\bar{A} \oplus B \odot \bar{C}$

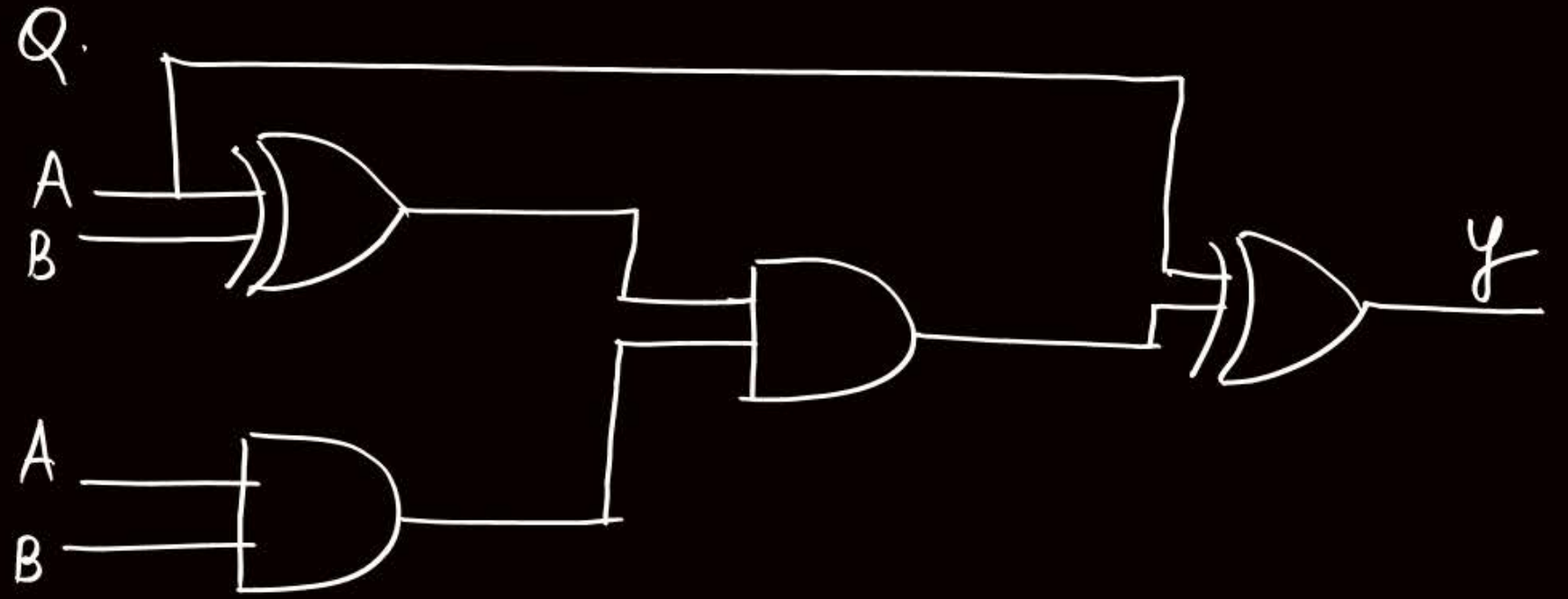

Y is


a. A

b. $A+B$

c. $A \odot B$

d. None of these.

#Q

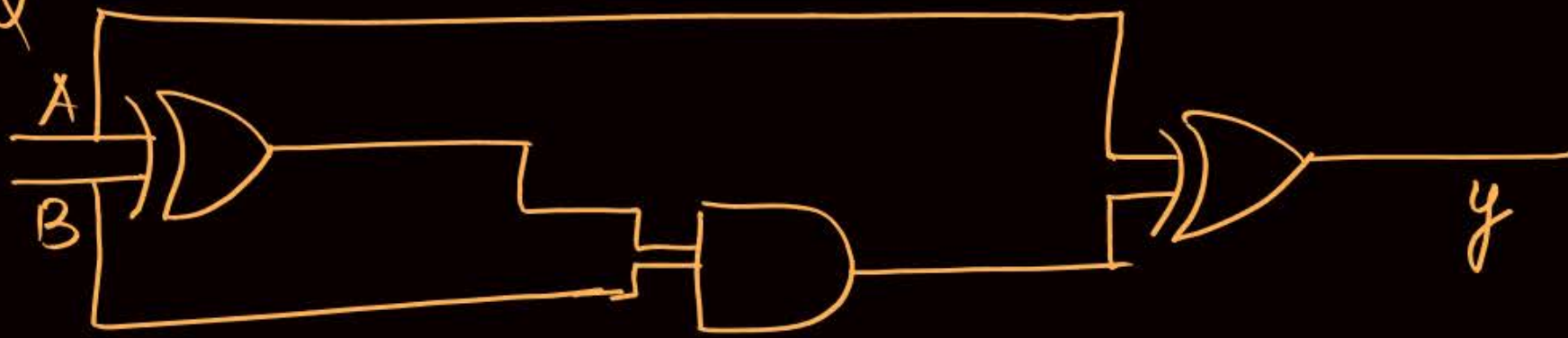

y is

- a. $A + B$
- b. $A B$
- c. $\bar{A} B$
- d. $A \odot B$



2 Minute Summary

→ XOR & XNOR

Thank you

GW
Soldiers !

