

COMPUTER SCIENCE & IT

DIGITAL LOGIC



Lecture No: 05

Sequential Circuit



By- Chandan Gupta Sir

Recap of Previous Lecture



- Asynchronous Counter
-
-



Topics to be Covered


Synchronous Counter



Q.

$Q_2 = 1$

$Q_1 = 1$

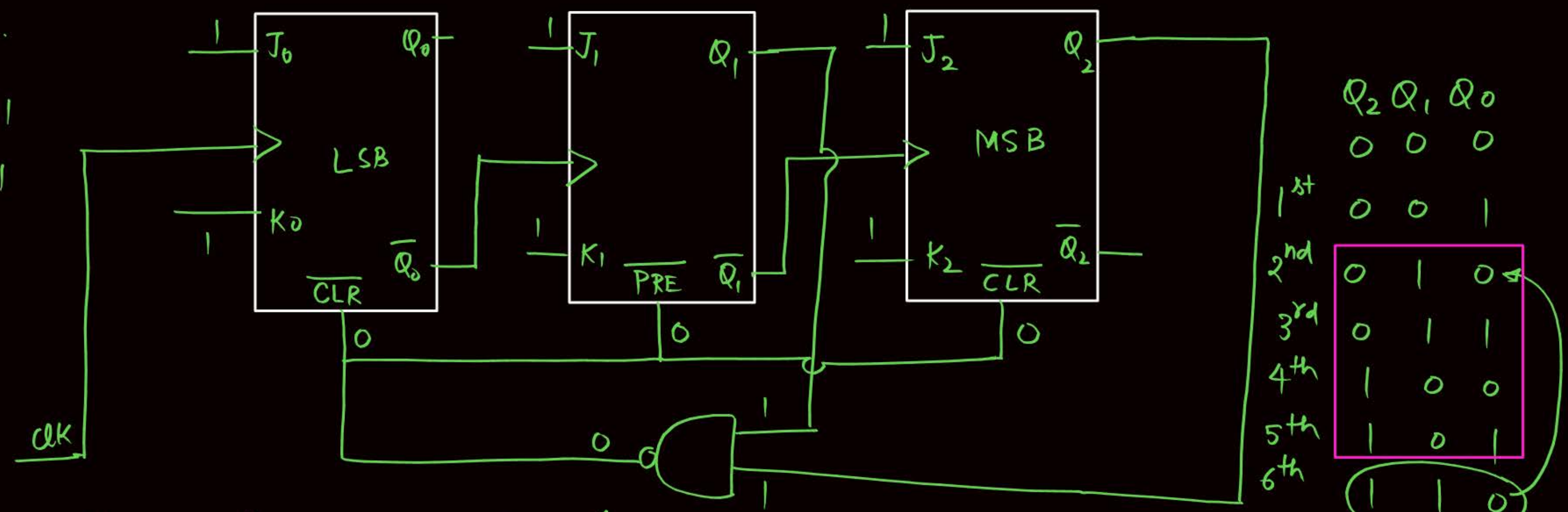


MOD no. of the above counter 4.

	Q_2	Q_1	Q_0
1 st	0	0	0
2 nd	0	0	1
3 rd	0	1	0
4 th	0	1	1
5 th	1	0	0
6 th	1	0	1

[D-FF and T-FF]

- What is D-FF ?

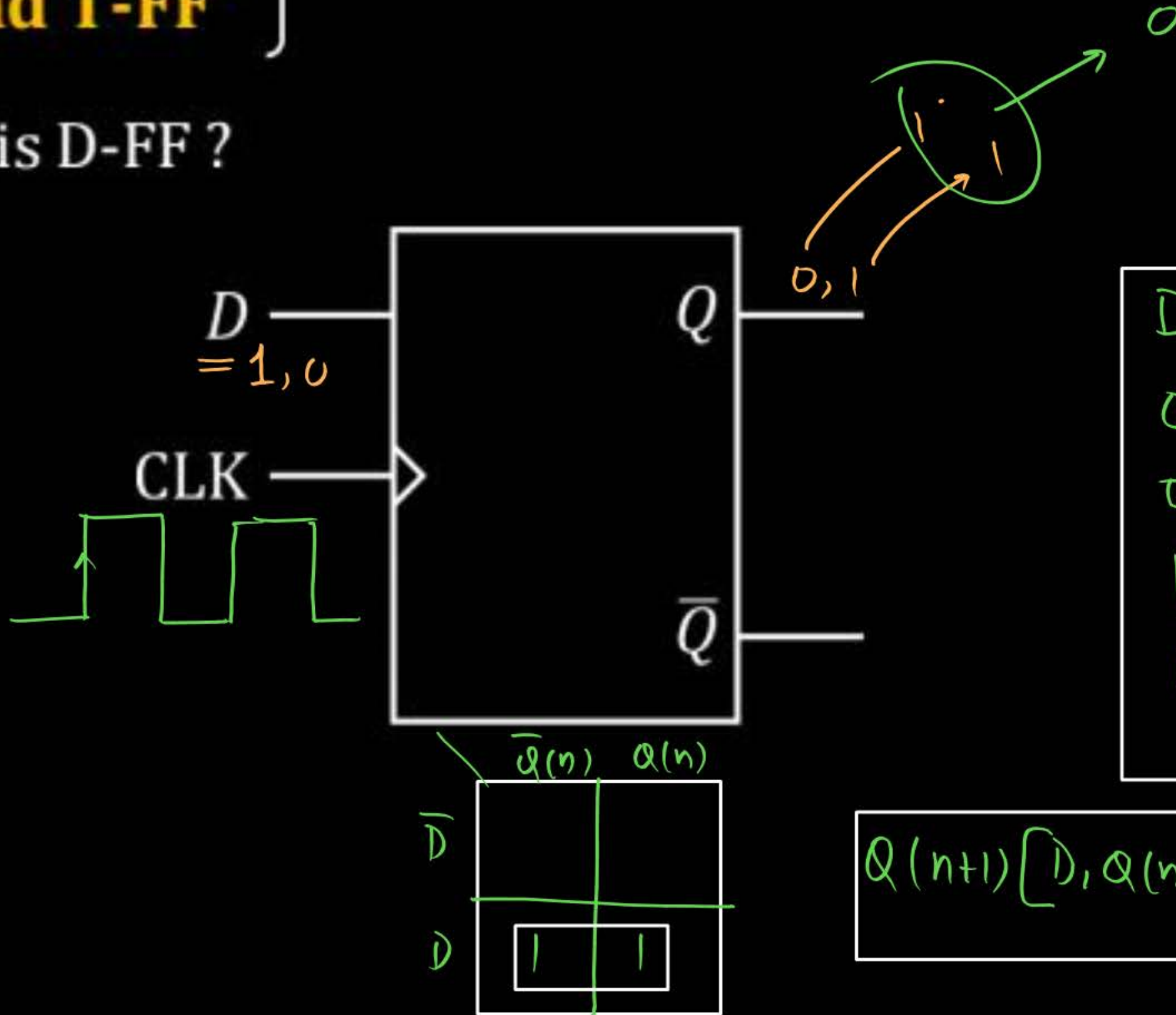

$$Q(n+1) = D$$

Characteristic table

D	$Q(n)$	$Q(n+1)$
0	0	0
0	1	0
1	0	1
1	1	1

$$Q(n+1)[D, Q(n)] = \sum(2, 3) = D$$

	$\bar{Q}(n)$	$Q(n)$
\bar{D}		
D	1	1


- Excitation table :

$Q(n)$	$Q(n+1)$	D
0	0	0
0	1	1
1	0	0
1	1	1

[T-FF]



- What is T-FF?

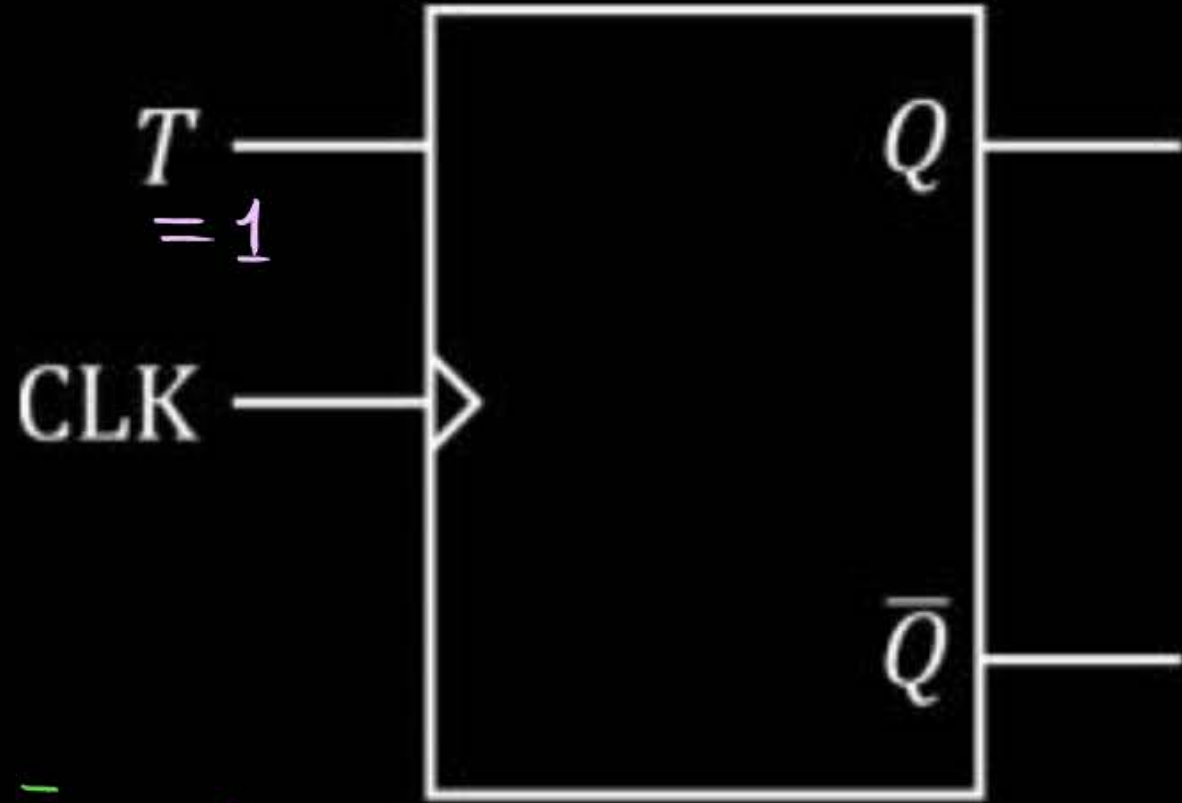

$$Q(n+1) = T \oplus Q(n)$$

$$Q(n+1) = 1 \oplus Q(n) = \overline{Q(n)}$$

Characteristic table

T	Q(n)	Q(n+1)
0	0	0
0	1	1
1	0	1
1	1	0

Hold state (for T=0, Q(n)=0 or 1)

Toggle state (for T=1, Q(n)=0 or 1)

	$\overline{Q}(n)$	Q(n)
H		1
T	1	

$$Q(n+1)[T, Q(n)]$$

$$= \Sigma(1, 2) = \overline{T}Q(n) + T\overline{Q}(n) = T \oplus Q(n)$$


- Excitation table :

$Q(n)$	$Q(n+1)$	T
0	0	0
0	1	1
1	0	1
1	1	0


[Toggle mode of operation]



(i)

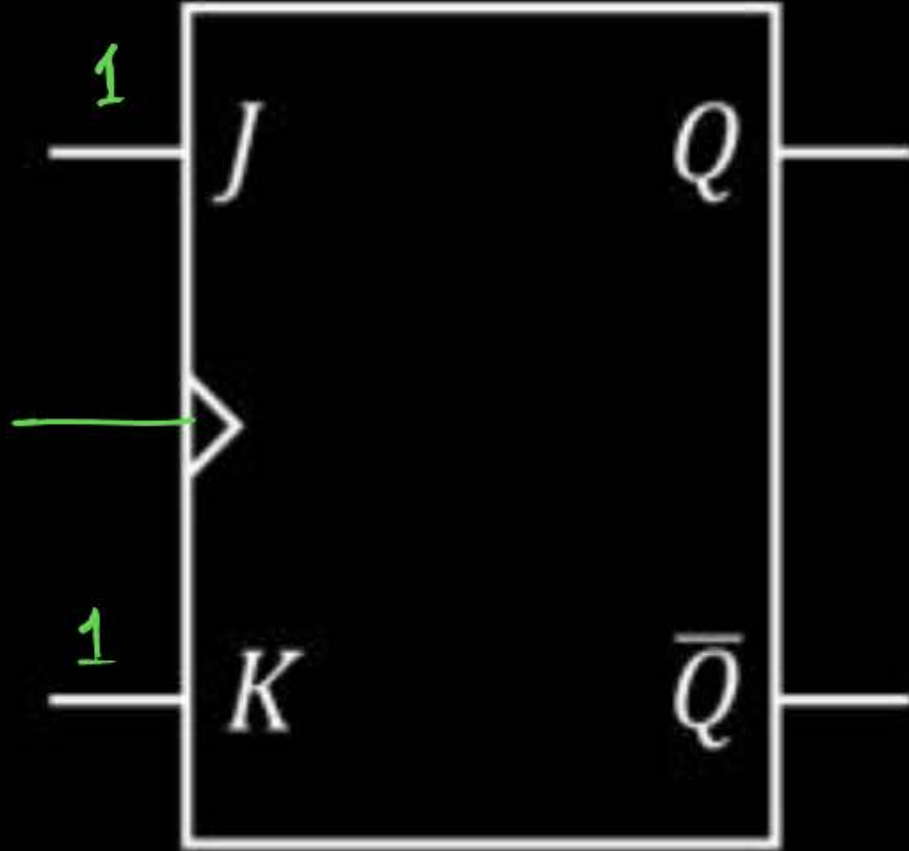

(ii)

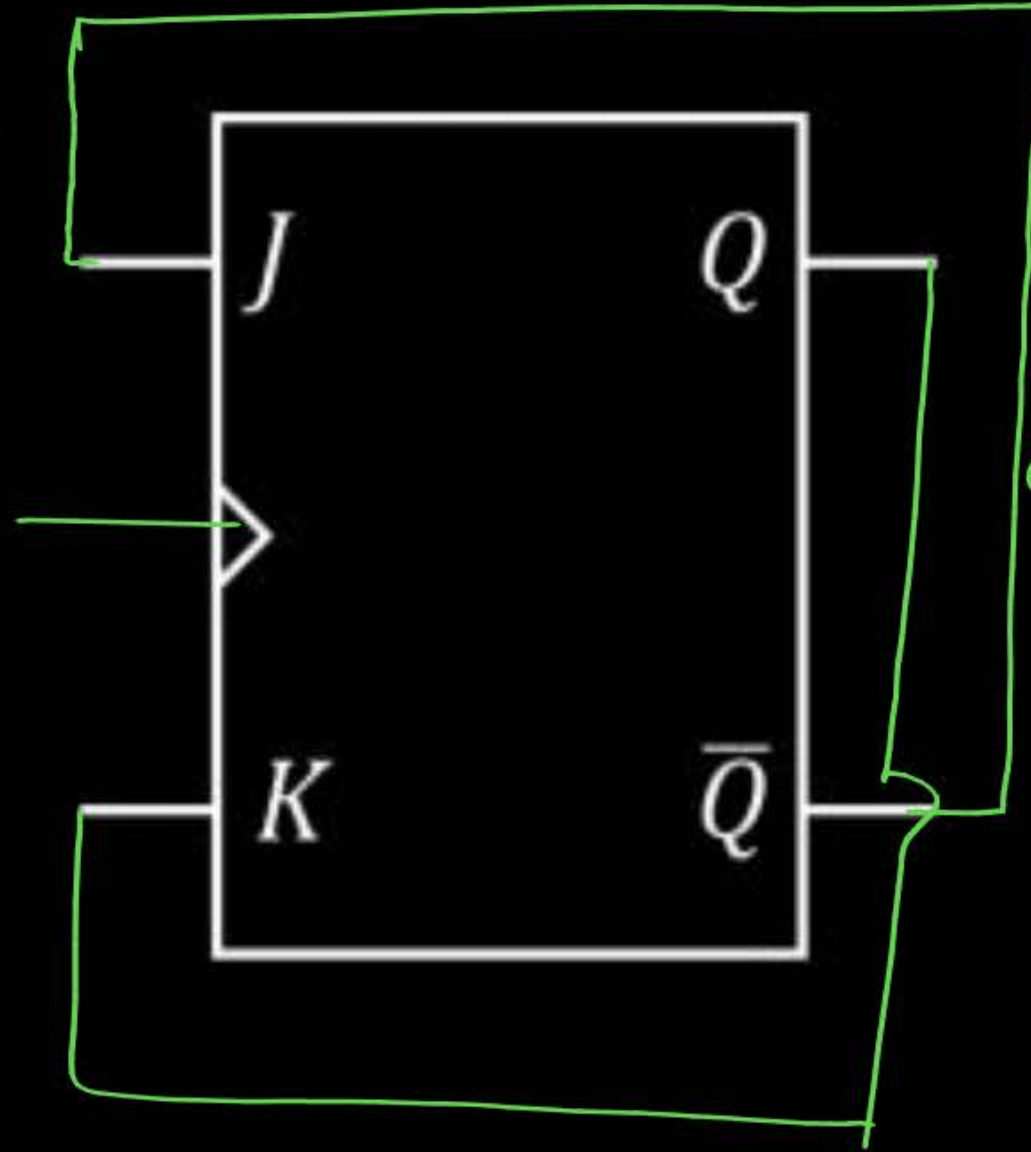


$$\begin{aligned} Q(n+1) &= J \bar{Q}(n) + \bar{K} Q(n) \\ &= \bar{Q}(n) \bar{Q}(n) + \bar{Q}(n) \cdot Q(n) \end{aligned}$$

$$Q(n+1) = \bar{Q}(n)$$


$$\boxed{Q(n+1) = \bar{Q}(n)}$$

↓
toggle
mode
of operation
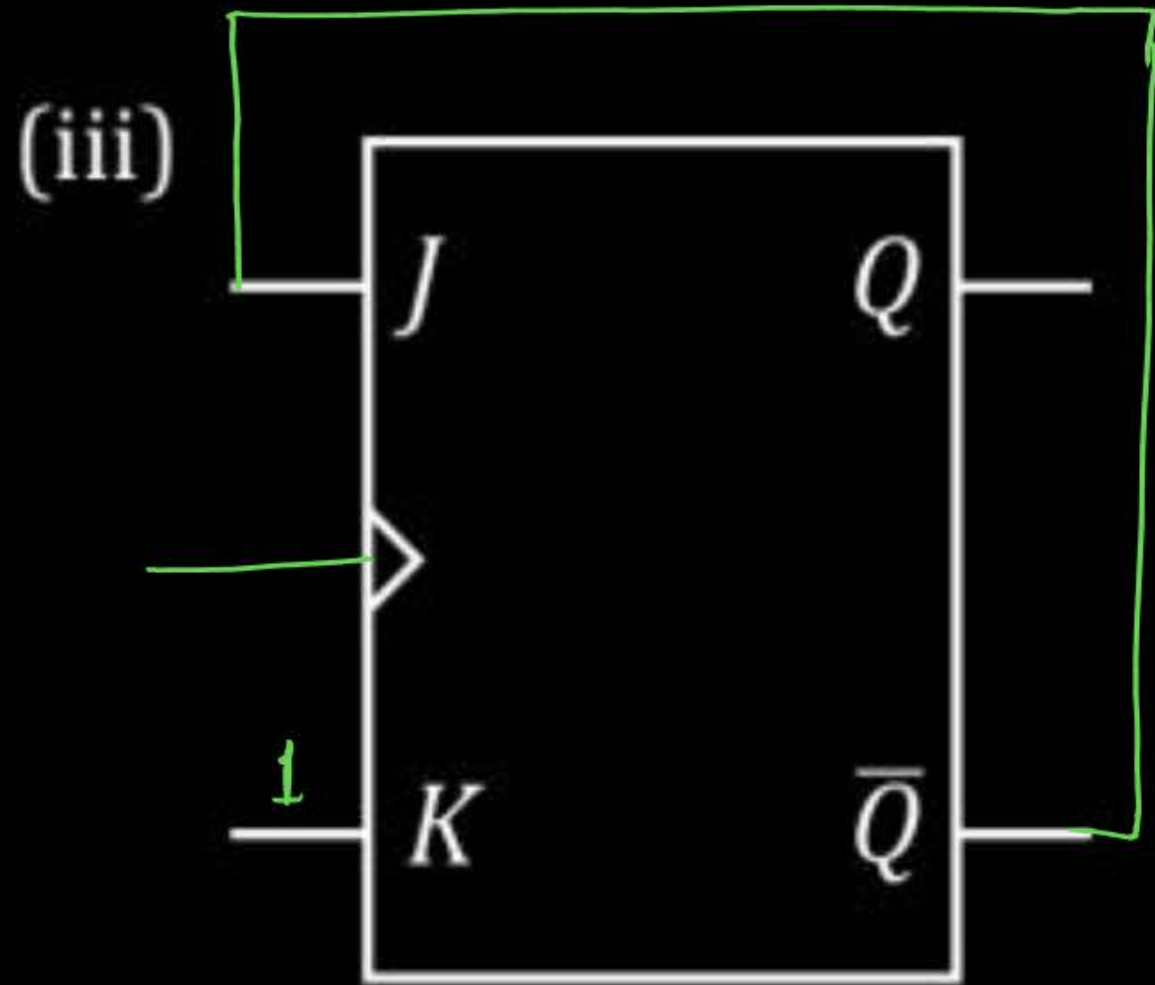
$$Q(n+1) = J \bar{Q}(n) + \bar{K} Q(n) = \bar{Q}(n) + 0 = \bar{Q}(n)$$



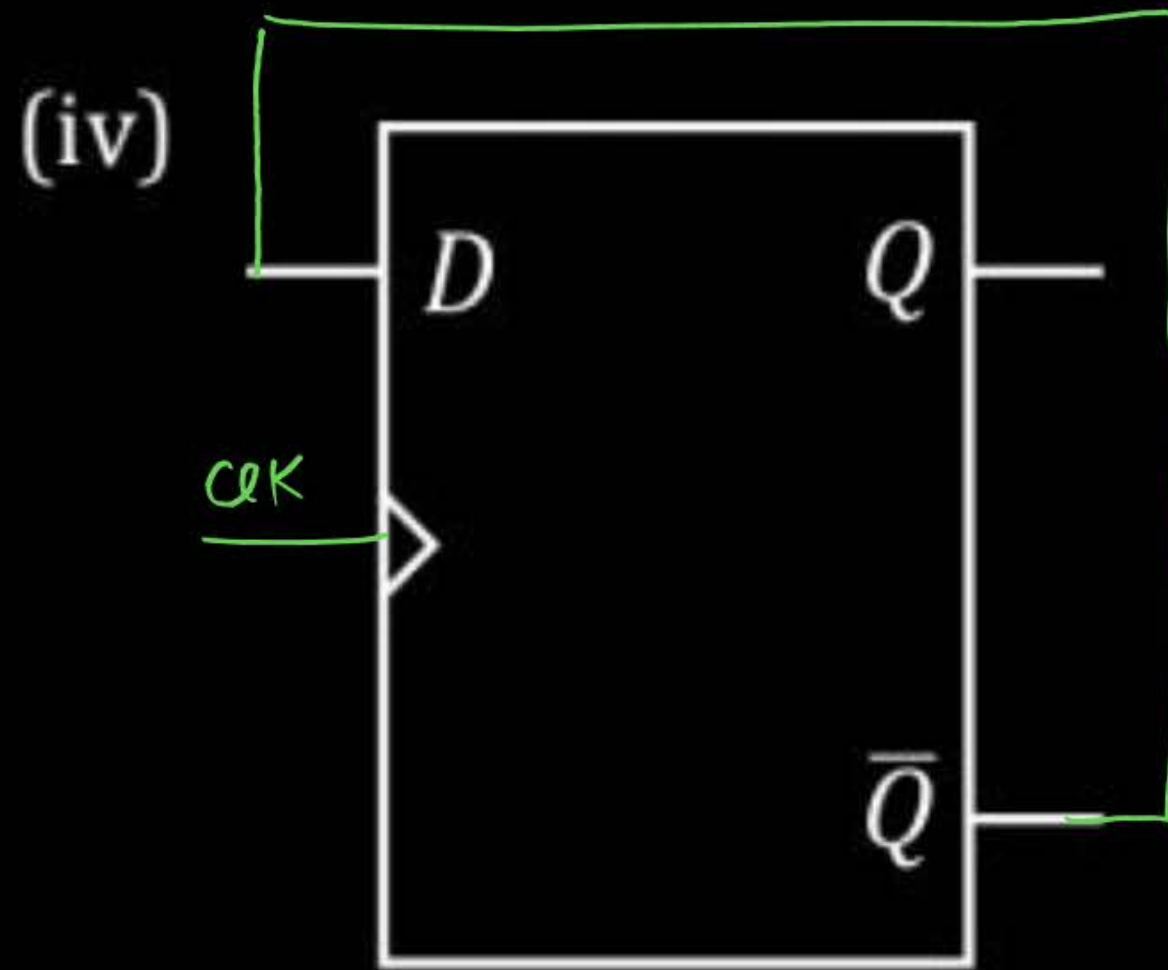
$$\begin{aligned}
 Q(n+1) &= \bar{J} \bar{Q}(n) + \bar{K} Q(n) \\
 &= \bar{Q}(n) \bar{Q}(n) + \bar{J} Q(n) \\
 Q(n+1) &= \bar{Q}(n)
 \end{aligned}$$




$$Q(n+1) = D = \bar{Q}(n)$$

(v)

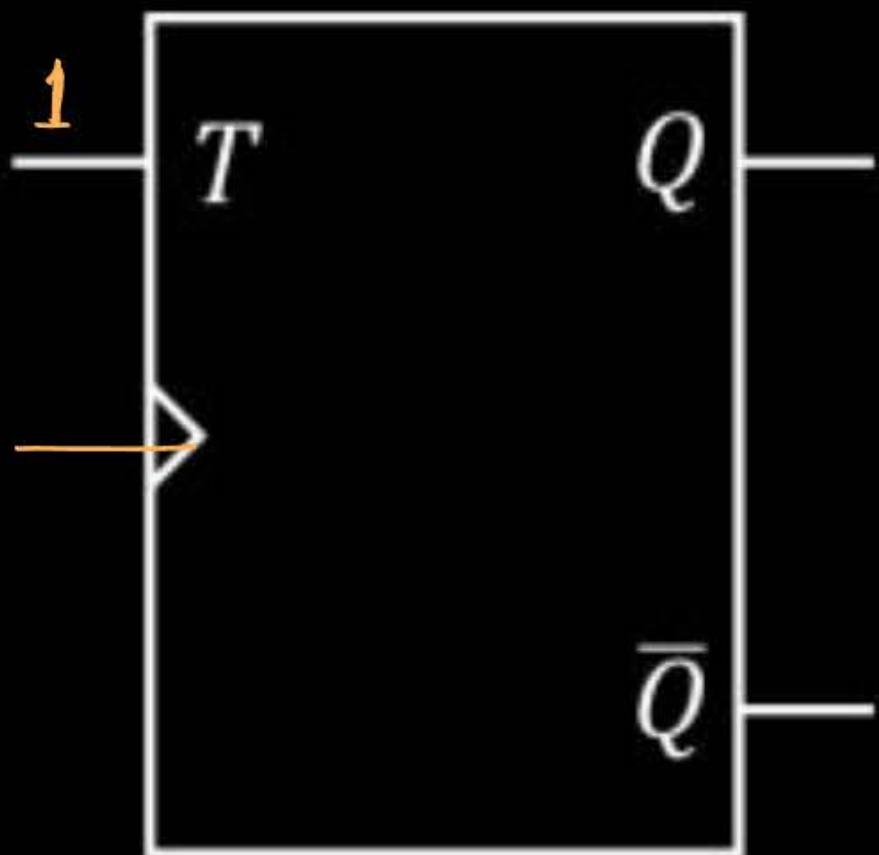
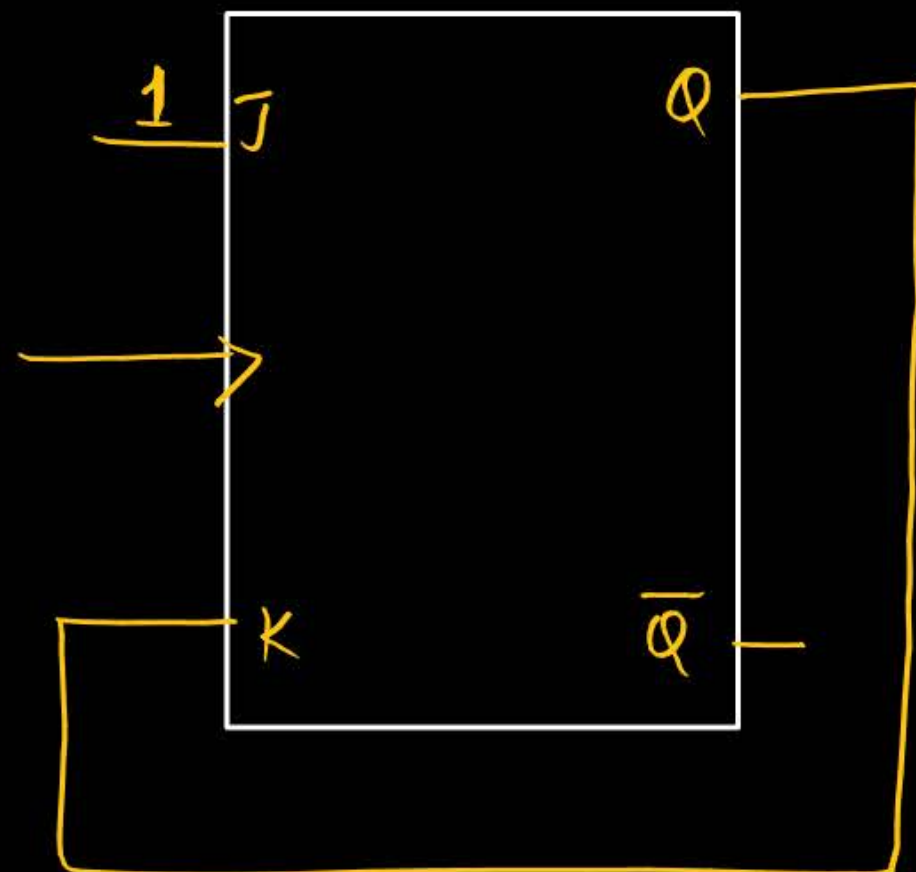
$$Q(n+1) = T \oplus Q(n) = 1 \oplus Q(n) = \overline{Q(n)}$$




$$\begin{aligned} Q(n+1) &= J\overline{Q}(n) + \overline{K}Q(n) \\ &= 1\overline{Q}(n) + \overline{Q(n)}Q(n) \\ Q(n+1) &= \overline{Q}(n) \end{aligned}$$

	$f_{clk}/2$	
	Q	
1 st	0] → MOD-2 Counter
	1	
2 nd	0	
3 rd	1	

Toggle mode of operation is the smallest counter possible i.e. MOD-2 Counter.



Lets analyze asynchronous counter :

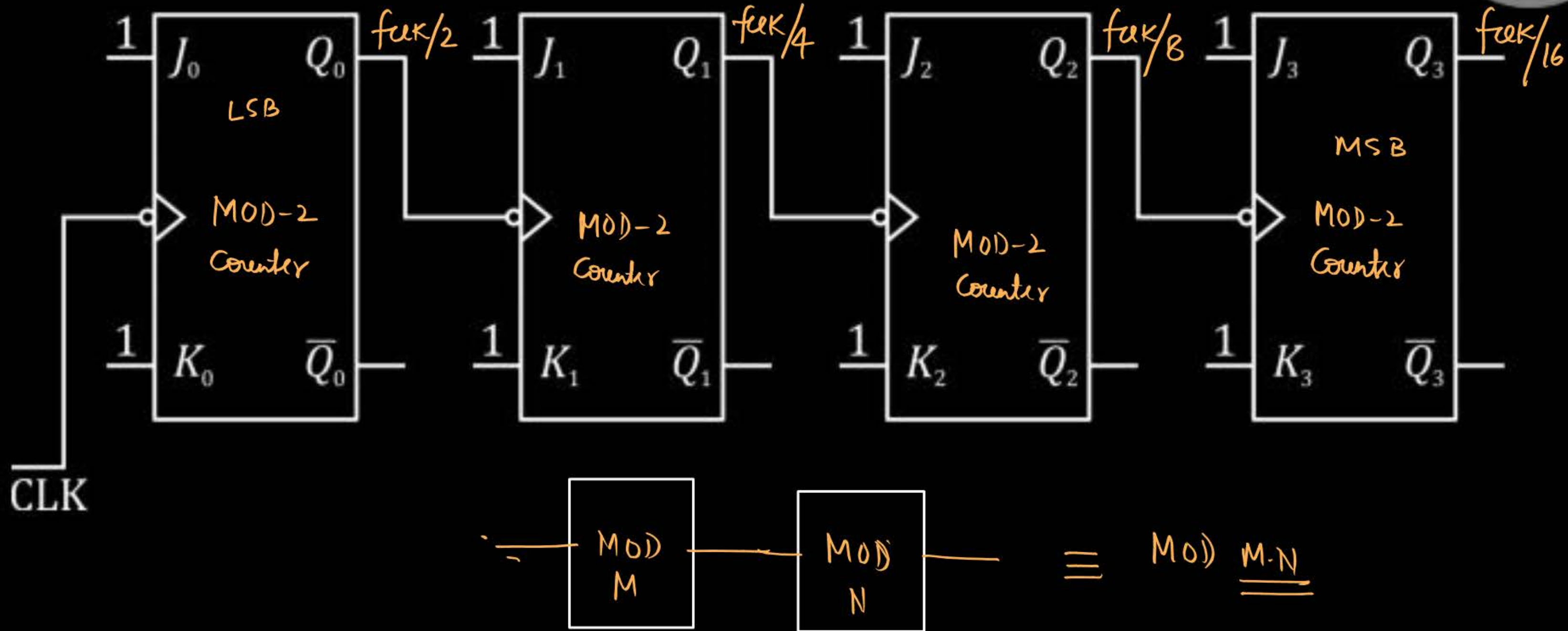

[Synchronous Counter]



- What is synchronous counter ?

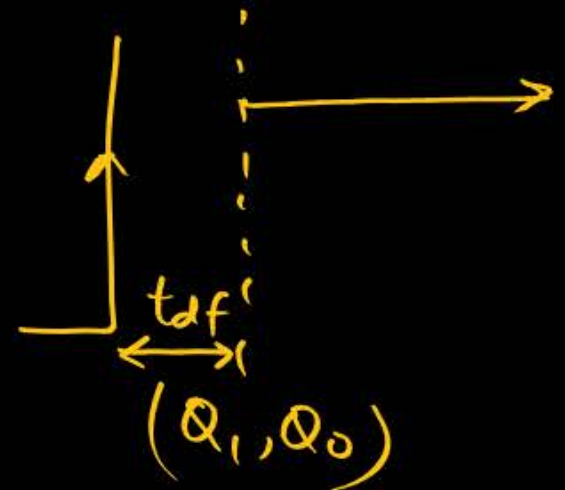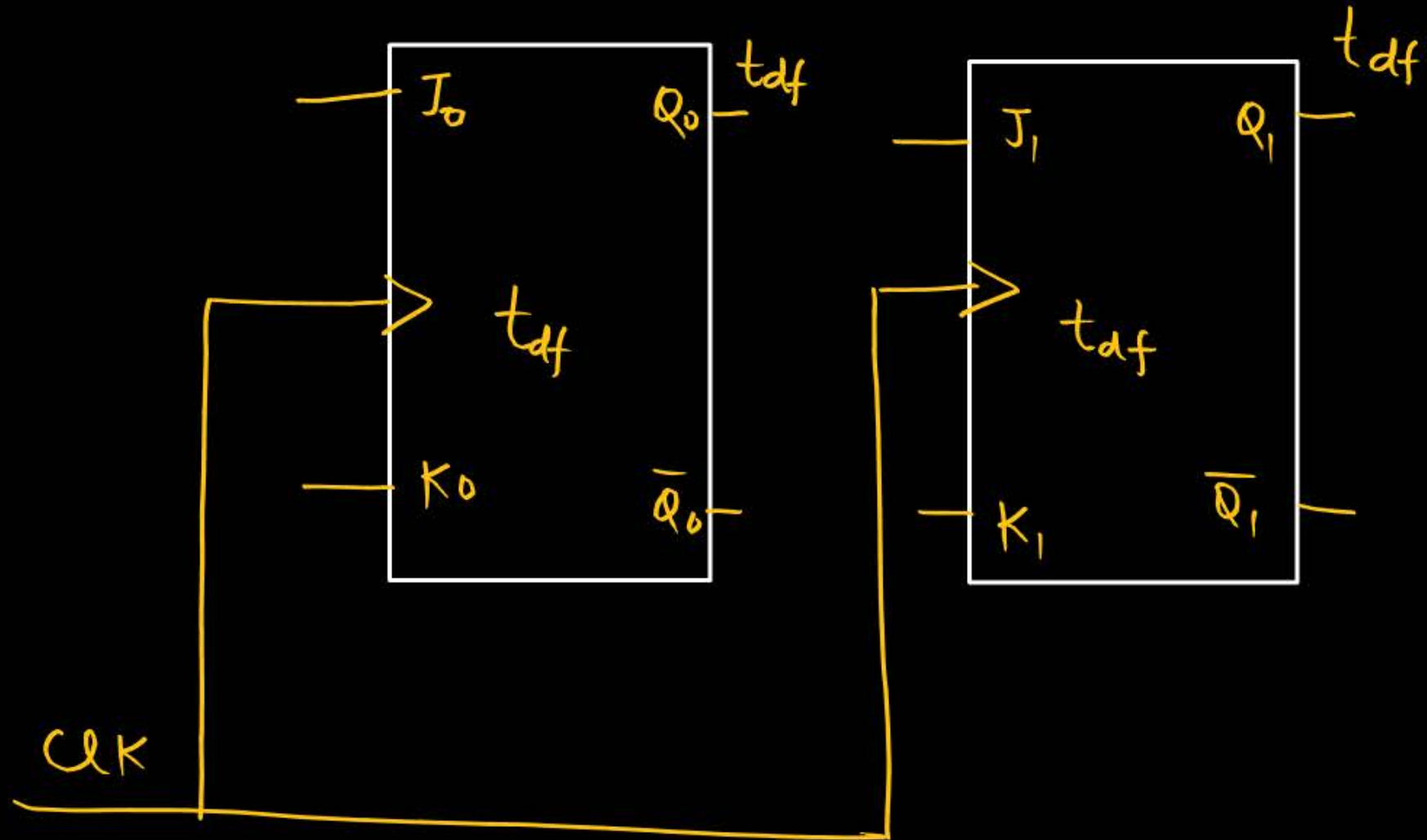

$$T_{clk} \geq t_{df}$$

$$f_{clk} \leq 1/t_{df}$$

$$(f_{clk})_{max} = \frac{1}{t_{df}}$$



[How to design a Synchronous Counter]

- $0 - 3 - 2 - 1 \longrightarrow \text{MOD no.} = 4 \longrightarrow 2\text{FF} \longrightarrow$

Design above counter using JK-FF

$Q_1(n)$	$Q_0(n)$	$Q_1(n+1)$	$Q_0(n+1)$	J_1	K_1	J_0	K_0
0	0	1	1	1	X	1	X
0	1	0	0	0	X	X	1
1	0	0	1	X	1	1	X
1	1	1	0	X	0	X	1

	Q_1	Q_0
	0	0
1 st	1	1
2 nd	1	0
3 rd	0	1
4 th	0	0

$$J_1[Q_1(n), Q_0(n)] = \Sigma(0) + d\Sigma(2,3) \quad , \quad K_1 = \Sigma 2 + d\Sigma(0,1)$$

$$J_0 = \Sigma(0,2) + d\Sigma(1,3) \quad , \quad K_0 = \Sigma(1,3) + d\Sigma(0,2)$$

J_1	$\overline{Q_0(n)}$	$Q_0(n)$
$\overline{Q_1(n)}$	1	
$Q_1(n)$	X	X

$$\rightarrow J_1 = \overline{Q_0(n)}$$

K_1	$\overline{Q_0(n)}$	$Q_0(n)$
$\overline{Q_1(n)}$	X	X
$Q_1(n)$	1	


$$\rightarrow K_1 = \overline{Q_0(n)}$$

J_0	$\overline{Q_0(n)}$	$Q_0(n)$
$\overline{Q_1(n)}$	1	X
$Q_1(n)$	1	X

$$J_0 = 1$$

K_0	$\overline{Q_0(n)}$	$Q_0(n)$
$\overline{Q_1(n)}$	X	1
$Q_1(n)$	X	1

$$K_0 = 1$$

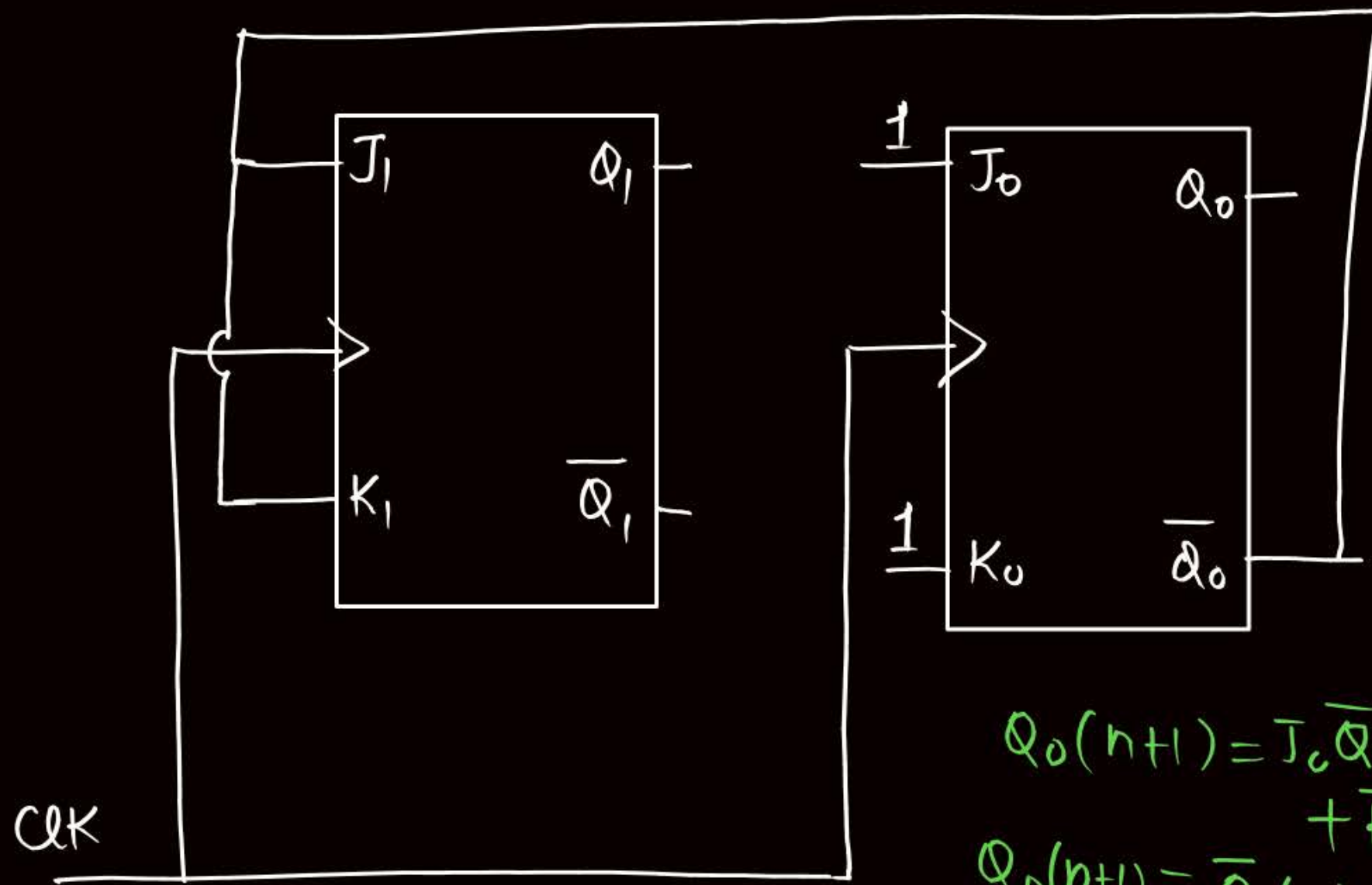

$$Q_1 = 0, Q_0 = 0$$

$$Q_1, Q_0 = (00)$$

	Q_1	Q_0	
	0	0	←
1 st	1	1	
2 nd	1	0	
3 rd	0	1	←
4 th	0	0	

MOD no
4

$$Q_0(n+1) = J_0 \bar{Q}_0(n) + \bar{K}_0 Q_0(n)$$

$$Q_0(n+1) = \bar{Q}_0(n)$$

$$Q_1(n+1) = J_1 \bar{Q}_1(n) + \bar{K}_1 Q_1(n)$$

$$= \bar{Q}_0(n) \bar{Q}_1(n) + Q_0(n) Q_1(n)$$

$$= Q_1(n) \odot Q_0(n)$$

Q_0	Q_1
0	0
1	1
0	1
1	0

$$Q_0, Q_1 = (00)$$

- Design counter 0 – 1 – 2 – 4 – 6 using T-FF $\rightarrow \text{MOD no. } 5 \rightarrow 3\text{FF}$

$Q_2(n)$	$Q_1(n)$	$Q_0(n)$	$Q_2(n+1)$	$Q_1(n+1)$	$Q_0(n+1)$	T_2	T_1	T_0
0	0	0	0	0	1	0	0	1
0	0	1	0	1	0	0	1	1
0	1	0	1	0	0	1	1	0
0	1	1	X	X	X	X	X	X
1	0	0	1	1	0	0	1	0
1	0	1	X	X	X	X	X	X
1	1	0	0	0	0	1	1	0
1	1	1	X	X	X	X	X	X

$$T_2 = \Sigma(2,6) + d \Sigma(3,5,7)$$

$$T_1 = \Sigma(1,2,4,6) + d \Sigma(3,5,7)$$

$$T_0 = \Sigma(0,1) + d \Sigma(3,5,7)$$

T_2

	$\bar{Q}_1 \bar{Q}_0$	$\bar{Q}_1 Q_0$	$Q_1 Q_0$	$Q_1 \bar{Q}_0$
$\bar{Q}_2(n)$			X	1
$Q_2(n)$		X	X	1

Q_1
 $T_2 = Q_1(n)$

T_1

	$\bar{Q}_1 \bar{Q}_0$	$\bar{Q}_1 Q_0$	$Q_1 Q_0$	$Q_1 \bar{Q}_0$
\bar{Q}_2		1	X	1
Q_2	1	X	X	1


$T_1 = Q_2 + Q_1 + Q_0$

T_0

	$\bar{Q}_1 \bar{Q}_0$	$\bar{Q}_1 Q_0$	$Q_1 Q_0$	$Q_1 \bar{Q}_0$
\bar{Q}_2	1	1	X	
Q_2		X	X	

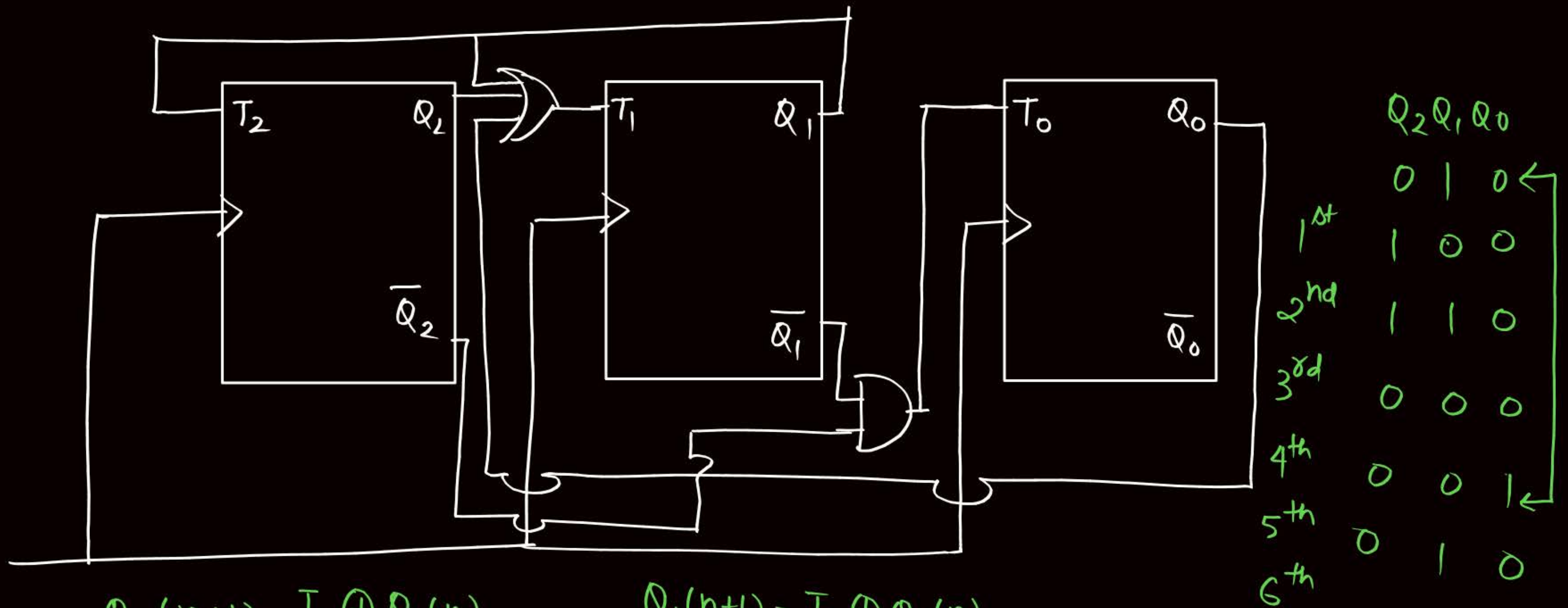$T_0 = \bar{Q}_2(n) \bar{Q}_1(n) = \overline{Q_2(n) + Q_1(n)}$





$$Q_2(n+1) = T_2 \oplus Q_2(n)$$

$$= Q_1(n) \oplus Q_2(n)$$

$$Q_1(n+1) = T_1 \oplus Q_1(n)$$

$$= [Q_2(n) + Q_1(n) + Q_0(n)] \oplus Q_1(n)$$

$$= \overline{Q_2(n)} \cdot \overline{Q_1(n)} \cdot \overline{Q_0(n)} \cdot Q_1(n) + [Q_2(n) + Q_1(n) + Q_0(n)] \cdot Q_1(n)$$

$$Q_0(n+1) = T_0 \oplus Q_0(n)$$

$$= \overline{Q_1(n)} \overline{Q_2(n)} \oplus Q_0(n)$$

$$= \overline{Q_2(n) + Q_1(n)} \oplus Q_0(n)$$

$$Q_1(n+1) = [Q_2(n) + Q_0(n)] \overline{Q_1(n)}$$

[Question]


A sequential circuit is as given below :

$$Q_1(n+1) = J_1 \bar{Q}_1(n) + \bar{K}_1 Q_1(n)$$

$$= Q_0(n) \bar{Q}_1(n) + \bar{Q}_0(n) Q_1(n)$$

$$Q_1(n+1) = Q_1(n) \oplus Q_0(n)$$

$$Q_0(n+1) = \bar{Q}_0(n)$$

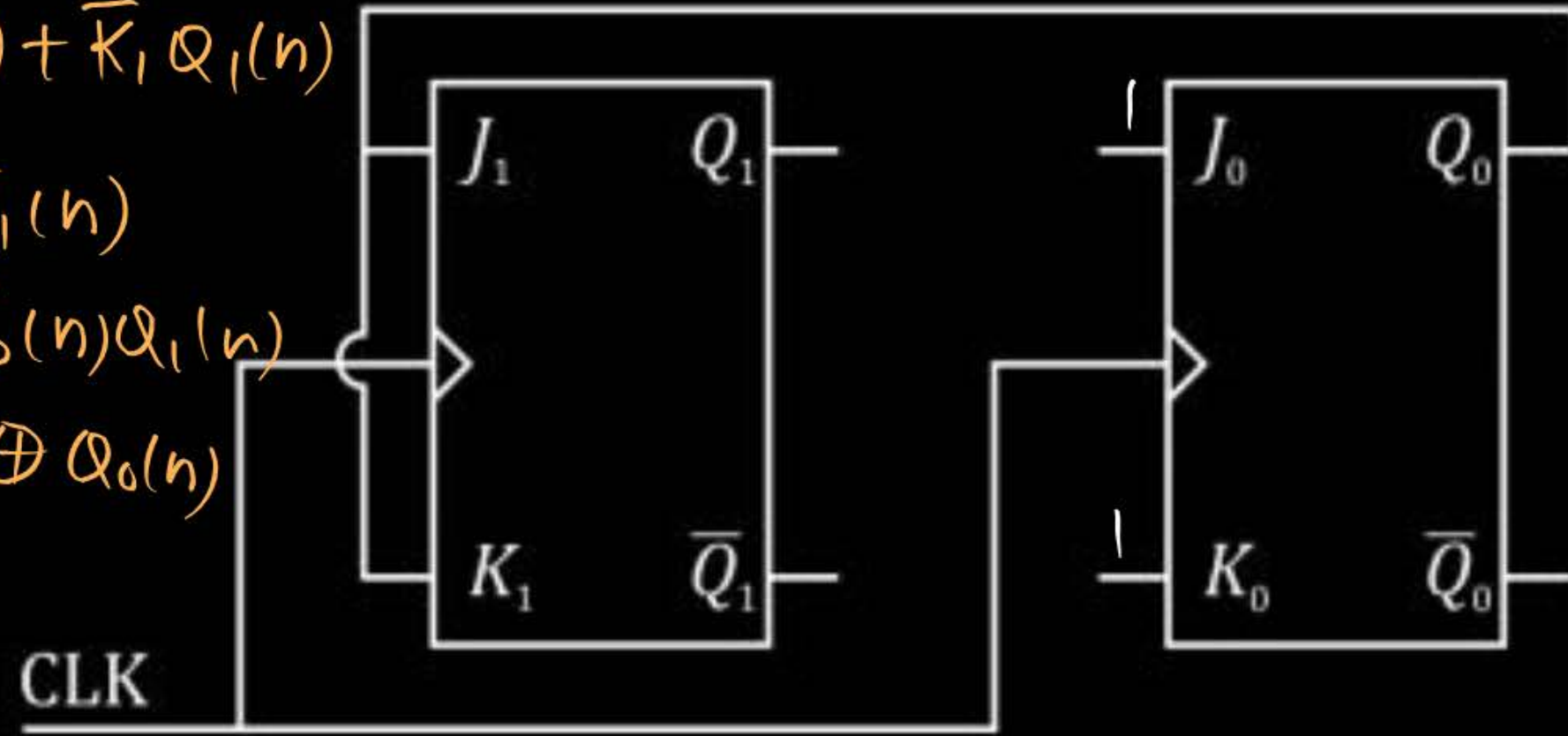

	Q_0	Q_1
	0	0
1 st	1	0
2 nd	0	1
3 rd	1	1
4 th	0	0

Initial state of the synchronous counter is given as $Q_0 Q_1 = (00)_2$ what will be states of counter after applying clock pulses.


- (a) 00 - 10 - 01 - 11 - 00
- (c) 00 - 11 - 10 - 01 - 00

- (b) 00 - 10 - 11 - 01 - 00
- (d) 00 - 01 - 10 - 11 - 00

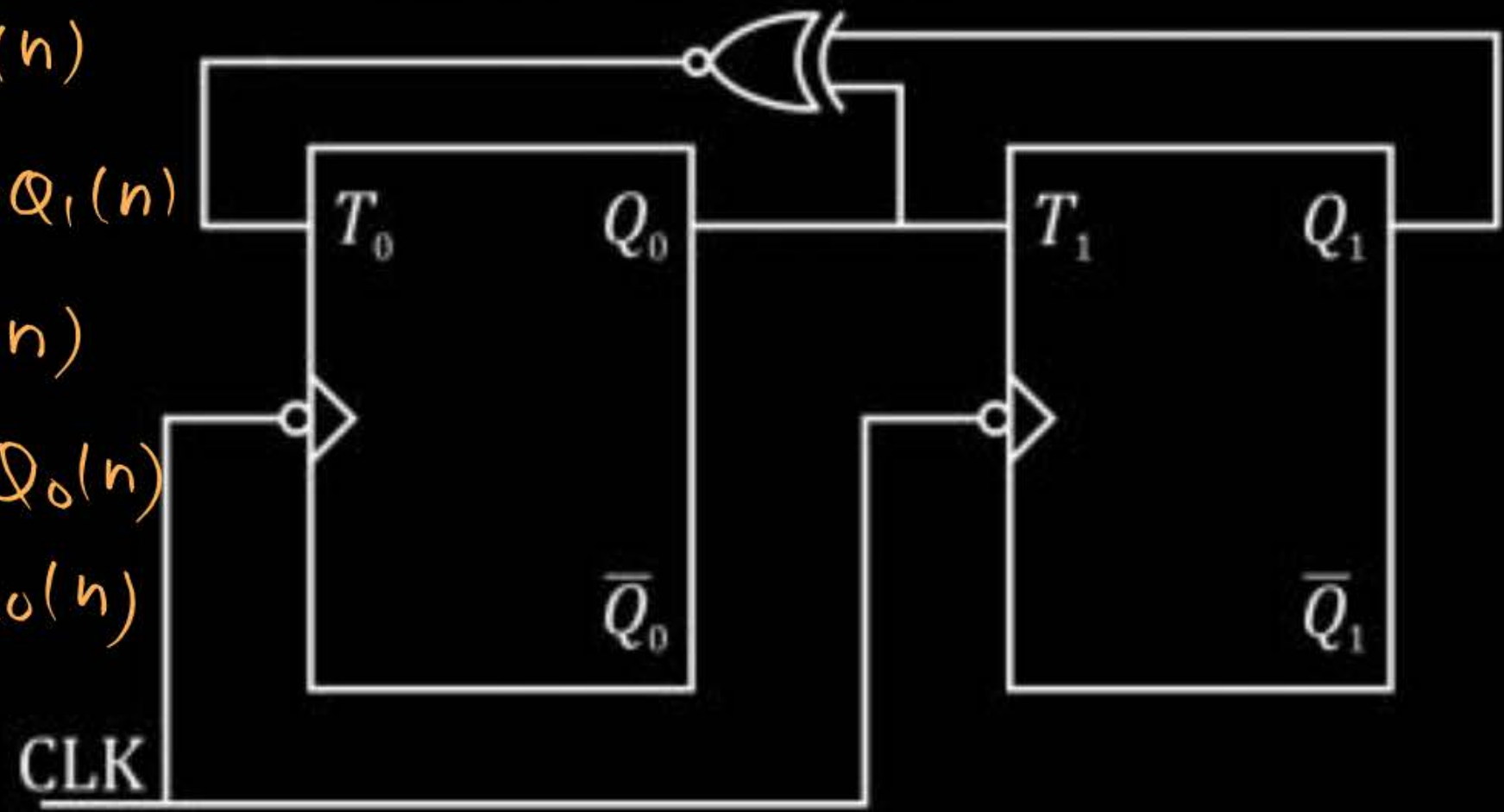[Question]

The initial state of the given counter is $Q_1Q_0 = (00)_2$. What will be states of counter after applying clock pulses :

$$\begin{aligned} (n+1) &= T_1 \oplus Q_1(n) \\ &= Q_0(n) \oplus Q_1(n) \\ (n+1) &= T_0 \oplus Q_0(n) \\ &= Q_1(n) \oplus Q_0(n) \\ (n+1) &= \overline{Q_1(n)} \oplus Q_0(n) \end{aligned}$$



	Q_1	Q_0	
1 st	0	0	MOD 3 = 3
2 nd	0	1	
3 rd	1	1	
	0	0	


- | | |
|---------------------------------------|----------------------------------|
| (a) 00 - 10 - 11 - 01 - 00 | (b) 00 - 01 - 11 - 00 |
| (c) 00 - 11 - 01 - 10 - 00 | (d) 00 - 01 - 10 - 00 |

[Question]

A sequential circuit is as given below :

$$Q_0(n+1) = D_0 = \overline{Q_1}(n)$$

$$Q_1(n+1) = D_1 = Q_0(n)$$

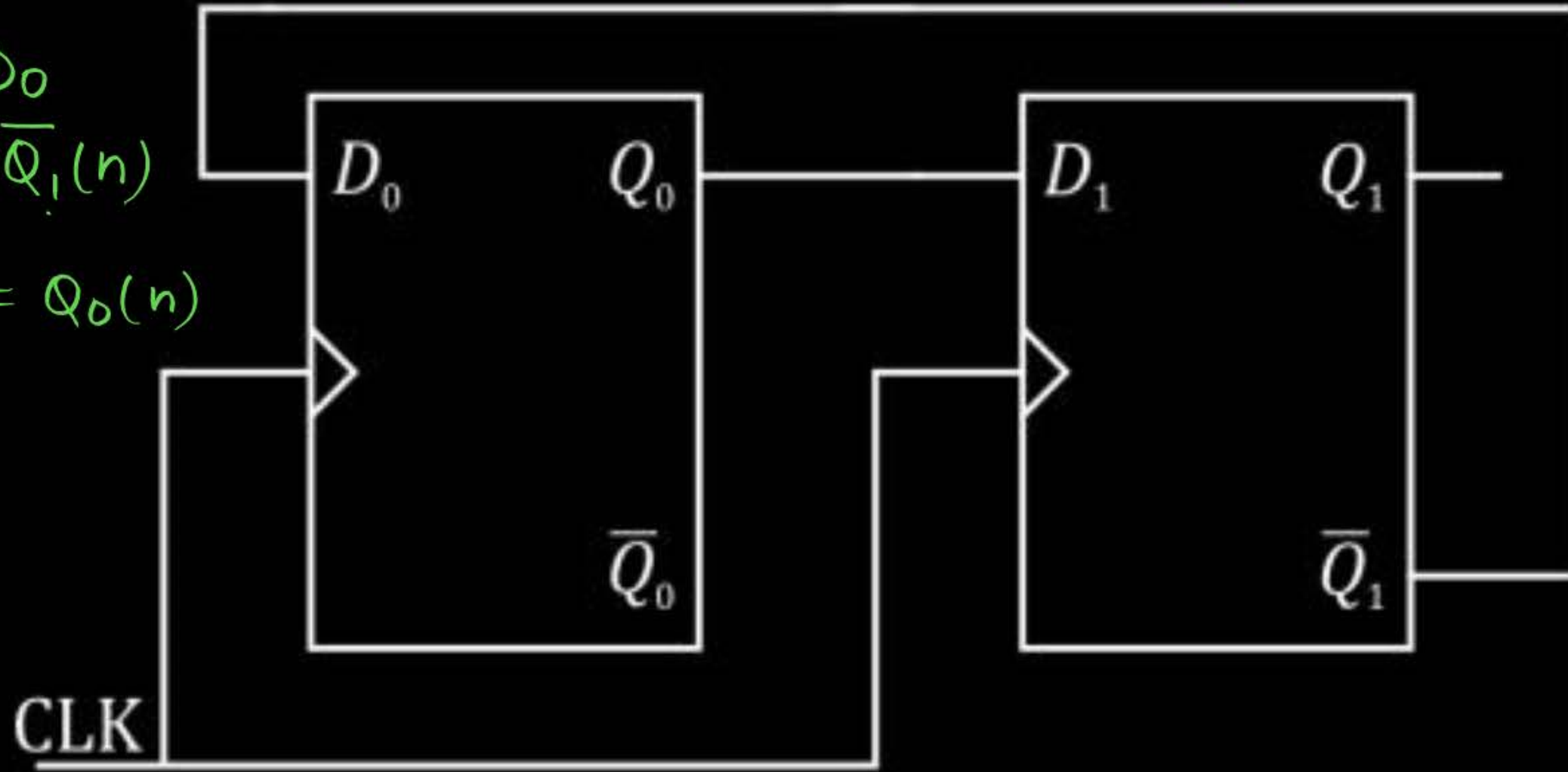

$$(0 - 2 - 3 - 1)$$

$$(0)_{10} \xrightarrow{4 \times 55} (0)_{10} \xrightarrow{221^{th}} (2)_{10} \xrightarrow{222^{th}} (3)_{10}$$

	Q_0	Q_1
	0	0
1 st	1	0
2 nd	1	1
3 rd	0	1
4 th	0	0


Mod no. 4

Initial state of the counter is $Q_0Q_1 = (00)_2$. What will the state of counter after application of 222 clock pulses ($\underline{3}$)₁₀.

[Question]

A sequential circuit is as given below :

H.W.

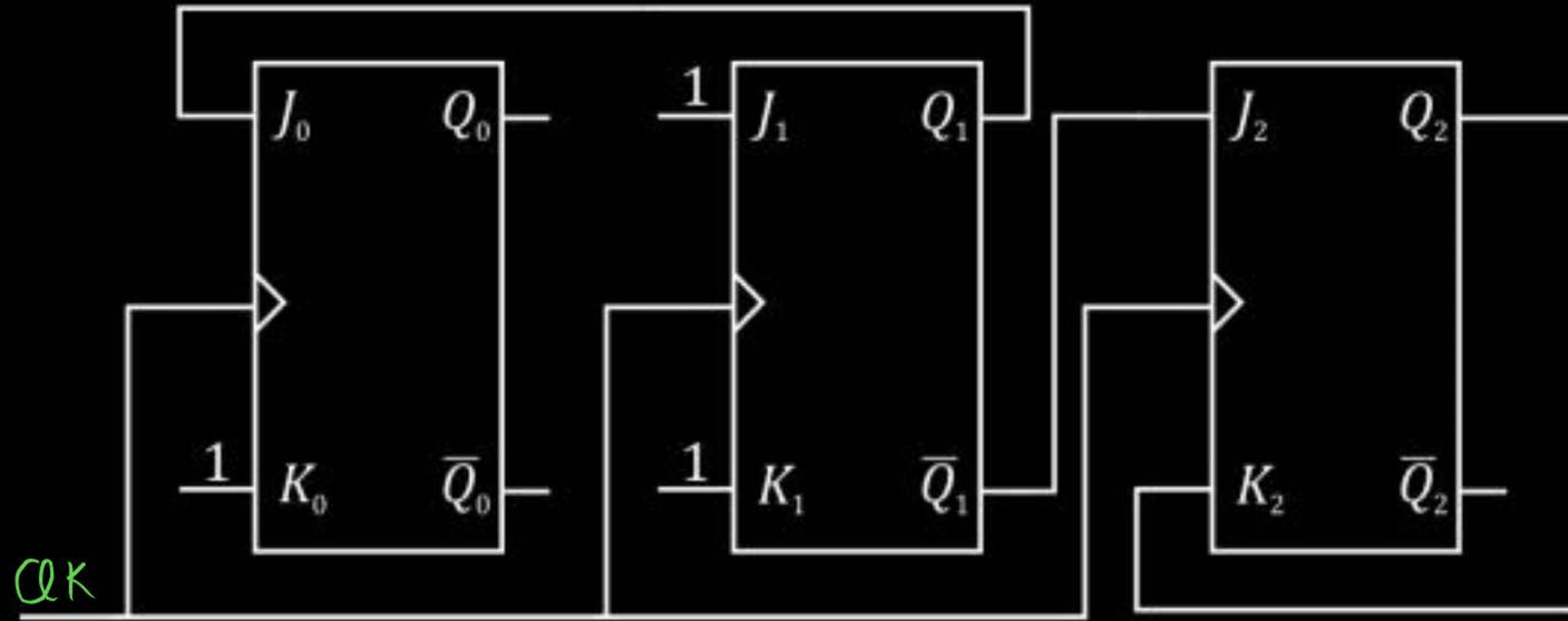


If initial state of counter is $Q_2Q_1Q_0 = (001)_2$, then after 8th clock pulse, counter will be in state ()₁₀.

[Question]

The output of the two FFs, Q_1 and Q_2 are initially at '0'. The sequence generated at Q_1 after application of clock pulses :

H.W.

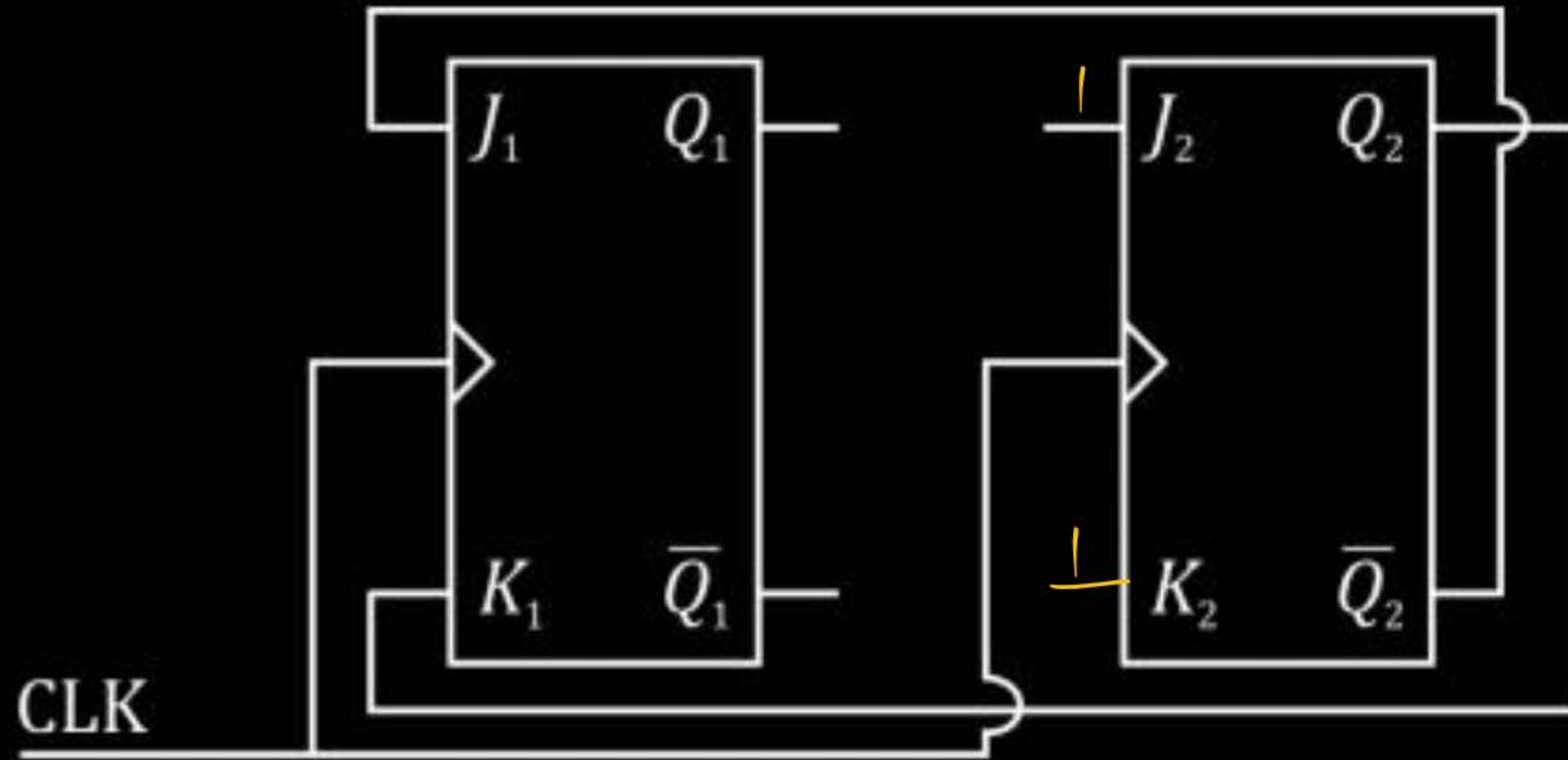

(a) 01110.....

(b) 01010.....

(c) 00110.....

(d) 01100.....



Topic : 2 Min Summary

→ Synchronous Counter

Thank you

GW
Soldiers !

