

COMPUTER SCIENCE & IT

DIGITAL LOGIC



Lecture No: 01

Sequential Circuit



By- Chandan Gupta Sir

Recap of Previous Lecture



Decoder & Encoder



Topics to be Covered

S-R latch


[**Sequential Circuit**] → O/P depends on present and past i/p values.



- Basic element of sequential circuit?

└→ SR latch

S-R Latch :

 

SR latch using NAND gate :

S	R	$Q(n+1)$
0	0	invalid state
0	1	1
1	0	0
1	1	$Q(n) \rightarrow$ hold state


→ Working :

- Concept of present state and next state :

S	R	$Q(n+1)$
0	0	invalid
0	1	1
1	0	0
1	1	$Q(n)$

- Invalid inputs : $S=0, R=0$ generates same value of Q & \bar{Q} and therefore they are invalid input state and will be never used on input side

SR latch using NOR gate :

 

S	R	$Q(n+1)$
0	0	$Q(n) \rightarrow \text{hold state}$
0	1	0
1	0	1
1	1	Invalid state

→ Working :

- Truth Table :

S	R	$Q(n+1)$
0	0	$Q(n)$
0	1	0
1	0	1
1	1	invalid state

$$S=0, R=1, Q(n)=? \quad Q(n+1)=0$$

$$S=0, R=0, Q(n)=0, Q(n+1)=0$$

$$S=1, R=0, Q(n)=0, Q(n+1)=1$$

$$S=0, R=0, Q(n)=1, Q(n+1)=1$$


- Invalid states :

$S=1, R=1$ is invalid state input because it generates output such that Q & \bar{Q} becomes same which is contradictory to design of latch.

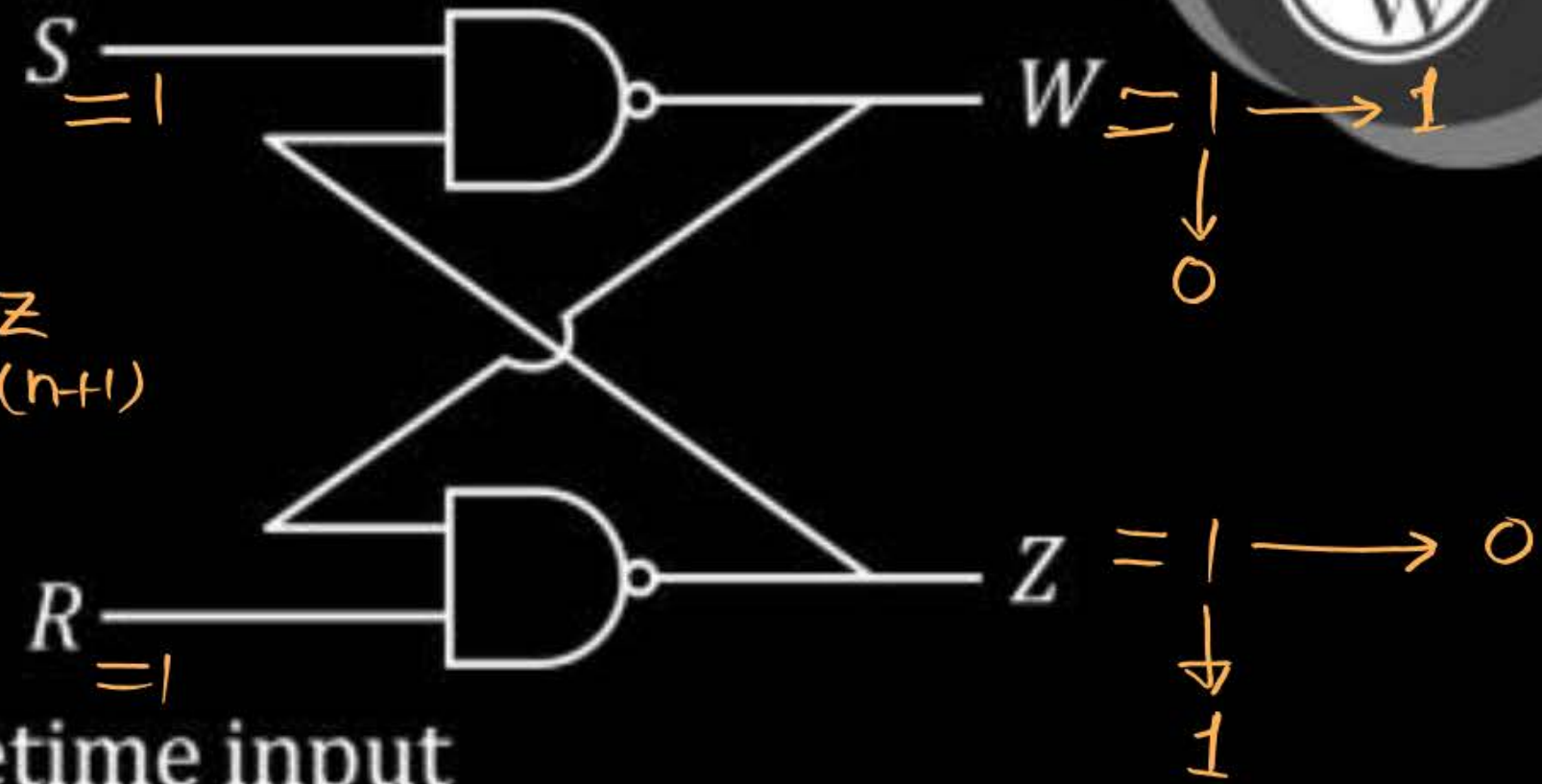[Question]

A NAND latch circuit is given below :

$S=0, R=0, Q(n)=?$, $Q(n+1)=1$, $\bar{Q}(n+1)=1$
 $S=1, R=1, Q(n)=1, \bar{Q}(n)=1 \rightarrow \overset{W}{Q}(n+1), \overset{Z}{\bar{Q}}(n+1)$



Initially input $S = R = 0$ and after sometime input changes from $S = R = 0$ to $S = R = 1$ then

(a) Output changes from $W = Z = 1$ to $W = Z = 1$.

✓ (b) Output changes from $W = Z = 1$ to either $W = 1$ and $Z = 0$ or $W = 0$ and $Z = 1$

(c) Output changes from $W = Z = 1$ to $W = Z = 0$


(d) None of these

- IMP Points :


Hold state i/p [NAND or NOR latch] will hold the present o/p in the next o/p if only if present output is a valid state [Q & \bar{Q} should be complement each other]. If present o/p state will be invalid o/p state [Q & \bar{Q} are same] then in next o/p, o/p will go to any of the valid state $(1, 0)$ or $(0, 1)$.

[S-R Flip-Flop]

- Circuit:

 

+ve level triggered FF

 

$$T_{CK} = T_{ON} + T_{OFF}$$

$$\% \text{ duty cycle} = \frac{T_{ON}}{T_{ON} + T_{OFF}} \times 100\%$$


$$= \frac{T_{ON}}{T_{CK}} \times 100\%$$



- Truth Table :

CLK	S	R	$Q(n+1)$
0	X	X	$Q(n)$
1	0	0	$Q(n)$
1	0	1	0
1	1	0	1
1	1	1	Invalid state

If circuit is changed to :

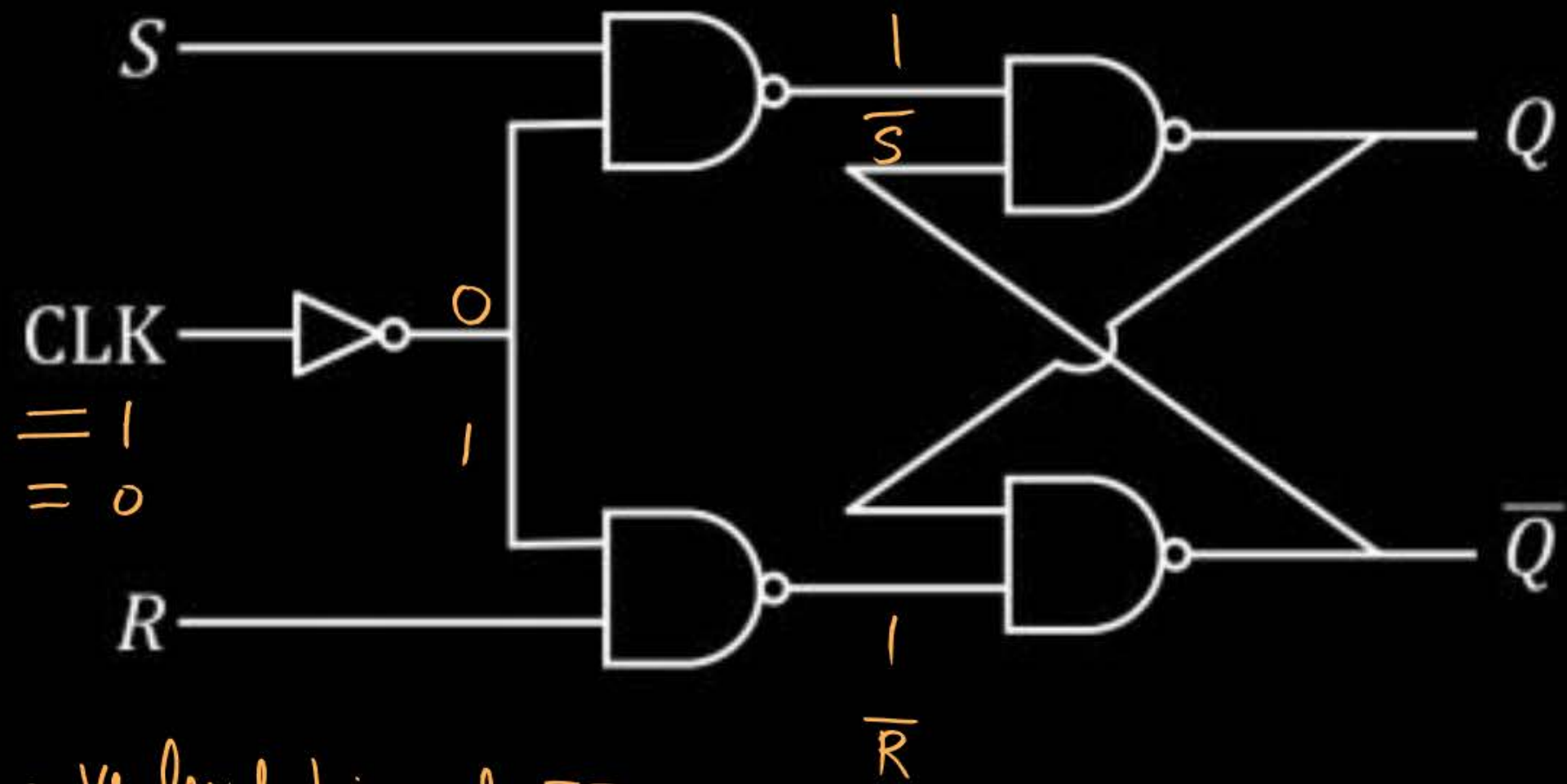


-ve level triggered FF

Then truth table will be :

CLK	S	R	$Q(n+1)$
CLK=1	X	X	$Q(n)$
CLK=0	0	0	$Q(n)$
CLK=0	0	1	0
CLK=0	1	0	1
CLK=0	1	1	Invalid State

[S-R FF – using NOR latch + Clock]

 

+ve level triggered FF.

Truth Table :

CLK	S	R	$Q(n+1)$
0	X	X	$Q(n)$
1	0	0	$Q(n)$
1	0	1	0
1	1	0	1
1	1	1	invalid state

[Characteristic Table of SR Flip-Flop]



When CKt is triggered

S	R	Q(n)	Q(n+1)
0	0	0	0
0	0	1	1
0	1	0	0
0	1	1	0
1	0	0	1
1	0	1	1
1	1	0	X
1	1	1	X

$$Q(n+1) [S, R, Q(n)] = \sum(1, 4, 5)$$

$$+ d \sum(6, 7)$$

Q(n+1)

	$\bar{R}\bar{Q}$	$\bar{R}Q$	RQ	$R\bar{Q}$
\bar{S}		1		
S	1	1	X	X

$$Q(n+1) = S + \bar{R}Q(n)$$


Valid only if $S \cdot R = 0$

[Excitation Table]

$Q(n)$	$Q(n+1)$	S	R
0	0	0	X
0	1	1	0
1	0	0	1
1	1	X	0

0	$\xrightarrow{(0,0)}$	0
0	$\xrightarrow{(0,1)}$	0
0	$\xrightarrow{(1,0)}$	1
1	$\xrightarrow{(0,1)}$	0
1	$\xrightarrow{(0,0)}$	1
1	$\xrightarrow{(1,0)}$	1

+ve level triggered S-R FF

 



Topic : 2 Min Summary

- S-R Latch
- SR FF

Thank you

GW
Soldiers !

