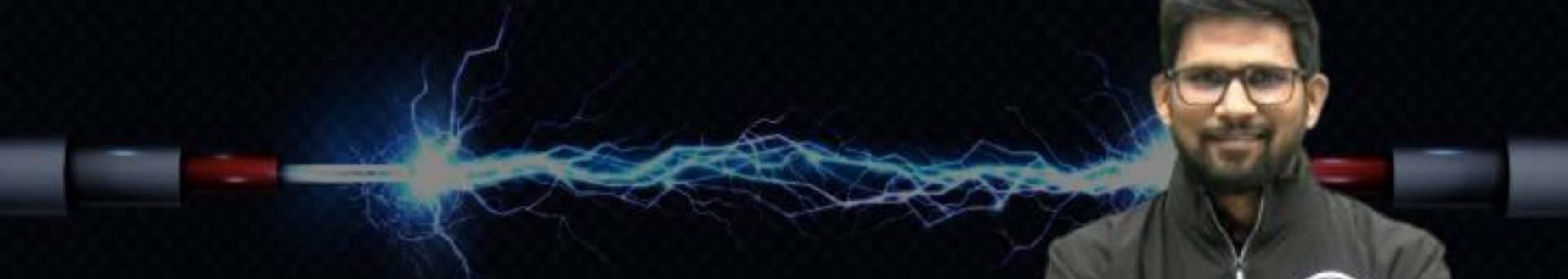


COMPUTER SCIENCE & IT

DIGITAL LOGIC




Lecture No. 08

Combinational Circuit



By- Chandan Gupta Sir



Recap of Previous Lecture

K-Map






Topics to be Covered


Comparator ckt



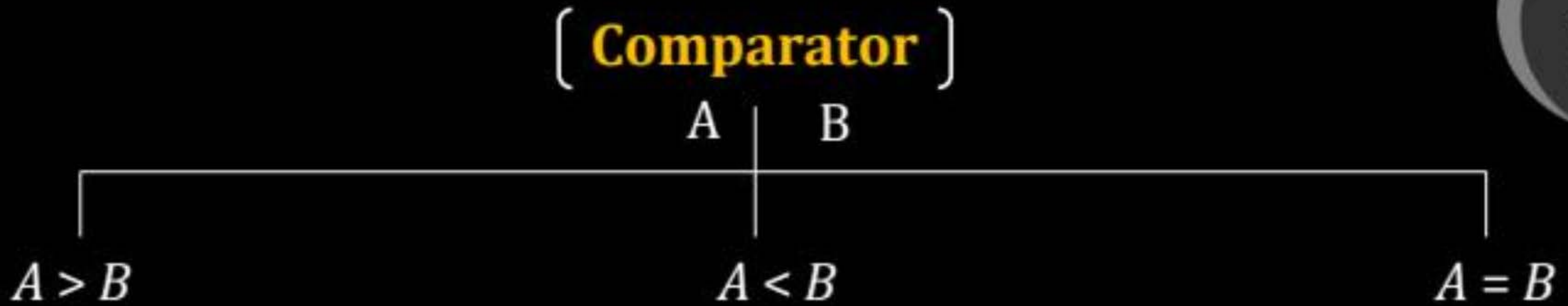


- A and B are single bit number then how to design comparator?

A	B	$y_1(A > B)$	$y_2(A < B)$	$y_3(A = B)$
0	0	0	0	1
0	1	0	1	0
1	0	1	0	0
1	1	0	0	1

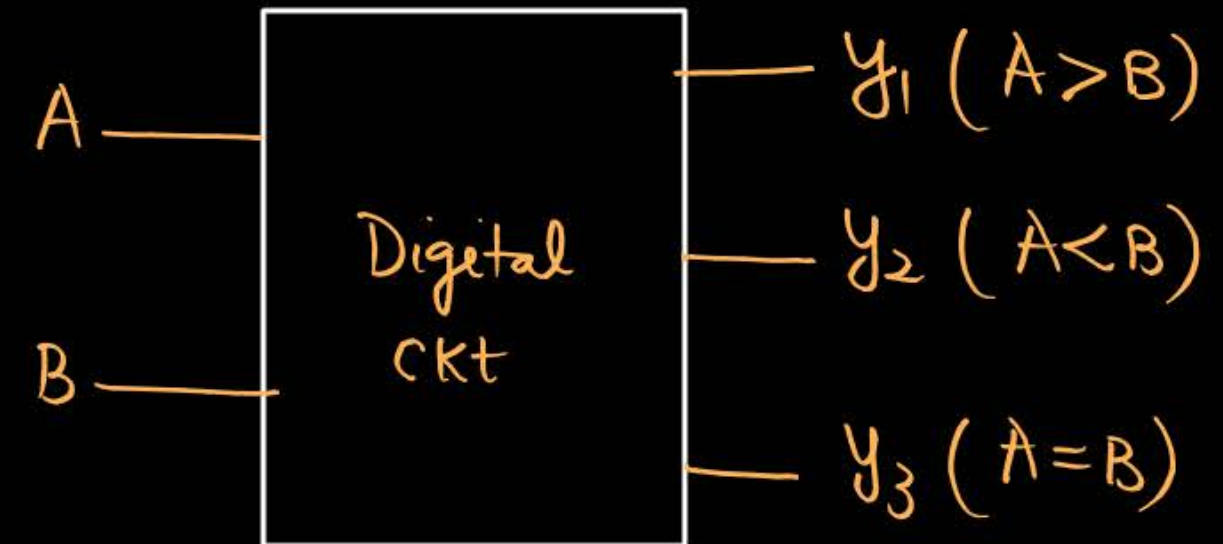

$$y_1(A, B) = \Sigma(2) \quad , \quad y_2(A, B) = \Sigma 1 \quad , \quad y_3(A, B) = \Sigma(0, 3)$$
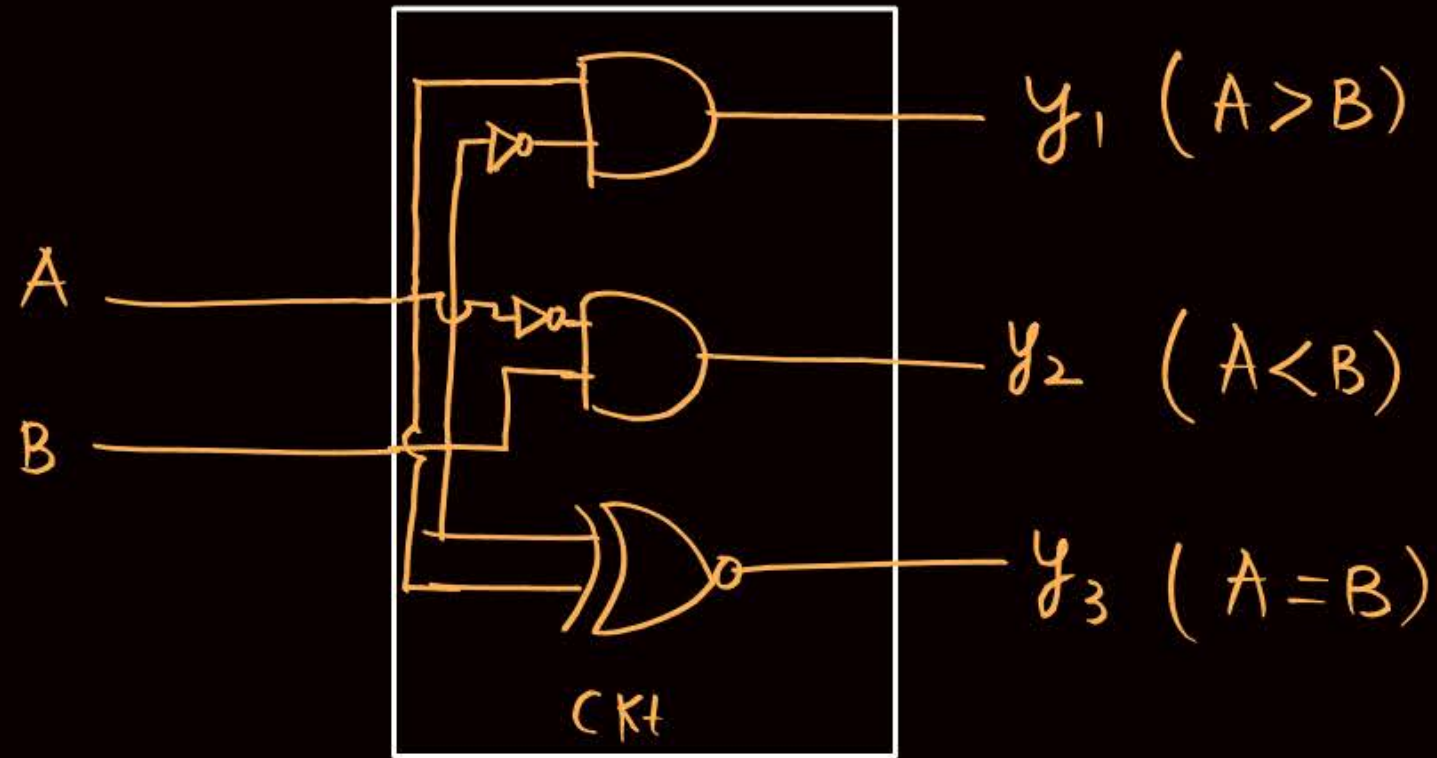
$$= A\bar{B} \quad \quad \quad = \bar{A}B \quad \quad \quad = \bar{A}\bar{B} + AB = A \odot B$$



- When A and B are 3-bit number then how to write the output of a comparator :

$$A = a_2 a_1 a_0$$


$$B = b_2 b_1 b_0$$

$$y_1(A > B) = (a_2 > b_2) + (a_2 = b_2) \cdot$$

$$+ (a_2 = b_2) \cdot (a_1 > b_1) + (a_2 = b_2) \cdot (a_1 = b_1) \cdot$$

$$+ (a_2 = b_2) \cdot (a_1 = b_1) \cdot (a_0 > b_0)$$
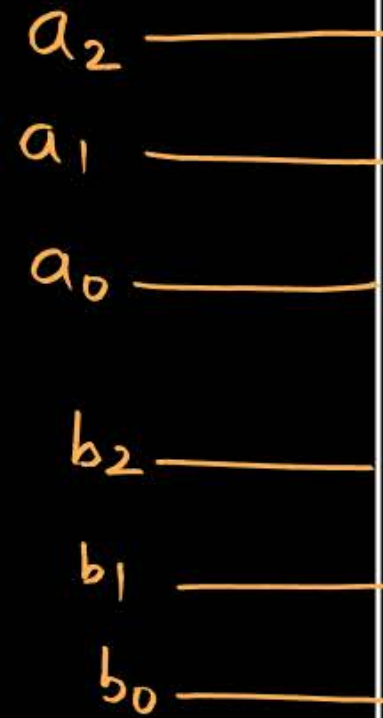
$$= a_2 \bar{b}_2 + (a_2 \odot b_2) \cdot (a_1 \bar{b}_1) + (a_2 \odot b_2) (a_1 \odot b_1) a_0 \bar{b}_0$$



$$y_2(A < B) = (a_2 < b_2) + (a_2 = b_2)(a_1 < b_1) + (a_2 = b_2)(a_1 = b_1)(a_0 < b_0)$$

$$= \bar{a}_2 b_2 + (a_2 \odot b_2) \cdot \bar{a}_1 b_1 + (a_2 \odot b_2)(a_1 \odot b_1) \cdot \bar{a}_0 b_0$$

$$y_3(A = B) = (a_2 = b_2) \cdot (a_1 = b_1) \cdot (a_0 = b_0) = (a_2 \odot b_2)(a_1 \odot b_1)(a_0 \odot b_0)$$

$$A = a_2 a_1 a_0$$

$$B = 0 b_1 b_0$$

$$\boxed{b_2 = 0}$$

$$y_1(A > B) = (a_2 > b_2) + (a_2 = b_2)(a_1 > b_1) + (a_2 = b_2)(a_1 = b_1)(a_0 > b_0)$$

$$= a_2 + \bar{a}_2(a_1 \bar{b}_1) + \bar{a}_2(a_1 \odot b_1) a_0 \bar{b}_0$$

$$y_2(A < B) = (a_2 < b_2) + (a_2 = b_2)(a_1 < b_1) + (a_2 = b_2)(a_1 = b_1)(a_0 < b_0)$$

$$= 0 + \bar{a}_2 \bar{a}_1 b_1 + \bar{a}_2 \cdot (a_1 \odot b_1) \bar{a}_0 b_0$$

$$y_3(A = B) = (a_2 \odot b_2)(a_1 \odot b_1)(a_0 \odot b_0)$$

$$= \bar{a}_2(a_1 \odot b_1)(a_0 \odot b_0)$$

$$A = a_1 a_0$$

$$B = b_1 b_0$$

A	B
0	0
1	1
2	2
3	3

$$N_1(A > B) = 0 + 1 + 2 + 3 = 6$$

$$N_2(A < B) = 0 + 1 + 2 + 3 = 6$$

$$N_3(A = B) = 4 = 2^2$$

$$A = n \text{ bit} \longrightarrow 0 \longrightarrow (2^n - 1)$$

$$B = n \text{ bit} \longrightarrow 0 \longrightarrow (2^n - 1)$$

↓
 $2^{2n} \longrightarrow \text{combinations}$

$$N_1(A > B) = 0 + 1 + 2 + 3 + \dots + (2^n - 1)$$

$$N_2(A < B) = 0 + 1 + 2 + 3 + \dots + (2^n - 1)$$

$$N_3(A = B) = 2^n$$

$$A = a_3 a_2 a_1 a_0 \Rightarrow 4 \text{ bit}$$

$$B = b_1 b_0 \Rightarrow 2 \text{ bit}$$



$$\downarrow$$

$$6 \text{ bits} \rightarrow 2^6 \rightarrow 64$$

A	B
0	0
1	1
2	1
3	2
⋮	⋮
⋮	3
⋮	⋮
14	⋮
15	⋮

$$N_1(A > B) = 0 + 1 + 2 + 3 + 4 + 11 \times 4 = 54$$

$$N_2(A < B) = 3 + 2 + 1 = 6 = (1 + 2 + 3)$$

$$N_3(A = B) = 4$$

$$N_2(B > A) = 0 + 1 + 2 + 3 = 6$$

$$A = n_1 \text{ bit} \Rightarrow 0 \text{ --- } (2^{n_1} - 1)$$

$$B = n_2 \text{ bit} \Rightarrow 0 \text{ --- } (2^{n_2} - 1)$$

$$(n_1 + n_2) \text{ bit}$$

$$2^{(n_1 + n_2)}$$

$$N'(A > B) = 2^{(n_1 + n_2)} - (N + M)$$

$$(n_1 > n_2)$$

$$N(B > A) = 0 + 1 + 2 + \dots + (2^{n_2} - 1)$$

$$M(B = A) = 2^{n_2}$$

A = 6 bit }
B = 3 bit } Total 9 bits

$$0 - (2^6 - 1)$$

$$0 - 63 \rightarrow A$$

$$\begin{array}{c} 0 - 7 - B \\ \hline \hline \end{array}$$

$$\downarrow \text{Total} = 2^3 = 8$$

$$N_1(A > B) = 2^9 - (28 + 8) = 512 - 36 = 476$$

$$N_2(A < B) = 0 + 1 + 2 + 3 + 4 + 5 + 6 + 7 = \frac{7 \times 8}{2} = 28$$

$$N_3(A = B) = 8$$

$$\begin{aligned} &1 + 2 + 3 + \dots + n \\ &= \frac{n(n+1)}{2} \end{aligned}$$

[Question]



We have two number A and B both A and B are 2-bit numbers then in how many combination $A > B$.

$$N_1(A > B) = N_2(A < B) = 0 + 1 + 2 + 3 = 6$$

(a) 5

✓ (b) 6

(c) 7

(d) 8

A — 0 — 3

B — 0 — 3

[Question]



We have two 4-bit number A and B then number of combinations in which $A < B$ _____

Number of combinations in which $A = B$ _____.

$$N_1(A > B) = N_2(A < B) = 0 + 1 + 2 + \dots + (2^4 - 1) = 0 + 1 + 2 + \dots + 15 = \frac{15 \times 16}{2} = 120$$

$$N_3(A = B) = 2^4 = 16$$



[Question]

Design a combinational circuit having 3-input and 1-output line.
The output is high when majority of input lines are at logic '0'.

H.W.


[Question] (H.W.)



Design a combinational circuit where input is 3-bit input and output is square of input number.

y_5

y_0

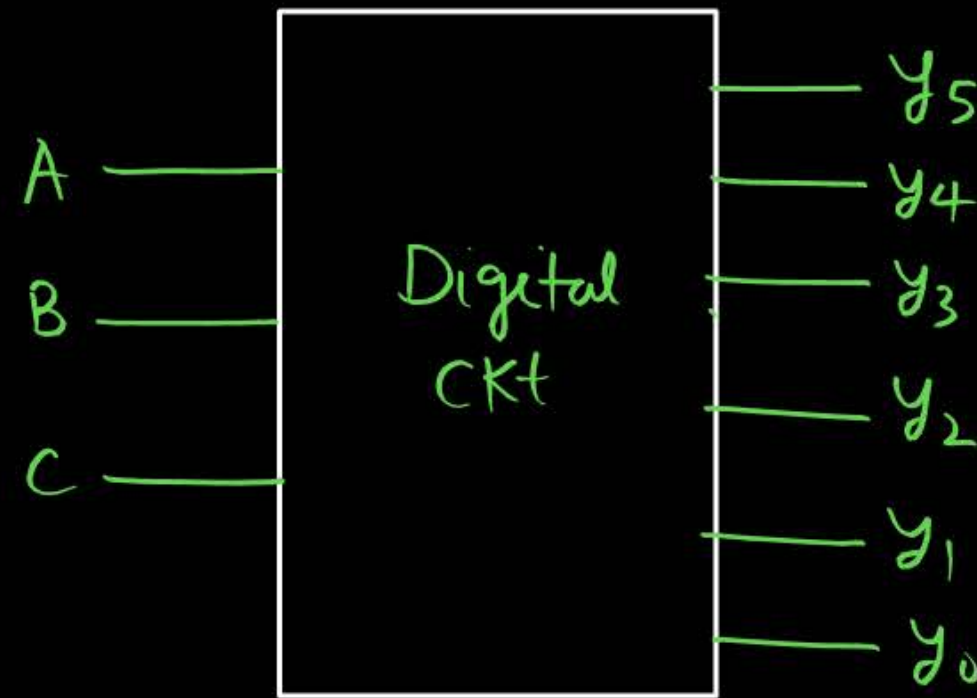

[Question]

H.W.



Design a combinational circuit where input is BCD code and output is '1' when input is divisible by 2.

[Question]

$$\begin{array}{ccc} A & \bar{B} & \\ 1 & 0 & 0 \rightarrow 4 \\ 1 & 0 & 1 \rightarrow 5 \end{array}$$

A logic circuit implements the Boolean function :

$$f(A, B, C) = A\bar{B} + \underbrace{\bar{A}\bar{B}\bar{C}}_{000} = \sum(0, 4, 5)$$

It is found that the input combination $B = 1$ and $C = 0$ can never occur. Then the simplified output $f(A, B, C)$ will be

(a) $\bar{B}\bar{C} + \bar{A}\bar{C}$

(b) $(A + \bar{C})(\bar{B} + \bar{C}) = \bar{C} + A\bar{B}$

(c) $\bar{A}\bar{B} + \bar{B}\bar{C}$

(d) None of these

$$\begin{array}{ccc} A & & \\ 0 & B=1, C=0 \rightarrow 2 \\ 1 & 1 & 0 \rightarrow 6 \end{array} \left. \vphantom{\begin{array}{ccc} A & & \\ 0 & B=1, C=0 \rightarrow 2 \\ 1 & 1 & 0 \rightarrow 6 \end{array}} \right\} \text{will never occur}$$

$$f(A, B, C) = \sum(0, 4, 5) + d\sum(2, 6)$$

	$\bar{B}\bar{C}$	$\bar{B}C$	BC	$B\bar{C}$
\bar{A}	1			X
A	1	1		X

$$= \bar{C} + (A\bar{B})$$

$$\begin{aligned} &= (\bar{C} + A) \cdot (\bar{C} + \bar{B}) \\ &= (\bar{B} + 0)(A + \bar{C}) \end{aligned}$$

H.W

Q.1. $A = 6 \text{ bit number}$
 $B = 8 \text{ bit number}$ $\longrightarrow N_1(A < B)$ _____.

Q.2. $A = 8 \text{ bit no.}$ $\longrightarrow N_2(A > B)$ _____.
 $B = 3 \text{ bit no.}$

Q.3. A is a 3 bit no. $a_2 a_1 a_0$ and B is a 5-bit no. $b_4 b_3 b_2 b_1 b_0$. Then
 logical o/p $y_1(A > B)$, $y_2(A < B)$ & $y_3(A = B)$ will be?



2 Minute Summary

- Comparator CKt and analysis
- Question Discussion.

Thank you

GW
Soldiers !

