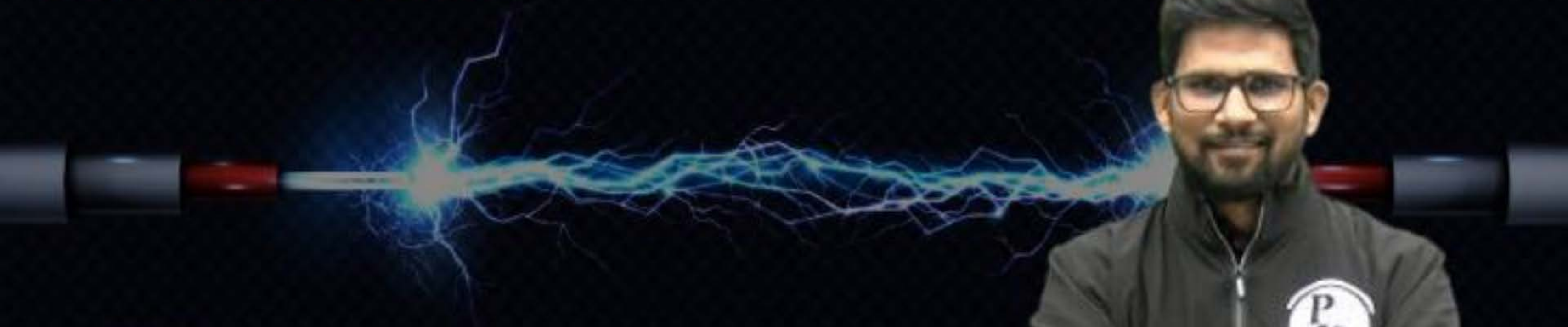


# COMPUTER SCIENCE & IT

## DIGITAL LOGIC




Lecture No. 04

**BOOLEAN THEOREMS AND  
GATES**



**By- Chandan Gupta Sir**



# Recap of Previous Lecture

Basic gates







# Topics to be Covered

Arithmetic gates


# [ XOR GATE ] 'Exclusive OR'



Representation:

$$\overline{1} \cdot 0 + 1 \cdot \overline{0} = 0 + 1 = 1$$
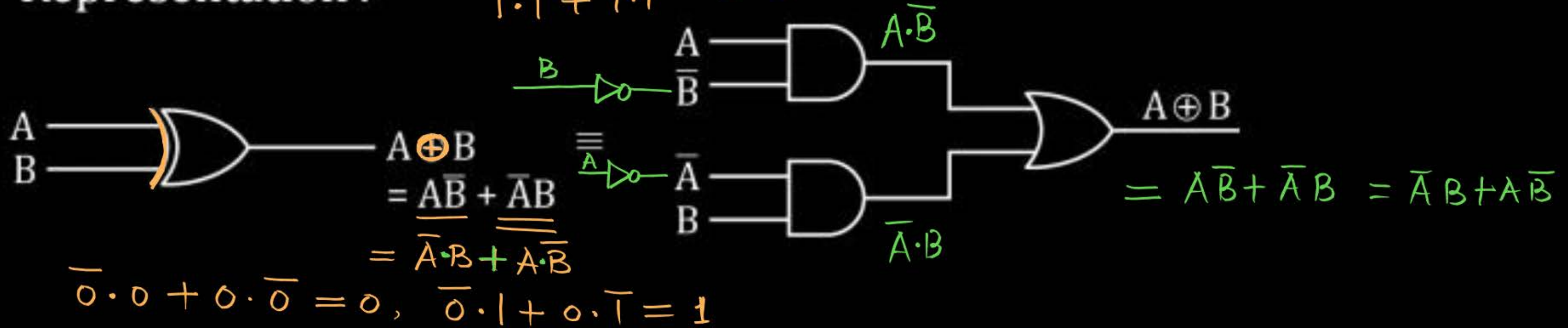
$$\overline{1} \cdot 1 + 1 \cdot \overline{1} = 0$$



	A	B	$y = A \oplus B$
0	0	0	$0 \oplus 0 = 0$
1	0	1	$0 \oplus 1 = 1$
2	1	0	$1 \oplus 0 = 1$
3	1	1	$1 \oplus 1 = 0$

$$\begin{aligned}
 y(A,B) &= \sum(1,2) \\
 &= \pi(0,3) \\
 &= \overline{A} \cdot B + A \cdot \overline{B} \\
 &= (A+B) \cdot (\overline{A} + \overline{B}) \checkmark
 \end{aligned}$$

$$x \oplus y = \overline{x} \cdot y + x \cdot \overline{y}$$

$$\begin{aligned}
 x \oplus \overline{y} &= \overline{x} \cdot \overline{\overline{y}} + x \cdot \overline{\overline{y}} \\
 &= \overline{x} \cdot y + x \cdot y
 \end{aligned}$$

$$\overline{x} \oplus \overline{y} = \overline{\overline{x}} \cdot \overline{\overline{y}} + \overline{x} \cdot \overline{\overline{y}} = x \cdot y + \overline{x} \cdot y$$



$$\bullet \quad x \oplus xy = \overline{x} \cdot xy + x \cdot \overline{xy} = 0 + x \cdot (\overline{x} + \overline{y}) = 0 + x\overline{y} = x\overline{y}$$



$$\begin{aligned} \bullet \quad xy \oplus yz &= \overline{xy} \cdot yz + xy \cdot \overline{yz} = (\overline{x} + \overline{y}) \cdot yz + xy(\overline{y} + \overline{z}) \\ &= \overline{x}yz + xy\overline{z} \\ &= y[\underline{\overline{x}z} + \underline{xy\overline{z}}] = y[x \oplus z] \end{aligned}$$

$$3 + 7 + 8 = 10 + 8 = 18$$

$$3 + 15 = 18$$

$$\underbrace{1 \oplus 0}_{=1} \oplus 1 = 1 \oplus 1 = 0$$

- Commutative Law :

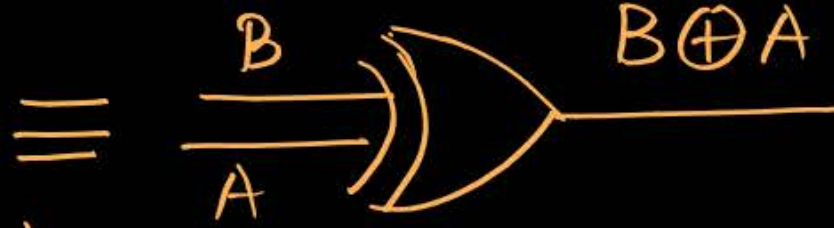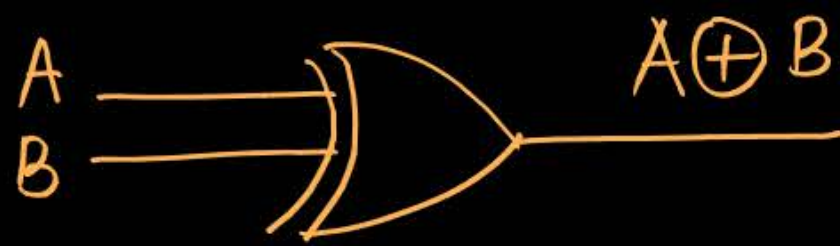

$$B \oplus A = A \oplus B$$

↳ It holds Commutative law.

↳ Position of variables is irrelevant

- Associative Law :

- It holds associative law  $\rightarrow$  meaning is that multi i/p XOR can be calculated using 2-i/p XOR operation.

$$A \oplus B \oplus C \Rightarrow (A \oplus B) \longrightarrow (A \oplus B) \oplus C$$

$$\Rightarrow (B \oplus C) \longrightarrow (B \oplus C) \oplus A = A \oplus B \oplus C$$

- Multi i/p XOR can be designed using 2-i/p XOR gate.

- Properties of XOR GATE :

- $A \oplus A = \bar{A} \cdot A + A \cdot \bar{A} = 0 \Rightarrow \bar{A} \oplus \bar{A} = 0$

- $A \oplus \bar{A} = \bar{A} \cdot \bar{A} + A \cdot \bar{\bar{A}} = \bar{A} + A = 1, \quad \bar{A} \oplus A = 1$

- $A \oplus A = 0 \Rightarrow A \oplus 0 = A = \bar{A} \cdot 0 + A \cdot \bar{0}$   
 $\quad \quad \quad = A$

$$\bar{A} \oplus 0 = \bar{A}$$

$$AB \oplus 0 = AB$$

- $A \oplus \bar{A} = 1 \Rightarrow A \oplus 1 = \bar{A} = \bar{A} \cdot 1 + A \cdot \bar{1} = \bar{A}$   
 $\quad \quad \quad \bar{A} \oplus 1 = A$

$$AB \oplus 1 = \overline{AB}$$



- Exchange properties of XOR GATE :

- $$A \oplus B = C \rightarrow \text{Given} \Rightarrow B \oplus A = C$$

$$A \oplus C = B \rightarrow \text{true}$$

$$\Rightarrow A \oplus C = A \oplus A \oplus B = 0 \oplus B = B$$

$$\Rightarrow B \oplus C = A \rightarrow \text{true}$$

$$B \oplus C = B \oplus A \oplus B = B \oplus B \oplus A = 0 \oplus A = A$$


- $A \oplus A \oplus A \oplus A \dots n \text{ times}$  [ $n$  - represents no. of  $A$ ]

then o/p = 0 for  $n$ -even

=  $A$  for  $n$ -odd

$$A \oplus A = 0$$

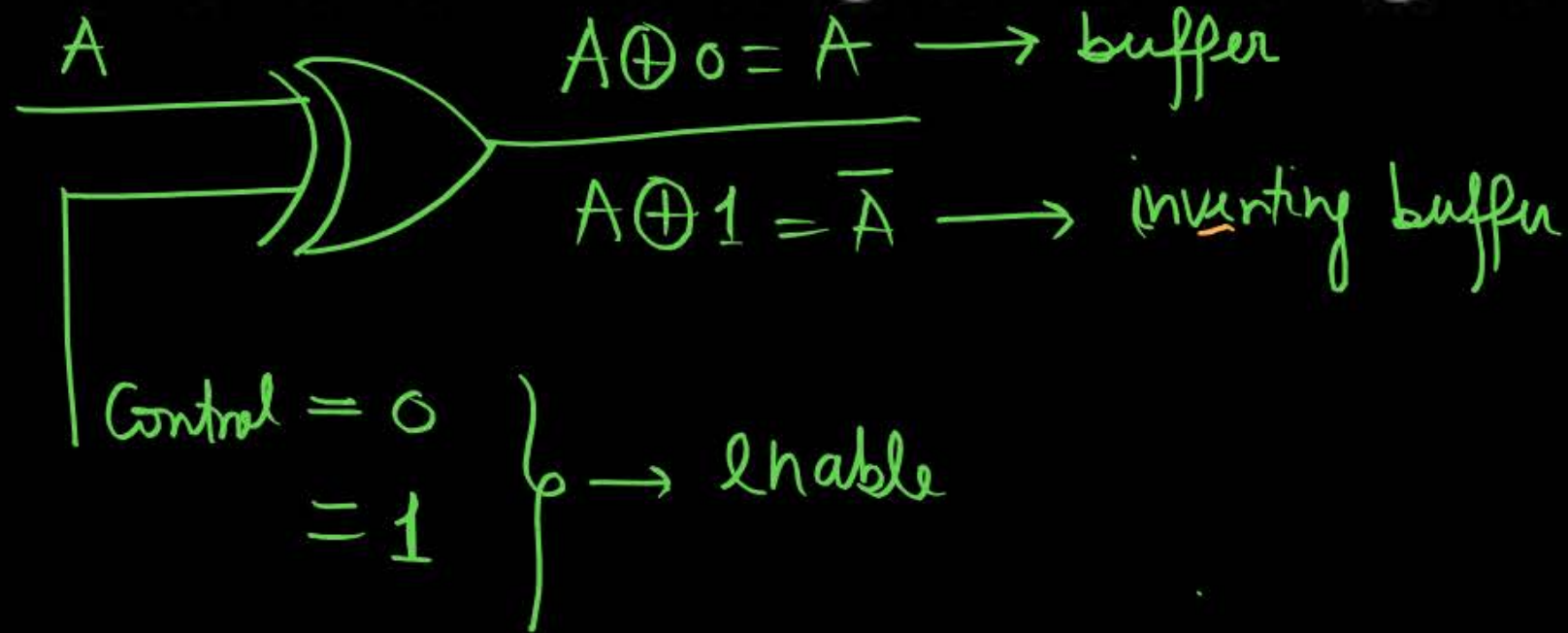- Buffer and inverting buffer using XOR :



$$\underbrace{A \oplus A} \oplus \underbrace{A \oplus A}$$

$$= 0 \oplus 0 = 0$$


$$\underbrace{A \oplus A} \oplus A = 0 \oplus A = A$$



# [XNOR GATE] 'Exclusive NOR'



Representation :

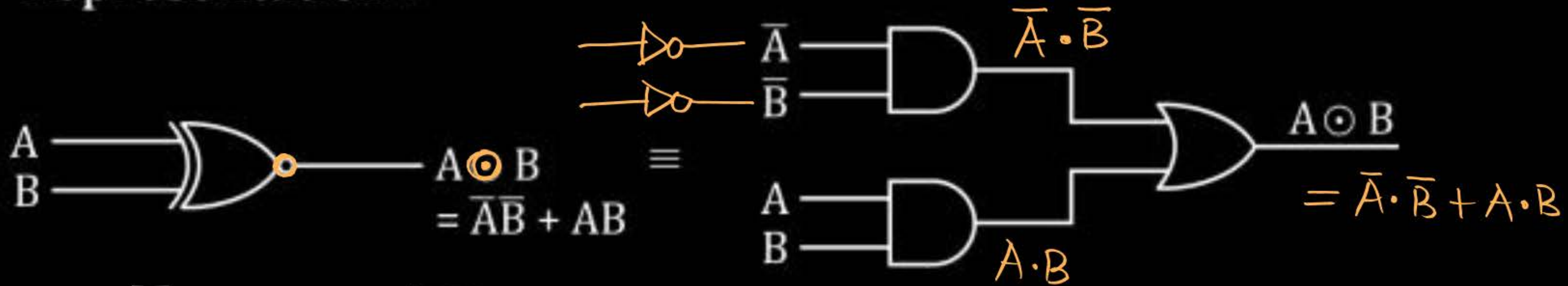

$$y_1 = \overline{y} \Rightarrow A \oplus B = \overline{A \odot B}$$

$$\overline{A \odot B} = A \odot B$$

$A \oplus B$

	A	B	$y = A \odot B$	$y_1$
0	0	0	$0 \odot 0 = 1$	0
1	0	1	$0 \odot 1 = 0$	1
2	1	0	$1 \odot 0 = 0$	1
3	1	1	$1 \odot 1 = 1$	0

$$A \odot B, y(A, B) = \sum(0, 3) = \prod(1, 2)$$

$$= \overline{A} \cdot \overline{B} + A \cdot B = (A + \overline{B}) \cdot (\overline{A} + B)$$

$$= (\overline{A} + B)(A + \overline{B})$$

$$A \oplus B = \sum(1, 2) = \prod(0, 3)$$

$$x \odot y = \overline{x} \cdot \overline{y} + x \cdot y$$


$$\overline{x} \odot y = \overline{\overline{x}} \cdot \overline{y} + \overline{x} \cdot y$$

$$= x \cdot \overline{y} + \overline{x} \cdot y = \overline{x} \cdot y + x \cdot \overline{y}$$

$$\overline{x} \odot \overline{y} = \overline{\overline{x}} \cdot \overline{\overline{y}} + \overline{x} \cdot \overline{y}$$

$$= x \cdot y + \overline{x} \cdot \overline{y}$$

- Commutative Law :

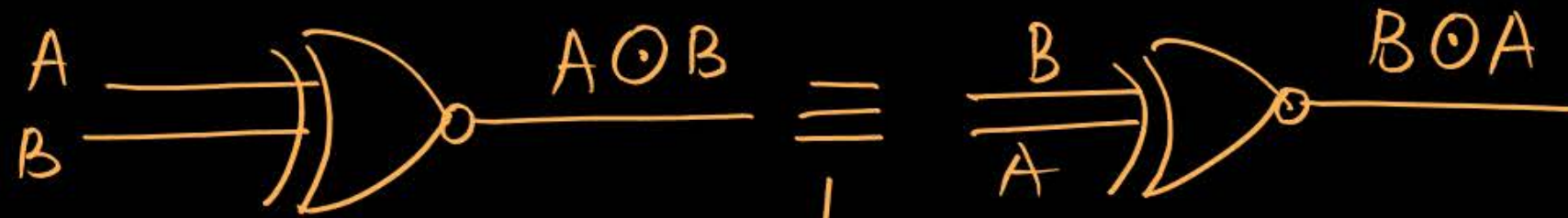

$$A \oplus B = B \oplus A$$

→ It holds commutative law.

→ Position of variable is irrelevant.



- Associative Law :

- It holds associative law  $\rightarrow$  meaning is that we can calculate multi i/p XNOR using 2-i/p XNOR operation.

$$A \odot B \odot C \Rightarrow (A \odot B) \Rightarrow (A \odot B) \odot C$$

$$\Rightarrow (B \odot C) \Rightarrow (B \odot C) \odot A = A \odot (B \odot C)$$

- That means, we can design multi i/p XNOR gate using 2-i/p XNOR gate.



## 2 Minute Summary

→ XOR & XNOR gates



**Thank you**

**GW**  
*Soldiers !*

