

COMPUTER SCIENCE & IT

DIGITAL LOGIC



Lecture No: 07

Miscellaneous Topics



By- Chandan Gupta Sir

Recap of Previous Lecture



- State transition Diagram
-
-



Topics to be Covered



Concept Delay



[MCQ]

Consider the following state diagram and its realization by a JK flip flop :
The combinational circuit generates J and K in terms of x, y and Q. The Boolean expressions for J and K are :

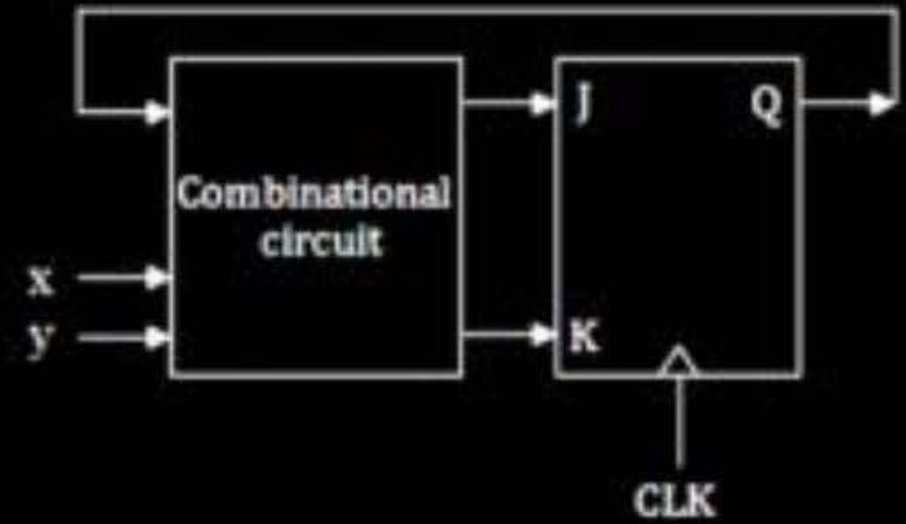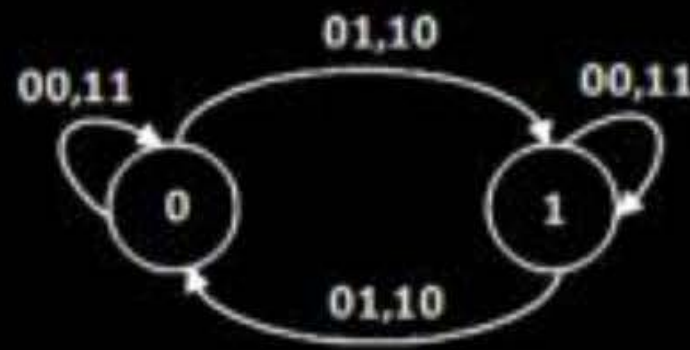- ☐ A $(x \oplus y)'$ and $(x \oplus y)'$ ✗
- ☐ B $(x \oplus y)'$ and $x \oplus y$ ✗
- ☐ C $x \oplus y$ and $(x \oplus y)'$ ✗
- ☒ D $x \oplus y$ and $x \oplus y$





x	y	$Q(n)$	$Q(n+1)$	J	K
0	0	0	0	0	X
0	0	1	1	X	0
0	1	0	1	1	X
0	1	1	0	X	1
1	0	0	1	1	X
1	0	1	0	X	1
1	1	0	0	0	X
1	1	1	1	0	X

$$Q(n+1) = P\bar{Q}(n) + \bar{P}Q(n)$$



$$Q(n+1) = P \oplus Q(n) = \underline{\underline{x \oplus y \oplus Q(n)}}$$

	$\bar{y}\bar{Q}$	$\bar{y}Q$	yQ	$y\bar{Q}$
\bar{x}		1		1
x	1		1	

$$\begin{aligned}
 Q(n+1) &= \bar{x}\bar{y}Q(n) + \bar{x}y\bar{Q}(n) + x\bar{y}\bar{Q}(n) + xyQ(n) \\
 &= (\bar{x}y + x\bar{y})\bar{Q}(n) + (\bar{x}\bar{y} + xy)Q(n) \\
 &= \underline{\underline{(x \oplus y)\bar{Q}(n)}} + \underline{\underline{(x \odot y)Q(n)}}
 \end{aligned}$$




Concept of Delay:

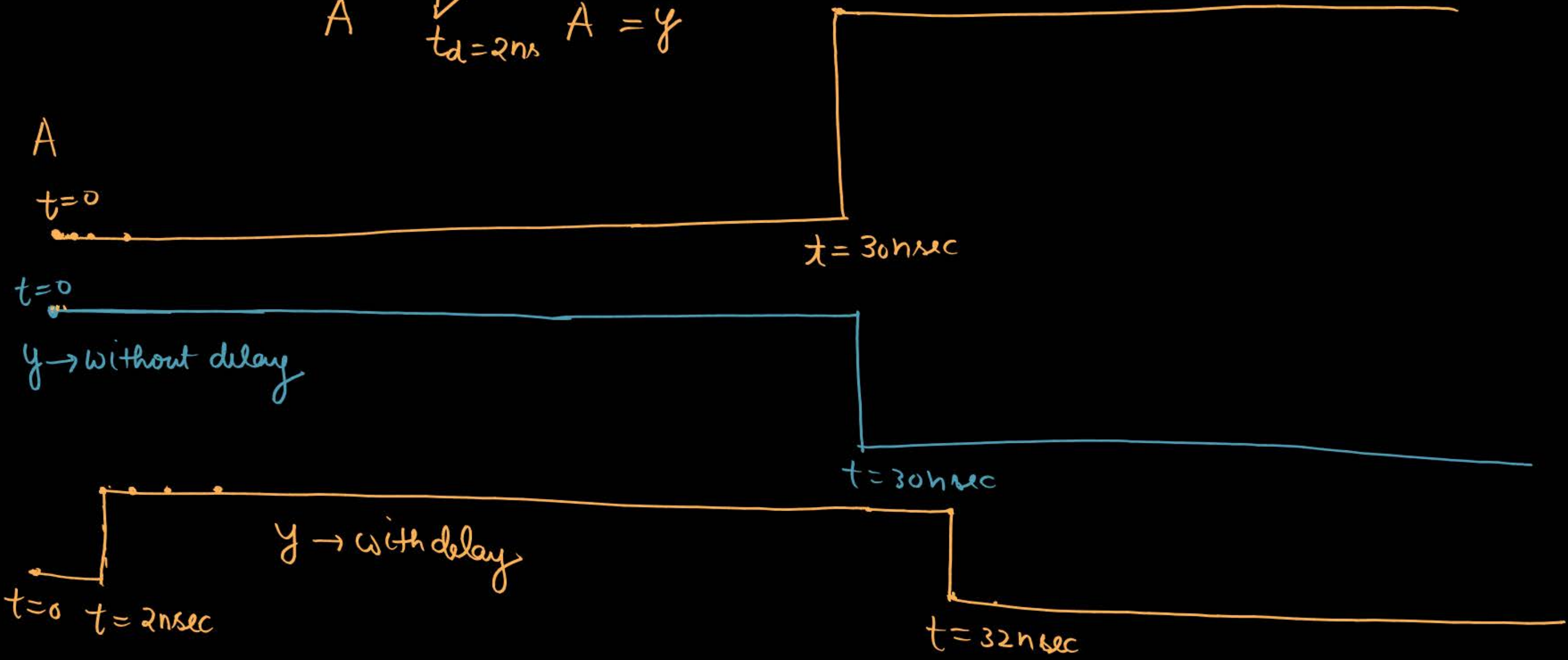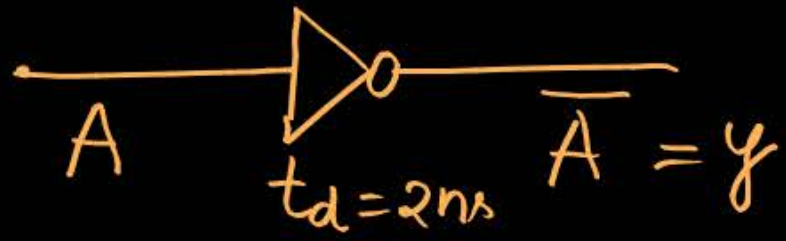




$y \rightarrow$ without delay

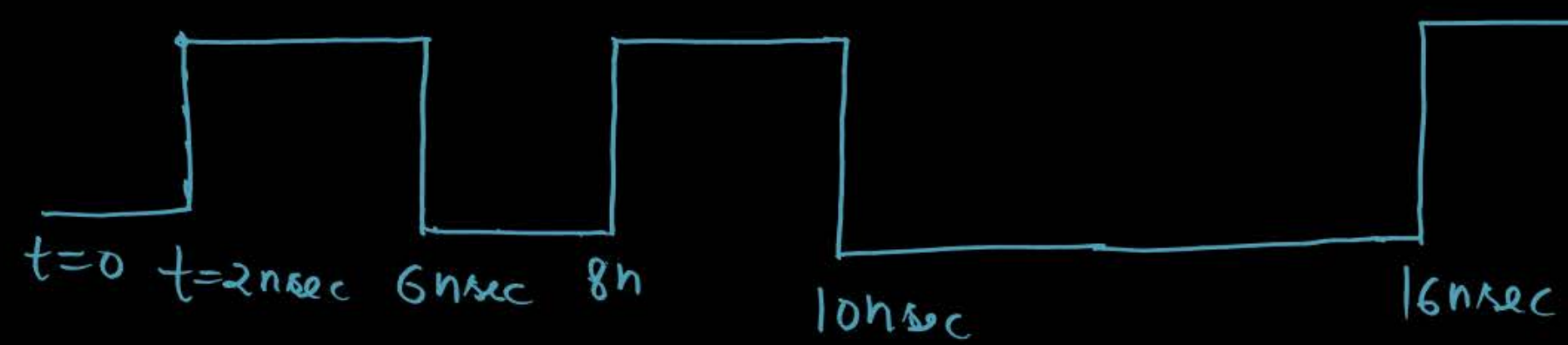

y with delay of 2ns


#

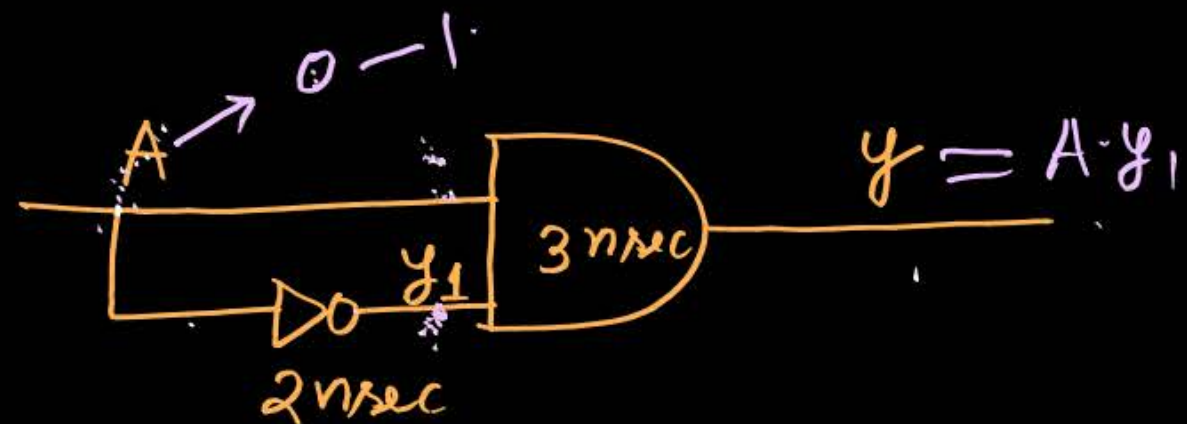


$$y_1 = \bar{A}$$

$$y = A \cdot \bar{A} = 0$$

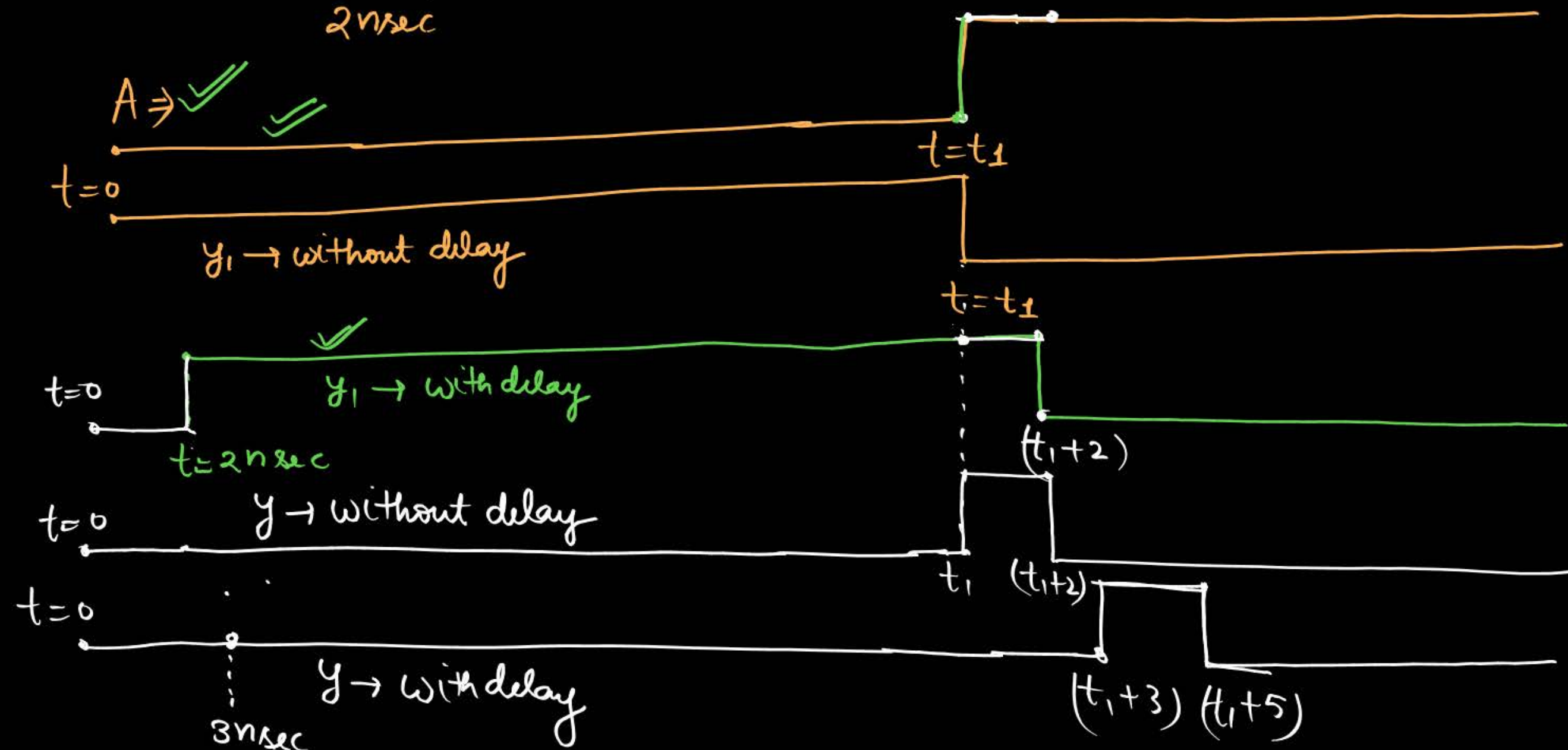
take O/P AND
gate to be NAND
gate
and plot
the waveform







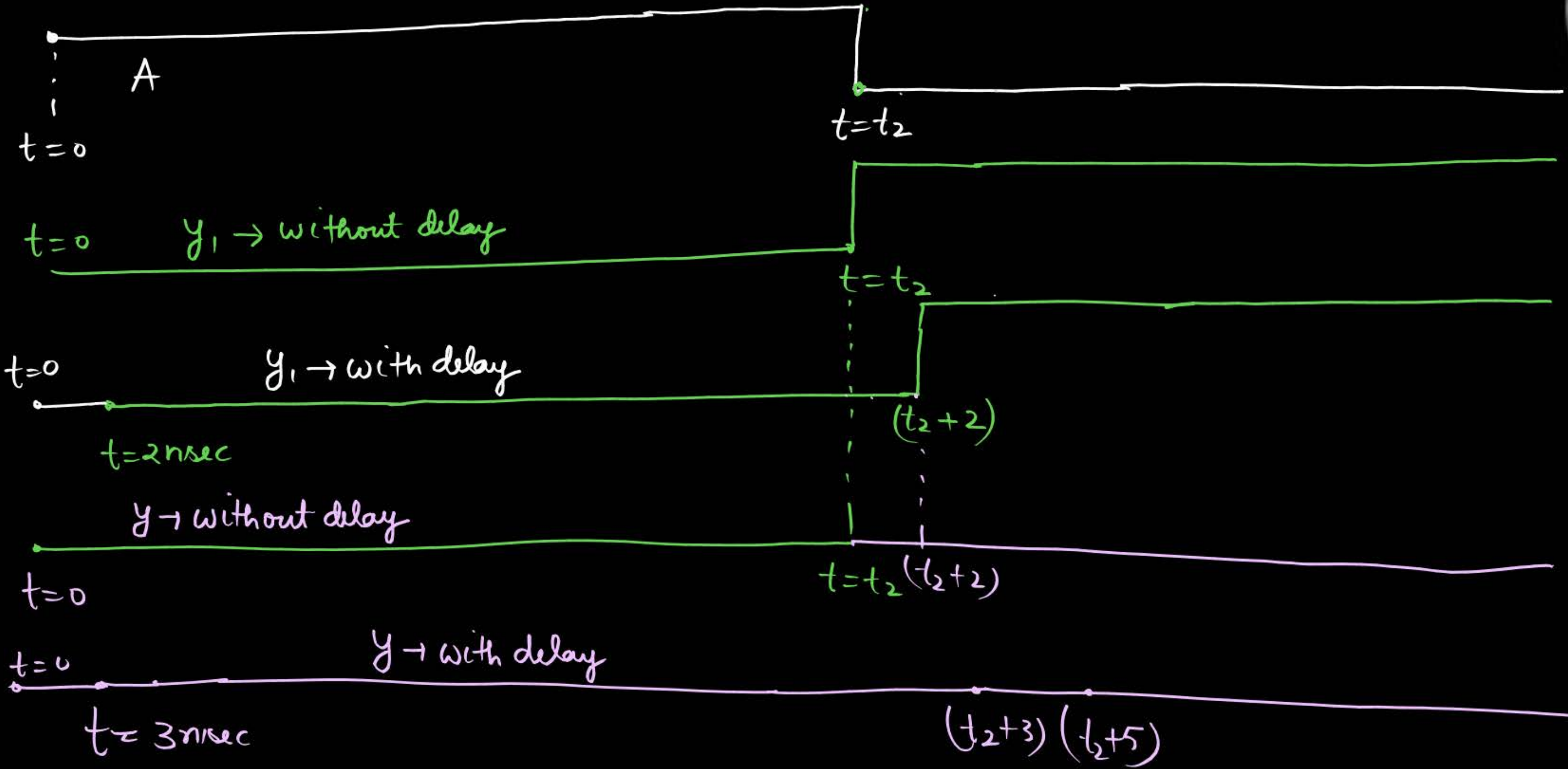



[MCQ]

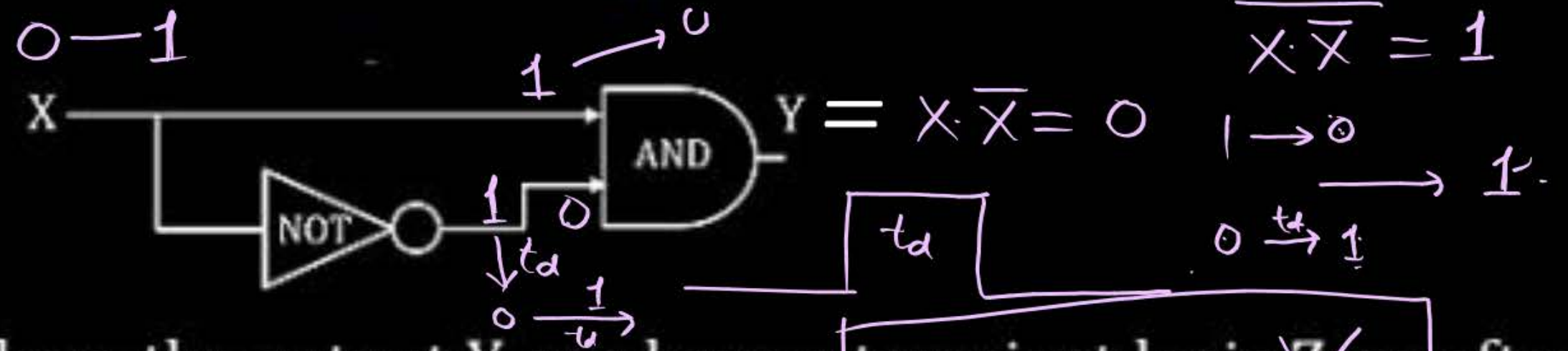
Consider the circuit shown below where the gates may have propagation delays. Assume that all signal transitions occur instantaneously and that wires have no delays. Which of the following statements about the circuit is/are CORRECT?



- ☐ A With propagation delays, the output Y can have a transient logic Zero after X transitions from logic One to logic Zero
- ☐ B With no propagation delays, the output Y is always logic One \times
- ☒ C With no propagation delays, the output Y is always logic Zero \checkmark
- ☒ D With propagation delays, the output Y can have a transient logic One after X transitions from logic Zero to logic One

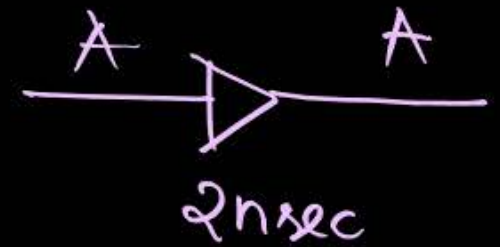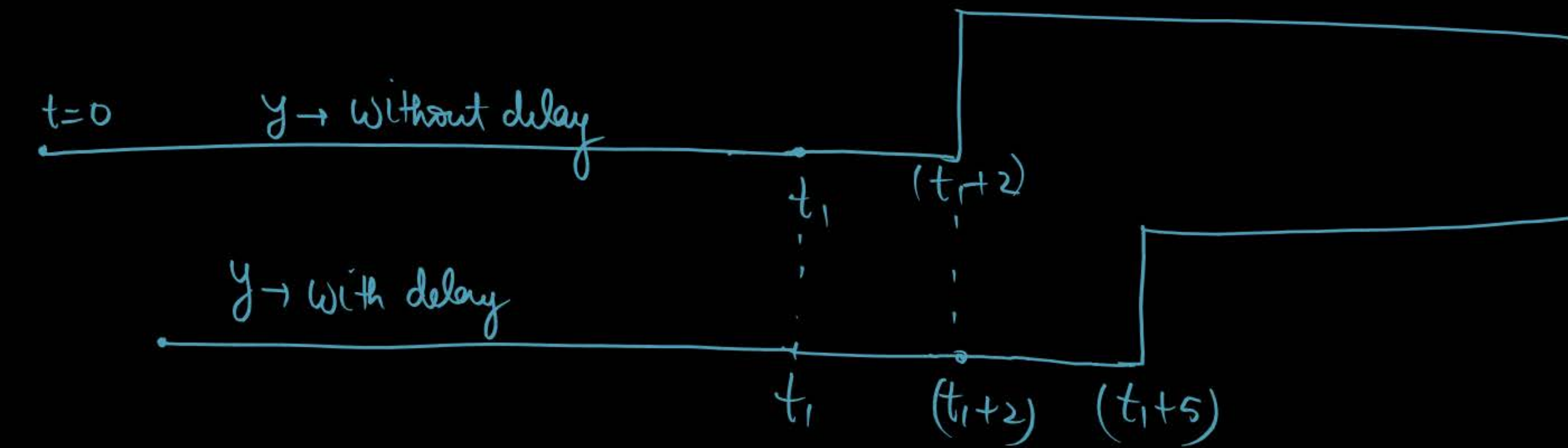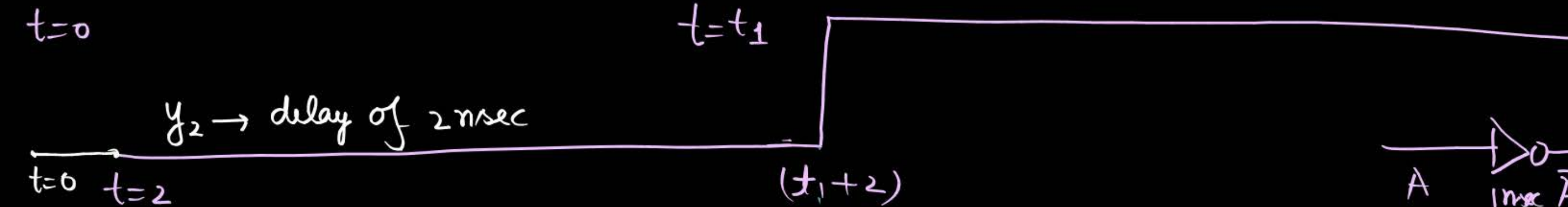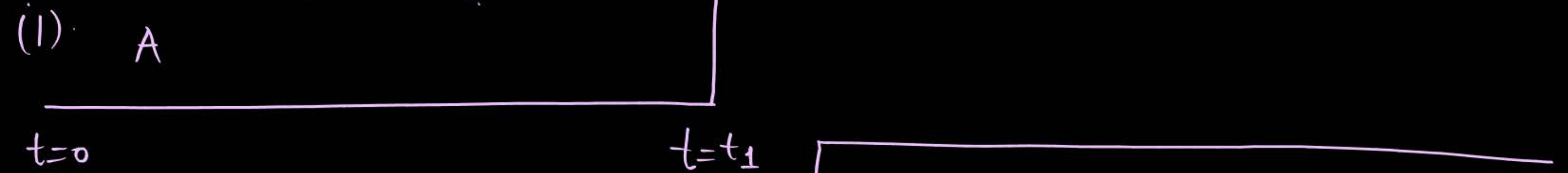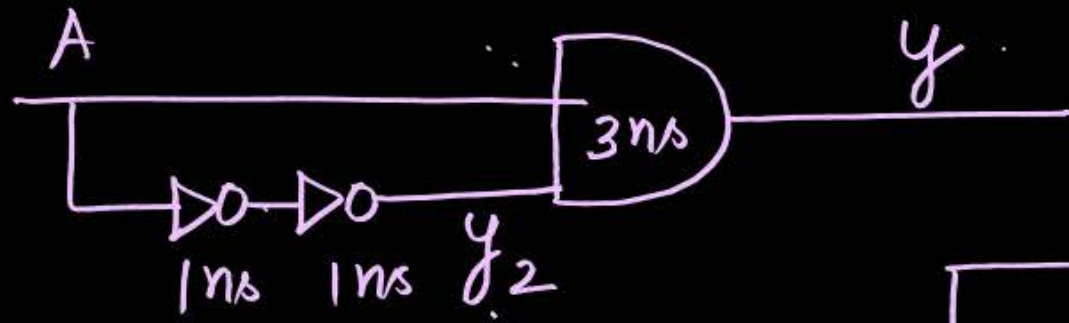

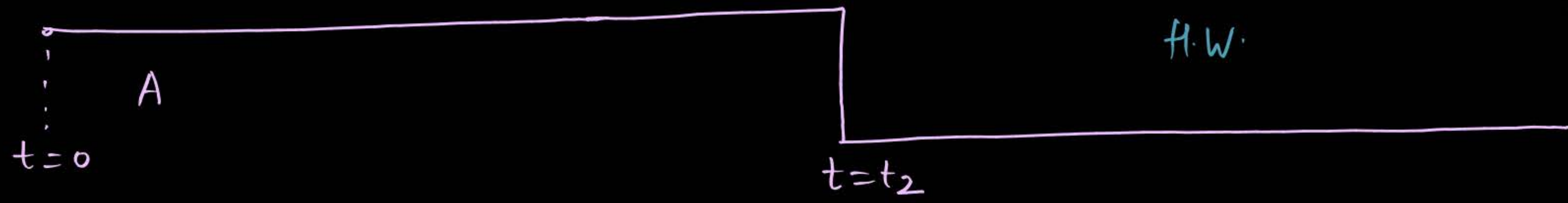

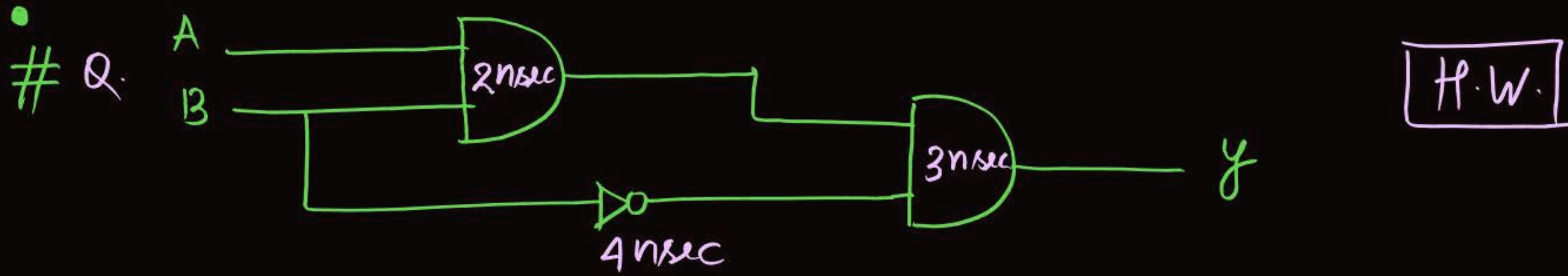

Initially $A=0$, $B=0$ for a long time and then A and B are changed to $(1,1)$ then
 o/p y will go '1' for a duration t_1 nsec after changing A & B from $(0,0)$ to $(1,1)$
 then value of t_1 _____ nsec.


Functionally Complete Function

- $f = \overline{A \cdot B} = \Sigma(0, 1, 2) = \left\{ \begin{matrix} \text{AND} \\ f_1 \end{matrix}, \begin{matrix} \text{NOT} \\ f_2 \end{matrix} \right\}$

- Total-0 preserving function: $[T_0]$

$$f(A, B, C) \Rightarrow f(0, 0, 0) = 0 \longrightarrow T_0$$

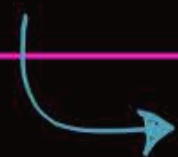$= 1 \longrightarrow$ it is not a total 0 preserving function.



$$f(A, B, \overline{C})$$

$$\begin{matrix} A=0 \\ B=0, \end{matrix} \quad \overline{C}=0$$

$$f(0, 0, 0) = 0 \longrightarrow T_0$$

$1 \longrightarrow$ it is not a T_0 .

Total - 1 preserving function: \rightarrow T_1 :

$$f(A, B, C) \Rightarrow f(1, 1, 1) = 1 \rightarrow T_1$$
$$= 0 \rightarrow \text{it is not a } T_1$$

$$f(A, \bar{B}, \bar{C})$$

$$\begin{matrix} A=1 \\ \bar{B}=1 \\ \bar{C}=1 \end{matrix} \left[\begin{array}{l} \rightarrow f(1, 1, 1) = 1 \rightarrow T_1 \\ = 0 \rightarrow \text{it is not a } T_1 \end{array} \right]$$

• Linear function: L:

$f(A, B, C) \longrightarrow$ is said to be linear if ^{all} for an even no. of 1's ^{combination} output is 1 & ^{linear} for an odd no. of 1's O/P is zero and vice versa.

$\Sigma (\quad)$

	A	B	y_1 ^{combination linear}	y_2 ^{non linear}	y_3 ^{non linear}	y_4 ^{non linear}	y_5 ^{linear}
\longrightarrow	0	0	0	0	0	0	1
\longleftarrow	0	1	1	1	1	0	0
\longleftarrow	1	0	1	0	1	0	0
\longrightarrow	1	1	0	1	1	1	1

Monotonic function M:

if any i/p is changed from 0—1 then if o/p is not decreasing then it is said to be monotonic function.

A	B	$\uparrow \underline{M}$	M	$\frac{NM}{Y_3}$	$\frac{NM}{Y_4}$	$\frac{NM}{Y_5}$	$\frac{NM}{Y_6}$
		Y_1	Y_2	Y_3	Y_4	Y_5	Y_6
0	0	0	0	1	1	0	1
0	1	1	0	1	0	1	0
1	0	1	0	1	0	1	0
1	1	1	1	0	0	0	1

Self Dual Boolean function S:

$$f^D = f$$

H.W

1. $f(A, B, C) = A + \bar{B}\bar{C} \longrightarrow T_0, T_1, L, M, S$

2. $f(A, B, \bar{C}) = \bar{A} + \bar{B}C \longrightarrow T_0, T_1, L, M, S$

3. $f(A, B, C) = AB + BC + CA \longrightarrow T_0, T_1, L, M, S$

4. $f(A, B) = \bar{A}\bar{B}$

5. $f(A, \bar{B}) = \bar{A}B$

Q. 6. $f(A, B) = \bar{A}B$

Q. 7. $f(A, B) = A + \bar{B}$

Q. 8. $f(\bar{A}, B) = \bar{A} + B$

Q. 9. $f(\bar{A}, B) = A + \bar{B}$

Q. 10. $f(A, \bar{B}) = A\bar{B}$



Topic : 2 Min Summary

- Concept of Delay
- Class of functions (boolean)

Thank you

GW
Soldiers !

